

Lecture 39

Memory:

- Memory element used in sequential circuits are relatively small and store few binary bits of information.
- Large memory capable of storing very large amount of information.
- Memories store data in units that have one, four, eight or higher number of bits.
- Smallest unit of binary data is a bit.
- Data is also handle in a 4-bit unit called a Nibble.
- The combination of two 4-bit units called Bytes.
- Each storage element of a memory can either store a logic 0 or

a logic 1 is called a cell.

Memory organization:

The memory array can be organized in several ways depending on the unit of data.

The 64-cell array organized as 8×8 cell array is considered as an 8 byte memory, that is, it has eight locations and each location store a single byte.

64-bit memory:

The 16×4 memory is used as a 16 nibble memory and the 64×1 is known as a 64 bit memory.

Memory capacity and density:

The capacity and the density of a memory are determined by the total number of cells implemented in a unit area.

Memory density on the other hand

specifies the number of bits store per unit area.

Basic operation on memory:

Two basic operation are performed on memory, that is,

- Reading of information from the memory
- Writing of data to the memory.

Address signals:

Address signals are required to specify the location in the memory from which information is accessed (read & write). A set of parallel address lines known as address bus carry the address information.

Memory select or enable signal:

In a computer system there are more than one memory chips to store program information.

All memory chips have a chip

enable or chip select signal which has to be activated before the memory can be accessed.

Memory types:

Two major categories of memory chips are

RAM (random access memory)

ROM (read only memory)

RAM:

- Ram allow a read or write operation to be carried out at any address.
- RAM don't store permanent data.
- All locations are accessible at equal time.
- RAM memory are also know as volatile memory.

Types of RAM:

Two types of RAM are given:

Static RAM

Dynamic RAM.

Static RAM:

Static RAM which uses

flip flops as storage element.

- In static Ram, each cell which is capable of storing a binary 0 or 1 is made up of flip flop which retain information.
- Static memory are faster.

Dynamic memory:

- Dynamic memory uses a capacitor to store a single bit of data.
- To store binary 1, capacitor is charged, to store 0, capacitor is uncharged.
- Dynamic memory is slower than static memory.

ROM:

- Rom chip retains data permanently.
- Rom chip are also know as non-volatile memory.
- ROM chips are read only, user can't write information.

ROM chip are programmed by the manufacturer.

3x8 decoder:

- A 3x8 decoder decodes a 3-bit address to select any one of eight location comprising of a group of 4-cells.
- For example, when the address is 000, the first output line of the 3x8 decoder is activated which is connected to the SEL input of 4 latches in the first row.

Subdivision of RAM:

Lecture 40

Subdivision of RAM:

RAM chips are subdivided into part are given:-

- Asynchronous RAM
- Synchronous SRAM.

Asynchronous SRAM:

The static memory described is an asynchronous SRAM, the operation of which does not depend upon the clock signal. The read and write operations are carried out asynchronously.

Synchronous SRAM:

Synchronous SRAM uses a clock signal which is used by microprocessor to synchronize its activities to synchronize the read and write operations for faster operation.

Drawback of DRAM:

The drawback of DRAM is the discharging of the capacitor over a period of time unless the capacitor is periodically recharged all the information stored in the form of binary bits in a capacitor based memory any

is lost.

The extra circuitry required to refresh the capacitor complicates the operation of the DRAM.

Address Multiplexing:

DRAM chips use address multiplexing to reduce the number of address lines by half.

The address required by to select a memory location is split into row and column address.

To access a DRAM location for reading or writing of information the row address is first applied at the address line.

Lecture 41

Fast mode page access:

In fast mode page access all the columns in the same row are either read or written.

A single row is considered to be

- 'Page' of memory storing data values in successive memory locations.
- The Fast Mode page access allows faster memory read and access times.

~~Distribub~~

Distributed mode:

In distributed mode, the refresh cycle is interspersed between normal read and write cycle.

Types of DRAMs:

- Types of DRAM are given below:-
- Fast page mode DRAM
 - Extended Data output (EDO) DRAM:
 - Synchronous DRAM

Types of ROM:

- ROMs are of different type are given:
- Mask ROM
 - PROM

- EPROM
- UV EPROM
- EEPROM

Mask ROM:

Data is permanently stored during the manufacturing process.

PROM:

- Programmable ROM allows storage of data by the user using a PROM programmer.
- The PROM once programmed store the data permanently.

EPROM:

Erasable PROM allows erasing and of stored data and reprogramming.

UV EPROM:

In a programmable ROM, Data is erase by exposing the PROM to ultraviolet light.

EEPROM:

Electrically erasable PROM is

is erased electrically.

- EEPROM allows in-circuit programming and does not need to be removed.

Types of EPROM:

Two types of EPROM are given:

- UV EPROM (ultraviolet EPROM)
- EEPROM (electrically erasable PROM)

Programming EPROM:

Programming the EPROM chip is done by applying a high dc voltage at V_{PP} pin and setting the output enable \overline{OE} to logic high.

Flash memory:

Flash memory have high density, that is, they store more information per unit area as more storage cells are implemented per unit area.

- These memories have read/write capability and are non-volatile and

can store for indefinite time period.

Flash memory operation:

Flash memory

have three operations:

- Programming operation
- Read operation
- Erase operation

Lecture 42

Flash memory array:

The flash memory array is arranged in the form of rows and columns. The row line is connected to the control gate of each MOS transistor which implements a single bit storage cell.

Types of memory:

Two types of memory

are given:-

FIFO (- first in first out)

LIFO (- last in first out)

FIFO memory:

- FIFO chips store this data in a memory stack with a FIFO style.

- This means that the data that is stored first is removed first.

- FIFO depth is the term given to the amount of memory that can be stored.

- FIFO memory is used for buffering application, when data need to be stored permanently.

LIFO memory:

- LIFO is a stack memory stored data.

- LIFO is short, last in first out.

- LIFO is a method of processing data, where the data last received is the first to be sent out after processed.

Lecture 43

Address decoders:

All memory chips have the first location identified by address zero.

The next location has the address one and successive memory locations have addresses assigned in an ascending order.

FPGAs:

An FPGA is a more flexible device than PLDs or instead of a single AND-OR gate array.

An FPGA device contains multiple logic blocks that can be individually programmed to perform different functions.

FPGA stand for field programming gate array.

Lecture 44

Single bit full-Adder:

A single bit Full-Adder can be similarly implemented by using a memory which has three storage locations.

Each storage location storing two bits.

A single bit full-Adder has three input variables A , B and C_{in} and two output variables Sum and C_{out} .

Analogue to digital conversion:

Analogue to digital converters single to are converted into digital signals by analogue to Digital (A/D) converter.

The conversion of analogue into a corresponding digital signal is done by first sampling the analogue signal and holding it stable for the A/D converter to convert the

signal into digital value.

Quantization:

The process of converting the analogue signal into a digital representation is known as quantization.

Operational Amplifier (Op-Amp):

Operational amplifier is a linear amplifier which has two input (inverting and non-inverting) and one output.


- It has a high voltage gain.

- high input impedance.

- low output impedance.

- Op-Amp is used as an inverting amplifier and as a comparator.

$$V_{out}/V_{in} = R_f/R_i$$

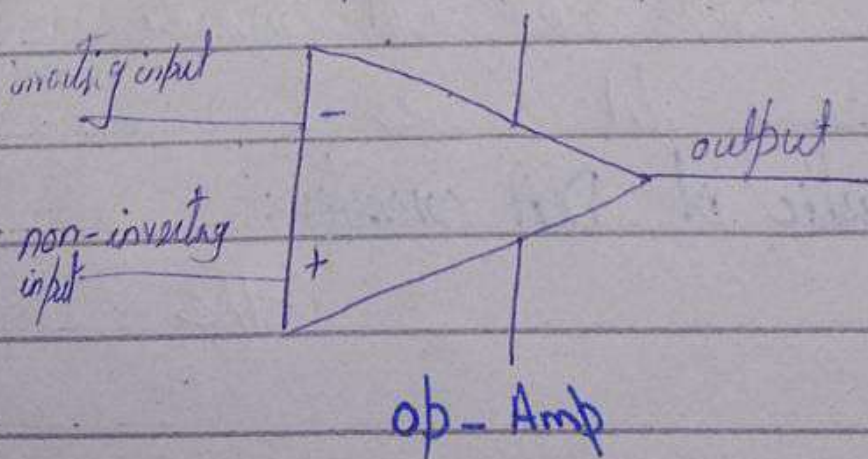

Dual-slope analogue to digital converter:

The Dual-slope A/D converter is used in digital voltmeter and other type of measuring instruments.

A Dual-slope A/D is slower than the flash converter.

Lecture 45

Analogue-to-Digital converter error:

There are three error are given below:

- Missing code
- Incorrect code
- Offset code

types of D/A converter:

There are two types are given:-

Binary-weighted-input D/A converter

R/2R ladder D/A converter

Characteristic of D/A converter:

The

characteristic of D/A converter are given below:

- Resolution
- Accuracy
- Linearity
- Monotonicity
- Settling time

Monotonicity:

In a monotonicity, the analogue output always increases or remains constant as the digital input increases.

End...