

Question No: 1 (Marks: 1) - Please choose one

A 8-bit serial in / parallel out shift register contains the value “8”, _____ clock signal(s) will be required to shift the value completely out of the register.

- ▶ 1
- ▶ 2
- ▶ 4
- ▶ **8 (Page 356) rep**

Question No: 2 (Marks: 1) - Please choose one

A frequency counter _____

- ▶ Counts pulse width
- ▶ **Counts no. of clock pulses in 1 second (Page 301)**
- ▶ Counts high and low range of given clock pulse
- ▶ None of given options

Question No: 3 (Marks: 1) - Please choose one

In a sequential circuit the next state is determined by _____ and _____

- ▶ State variable, current state
- ▶ Current state, flip-flop output
- ▶ Current state and external input
- ▶ **Input and clock signal applied (Page 305)**

Question No: 4 (Marks: 1) - Please choose one

The divide-by-60 counter in digital clock is implemented by using two cascading counters:

- ▶ **Mod-6, Mod-10 (Page 229) rep**
- ▶ Mod-50, Mod-10
- ▶ Mod-10, Mod-50
- ▶ Mod-50, Mod-6

Question No: 5 (Marks: 1) - Please choose one

In NOR gate based S-R latch if both S and R inputs are set to logic 0, the previous output state is maintained.

- ▶ **True (Page 221) rep**
- ▶ False

Question No: 6 (Marks: 1) - Please choose one

Flip flops are also called _____

- ▶ Bi-stable dualvibrators
- ▶ Bi-stable transformer
- ▶ **Bi-stable multivibrators (Page 228)**
- ▶ Bi-stable singlevibrators

Question No: 7 (Marks: 1) - Please choose one

The minimum time for which the input signal has to be maintained at the input of flip-flop is called _____ of the flip-flop.

- ▶ Set-up time
- ▶ **Hold time (Page 242) rep**
- ▶ Pulse Interval time
- ▶ Pulse Stability time (PST)

Question No: 8 (Marks: 1) - Please choose one

74HC163 has two enable input pins which are _____ and _____

- ▶ **ENP, ENT (Page 285)**
- ▶ ENI, ENC
- ▶ ENP, ENC
- ▶ ENT, ENI

Question No: 9 (Marks: 1) - Please choose one

_____ is said to occur when multiple internal variables change due to change in one input variable

- ▶ Clock Skew
- ▶ **Race condition (Page 267)**
- ▶ Hold delay
- ▶ Hold and Wait

Question No: 10 (Marks: 1) - Please choose one

Given the state diagram of an up/down counter, we can find _____

- ▶ **The next state of a given present state (Page 371)**
- ▶ The previous state of a given present state
- ▶ Both the next and previous states of a given state
- ▶ The state diagram shows only the inputs/outputs of a given states

Question No: 11 (Marks: 1) - Please choose one

The _____ input overrides the _____ input

- ▶ **Asynchronous, synchronous (Page 369) rep**
- ▶ Synchronous, asynchronous
- ▶ Preset input (PRE), Clear input (CLR)
- ▶ Clear input (CLR), Preset input (PRE)

Question No: 12 (Marks: 1) - Please choose one

A logic circuit with an output $X = \overline{A}BC + A\overline{B}$ consists of _____.

- ▶ two AND gates, two OR gates, two inverters
- ▶ three AND gates, two OR gates, one inverter
- ▶ **two AND gates, one OR gate, two inverters (Lecture 8)**
- ▶ two AND gates, one OR gate

Question No: 13 (Marks: 1) - Please choose one

A decade counter is _____.

- ▶ Mod-3 counter
- ▶ Mod-5 counter
- ▶ Mod-8 counter
- ▶ **Mod-10 counter (Page 274)**

Question No: 14 (Marks: 1) - Please choose one

In asynchronous transmission when the transmission line is idle, _____

- ▶ It is set to logic low
- ▶ **It is set to logic high (Page 356) rep**
- ▶ Remains in previous state
- ▶ State of transmission line is not used to start transmission


Question No: 15 (Marks: 1) - Please choose one

A Nibble consists of _____ bits

- ▶ 2
- ▶ **4 (Page 394)**
- ▶ 8
- ▶ 16

 Question No: 16 (Marks: 1) - Please choose one

The output of this circuit is always _____.



- ▶ 1
- ▶ 0
- ▶ **\bar{A} Click here for detail rep**
- ▶ $\bar{\bar{A}}$

Question No: 17 (Marks: 1) - Please choose one

Excess-8 code assigns _____ to “-8”

- ▶ 1110
- ▶ 1100
- ▶ 1000
- ▶ **0000 (Page 34) rep**

Question No: 18 (Marks: 1) - Please choose one

The voltage gain of the Inverting Amplifier is given by the relation _____

- ▶ **$V_{out}/V_{in} = -R_f/R_i$ (Page 446)**
- ▶ $V_{out}/R_f = -V_{in}/R_i$
- ▶ $R_f/V_{in} = -R_i/V_{out}$
- ▶ $R_f/V_{in} = R_i/V_{out}$

Question No: 19 (Marks: 1) - Please choose one
LUT is acronym for _____

- ▶ **Look Up Table (Page 439) rep**
- ▶ Local User Terminal
- ▶ Least Upper Time Period
- ▶ None of given options


Question No: 20 (Marks: 1) - Please choose one
DRAM stands for _____

- ▶ **Dynamic RAM (Page 407)**
- ▶ Data RAM
- ▶ Demoduler RAM
- ▶ None of given options

Question No: 21 (Marks: 1) - Please choose one
The three fundamental gates are _____

- ▶ AND, NAND, XOR
- ▶ OR, AND, NAND
- ▶ NOT, NOR, XOR
- ▶ **NOT, OR, AND (Page 40)**

 Question No: 22 (Marks: 1) - Please choose one



Which of the following statement is true regarding above block diagram?

- ▶ Triggering takes place on the negative-going edge of the CLK pulse
- ▶ Triggering takes place on the positive-going edge of the CLK pulse
- ▶ Triggering can take place anytime during the HIGH level of the CLK waveform
- ▶ Triggering can take place anytime during the LOW level of the CLK waveform

Question No: 23 (Marks: 1) - Please choose one
The total amount of memory that is supported by any digital system depends upon _____

- ▶ The organization of memory
- ▶ The structure of memory
- ▶ The size of decoding unit
- ▶ **The size of the address bus of the microprocessor (Page 430) rep**

Question No: 24 (Marks: 1) - Please choose one

The expression $F=A+B+C$ describes the operation of three bits _____ Gate.

▶ **OR (Page 42)**

- ▶ AND
- ▶ NOT
- ▶ NAND

Question No: 25 (Marks: 1) - Please choose one

Stack is an acronym for _____

- ▶ FIFO memory
- ▶ **LIFO memory (Page 429) rep**
- ▶ Flash Memory
- ▶ Bust Flash Memory

Question No: 26 (Marks: 1) - Please choose one

Addition of two octal numbers “36” and “71” results in _____

- ▶ 213
- ▶ 123
- ▶ **127**
- ▶ 345

Question No: 1 (Marks: 1) - Please choose one

The storage cell in SRAM is

- ▶ a flip –flop
- ▶ **a capacitor (Page 407)**
- ▶ a fuse
- ▶ a magnetic domain

Question No: 2 (Marks: 1) - Please choose one

What is the difference between a D latch and a D flip-flop?

- ▶ The D latch has a clock input.
- ▶ The D flip-flop has an enable input.
- ▶ The D latch is used for faster operation.
- ▶ **The D flip-flop has a clock input.** [Click here for detail](#)

Question No: 3 (Marks: 1) - Please choose one

For a positive edge-triggered J-K flip-flop with both J and K HIGH, the outputs will _____ if the clock goes HIGH.

▶ **toggle** [Click here for detail](#)

- ▶ set
- ▶ reset
- ▶ not change

Question No: 4 (Marks: 1) - Please choose one

The OR gate performs Boolean _____.

- ▶ multiplication
- ▶ subtraction
- ▶ division
- ▶ **addition (Page 42)**

Question No: 5 (Marks: 1) - Please choose one

If an S-R latch has a 1 on the S input and a 0 on the R input and then the S input goes to 0, the latch will be

- ▶ **set (Page 219)**
- ▶ reset
- ▶ invalid
- ▶ clear

5. Determine the values of A, B, C, and D that make the sum term $A(\bar{A}) + B + C(\bar{B}) + D$ equal to zero.

- ▶ A = 1, B = 0, C = 0, D = 0
- ▶ **A = 1, B = 0, C = 1, D = 0 (Lecture 8)**
- ▶ A = 0, B = 1, C = 0, D = 0
- ▶ A = 1, B = 0, C = 1, D = 1

Question No: 6 (Marks: 1) - Please choose one

The power dissipation, PD, of a logic gate is the product of the

- ▶ **dc supply voltage and the peak current** [Click here for detail](#)
- ▶ dc supply voltage and the average supply current
- ▶ ac supply voltage and the peak current
- ▶ ac supply voltage and the average supply current

Question No: 7 (Marks: 1) - Please choose one

A Karnaugh map is similar to a truth table because it presents all the possible values of input variables and the resulting output of each value.

- ▶ **True** [Click here for detail](#)
- ▶ False

Question No: 8 (Marks: 1) - Please choose one

NOR Gate can be used to perform the operation of AND, OR and NOT Gate

- ▶ **True (Page 50)**
- ▶ False

Question No: 9 (Marks: 1) - Please choose one

Using multiplexer as parallel to serial converter requires _____ connected to the multiplexer

▶ **A parallel to serial converter circuit (Page 244)**

- ▶ A counter circuit
- ▶ A BCD to Decimal decoder
- ▶ A 2-to-8 bit decoder

Question No: 10 (Marks: 1) - Please choose one

The 3-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

- ▶ 4
- ▶ **8 (Page 89)**
- ▶ 12
- ▶ 16

Question No: 11 (Marks: 1) - Please choose one

In designing any counter the transition from a current state to the next state is determined by

▶ **Current state and inputs (Page 332)**

- ▶ Only inputs
- ▶ Only current state
- ▶ current state and outputs

Question No: 12 (Marks: 1) - Please choose one

Sum term (Max term) is implemented using _____ gates

▶ **OR (Page 78)**

- ▶ AND
- ▶ NOT
- ▶ OR-AND

Question No: 13 (Marks: 1) - Please choose one

Given the state diagram of an up/down counter, we can find _____

- ▶ **The next state of a given present state (Page 371) rep**
- ▶ The previous state of a given present state
- ▶ Both the next and previous states of a given state
- ▶ The state diagram shows only the inputs/outputs of a given states

Question No: 14 (Marks: 1) - Please choose one

AT T0 THE VALUE STORED IN A 4-BIT LEFT SHIFT WAS "1". WHAT WILL BE THE VALUE OF REGISTER AFTER THREE CLOCK PULSES?

- ▶ 2
- ▶ 4
- ▶ 6
- ▶ **8 (not sure)**

Question No: 15 (Marks: 1) - Please choose one

WHEN BOTH THE INPUTS OF EDGE-TRIGGERED J-K FLOP-FLOP ARE SET TO LOGIC ZERO

- ▶ THE FLOP-FLOP IS TRIGGERED
- ▶ $Q=0$ AND $Q'=1$
- ▶ **$Q=1$ AND $Q'=0$ (Page 233)**
- ▶ THE OUTPUT OF FLIP-FLOP REMAINS UNCHANGED

Question No: 16 (Marks: 1) - Please choose one

If $S=1$ and $R=0$, then $Q(t+1) =$ _____ for positive edge triggered flip-flop

- ▶ 0
- ▶ **1 (Page 230)**
- ▶ Invalid
- ▶ Input is invalid

If $S=1$ and $R=1$, then $Q(t+1) =$ _____ for negative edge triggered flip-flop

- ▶ 0
- ▶ 1
- ▶ **Invalid (Page 233)**
- ▶ Input is invalid

Question No: 17 (Marks: 1) - Please choose one

The minimum time for which the input signal has to be maintained at the input of flip-flop is called _____ of the flip-flop.

- ▶ Set-up time
- ▶ **Hold time (Page 242) rep**
- ▶ Pulse Interval time
- ▶ Pulse Stability time (PST)

Question No: 18 (Marks: 1) - Please choose one

We have a digital circuit. Different parts of circuit operate at different clock frequencies (4MHZ, 2MHZ and 1MHZ), but we have a single clock source having a fix clock frequency (4MHZ), we can get help by

- ▶ Using S-R Flop-Flop
- ▶ D-flipflop
- ▶ **J-K flip-flop (Page 252)**
- ▶ T-Flip-Flop

Question No: 19 (Marks: 1) - Please choose one

A counter is implemented using three (3) flip-flops, possibly it will have _____ maximum output status.

- ▶ 3
- ▶ 7
- ▶ **8 (Page 272)**
- ▶ 15

Question No: 20 (Marks: 1) - Please choose one

In _____ Q output of the last flip-flop of the shift register is connected to the data input of the first flip-flop of the shift register.

- ▶ Moore machine
- ▶ Mealy machine
- ▶ Johnson counter
- ▶ **Ring counter (Page 355)**

Question No: 21 (Marks: 1) - Please choose one

The _____ of a ROM is the time it takes for the data to appear at the Data Output of the ROM chip after an address is applied at the address input lines

- ▶ Write Time
- ▶ Recycle Time
- ▶ Refresh Time
- ▶ **Access Time (Page 417)**

Question No: 22 (Marks: 1) - Please choose one

Bi-stable devices remain in either of their _____ states unless the inputs force the device to switch its state

- ▶ Ten
- ▶ Eight
- ▶ Three
- ▶ **Two (Page 262)**

Question No: 23 (Marks: 1) - Please choose one

_____ occurs when the same clock signal arrives at different times at different clock inputs due to propagation delay.

- ▶ Race condition
- ▶ **Clock Skew (Page 226) rep**
- ▶ Ripple Effect
- ▶ None of given options

Question No: 24 (Marks: 1) - Please choose one

The alternate solution for a multiplexer and a register circuit is _____

- ▶ **Parallel in / Serial out shift register (Page 356)**
- ▶ Serial in / Parallel out shift register
- ▶ Parallel in / Parallel out shift register
- ▶ Serial in / Serial Out shift register

Question No: 25 (Marks: 1) - Please choose one

Stack is an acronym for _____

- ▶ FIFO memory
- ▶ **LIFO memory (Page 429) rep**
- ▶ Flash Memory
- ▶ Bust Flash Memory

Question No: 26 (Marks: 1) - Please choose one

A full-adder has a Cin = 0. What are the sum (Σ) and the carry (Cout) when A = 1 and B = 1?

- ▶ = 0, Cout = 0
- ▶ = 0, Cout = 1 (Page 135)
- ▶ = 1, Cout = 0
- ▶ = 1, Cout = 1

Question No: 27 (Marks: 1) - Please choose one

THE GLITCHES DUE TO RACE CONDITION CAN BE AVOIDED BY USING A _____

- ▶ GATED FLIP-FLOPS
- ▶ PULSE TRIGGERED FLIP-FLOPS
- ▶ POSITIVE-EDGE TRIGGERED FLIP-FLOPS
- ▶ **NEGATIVE-EDGE TRIGGERED FLIP-FLOPS (Page 267)**

Question No: 28 (Marks: 1) - Please choose one

The design and implementation of synchronous counters start from _____

- ▶ Truth table
- ▶ k-map
- ▶ state table
- ▶ **state diagram (Page 319)**

Question No: 29 (Marks: 1) - Please choose one

THE HOURS COUNTER IS IMPLEMENTED USING _____

- ▶ ONLY A SINGLE MOD-12 COUNTER IS REQUIRED
- ▶ MOD-10 AND MOD-6 COUNTERS
- ▶ MOD-10 AND MOD-2 COUNTERS
- ▶ **A SINGLE DECADE COUNTER AND A FLIP-FLOP (Page 299)**

Question No: 30 (Marks: 1) - Please choose one

Given the state diagram of an up/down counter, we can find _____

- ▶ **The next state of a given present state (Page 371) rep**
- ▶ The previous state of a given present state
- ▶ Both the next and previous states of a given state
- ▶ The state diagram shows only the inputs/outputs of a given states

Question No: 31 (Marks: 1) - Please choose one

LUT is acronym for _____

- ▶ **Look Up Table (Page 439) rep**
- ▶ Local User Terminal
- ▶ Least Upper Time Period
- ▶ None of given options

Question No: 32 (Marks: 1) - Please choose one

_____ of a D/A converter is determined by comparing the actual output of a D/A converter with the expected output.

- ▶ Resolution
- ▶ **Accuracy (Page 460) rep**
- ▶ Quantization
- ▶ Missing Code

Question No: 33 (Marks: 1) - Please choose one

_____ is used to simplify the circuit that determines the next state.

- ▶ State diagram
- ▶ Next state table
- ▶ State reduction
- ▶ **State assignment (Page 335) rep**

Question No: 34 (Marks: 1) - Please choose one

The high density FLASH memory cell is implemented using _____

- ▶ **1 floating-gate MOS transistor (Page 419)**
- ▶ 2 floating-gate MOS transistors
- ▶ 4 floating-gate MOS transistors
- ▶ 6 floating-gate MOS transistors

Question No: 35 (Marks: 1) - Please choose one

Q2 := Q1 OR X OR Q3

The above ABEL expression will be

- ▶ Q2:= Q1 \$ X \$ Q3
- ▶ **Q2:= Q1 # X # Q3 (Page 210)**
- ▶ Q2:= Q1 & X & Q3
- ▶ Q2:= Q1 ! X ! Q3

Question No: 36 (Marks: 1) - Please choose one

Generally, the Power dissipation of _____ devices remains constant throughout their operation.

- ▶ **TTL (Page 65)**
- ▶ CMOS 3.5 series
- ▶ CMOS 5 Series
- ▶ Power dissipation of all circuits increases with time.

Question No: 37 (Marks: 1) - Please choose one

When the control line in tri-state buffer is high the buffer operates like a _____ gate

- ▶ AND
- ▶ OR
- ▶ **NOT (Page 196)**
- ▶ XOR

Question No: 38 (Marks: 1) - Please choose one

3.3 v CMOS series is characterized by _____ and _____ as compared to the 5 v CMOS series.

- ▶ Low switching speeds, high power dissipation
- ▶ Fast switching speeds, high power dissipation
- ▶ **Fast switching speeds, very low power dissipation (Page 61)**
- ▶ Low switching speeds, very low power dissipation