

# Lab Experiment # 11

## Sequential Circuits??

### Objectives

- To learn how to build combinational logic circuits using decoders.

### Background

