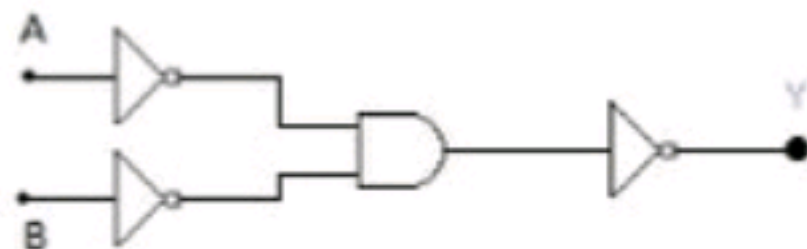


Question # 1 of 5 (Start time: 08:13:57 PM, 26 April 2024)

What will be the Boolean Equation for (Y) for the given Gate Level Diagram.




Select the correct option

<input type="radio"/>	$A'B'$
<input type="radio"/>	$A'B$
<input type="radio"/>	$A + B$
<input checked="" type="radio"/>	$A' + B$

Question # 4 of 5 (Start time: 03:50:49 PM, 03 May 2024)


DE Morgan's Theory is used to convert _____ gates to _____ ones.

Select the correct option

- | | |
|----------------------------------|------------------|
| <input type="radio"/> | AND/XOR, XOR/AND |
| <input type="radio"/> | AND/OR, NOR/NAND |
| <input checked="" type="radio"/> | AND/NAND, OR/NOR |
| <input type="radio"/> | OR/NOT, NOT/OR |
- 

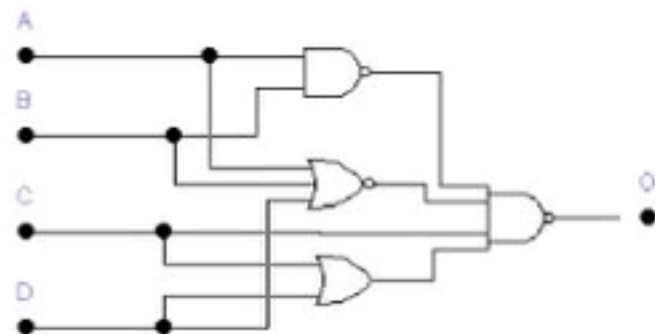Question # 10 of 10 (Start time: 10:12:16 AM, 07 May 2024)

What will be the simplified Boolean Expression of the stated Gate Level Diagram.



Select the correct option



$$A + B + C' + D$$



$$A + B' + C' + D$$



$$A' + B' + C' + D$$

Question # 3 of 10 (Start time: 10:01:14 AM, 23 May 2024)

In EWB, logic 1 is represented by using the _____ line

Select the correct option

<input checked="" type="radio"/>	V _{CC}
<input type="radio"/>	-V
<input type="radio"/>	Ground
<input type="radio"/>	V _{DD}

Question # 8 of 10 (Start time: 10:10:34 AM, 07 May 2024)

To draw a logic circuit for boolean expression $AB'+C$, how many gates are used?

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | 4 |
| <input type="radio"/> | 2 |
| <input checked="" type="radio"/> | 3 |
| <input type="radio"/> | 1 |

Question # 10 of 10 (Start time: 10:09:27 AM, 23 May 2024)

----- gate with a bubble at the output is know as NOR gate.

Select the correct option

<input type="radio"/>	NOT
<input type="radio"/>	AND
<input type="radio"/>	NAND
<input checked="" type="radio"/>	OR

Question # 5 of 10 (Start time: 10:04:21 AM, 23 May 2024)

The Boolean function $Z = A + B \cdot C'$ can be implemented in digital logic circuit by connecting _____ gates together.

Select the correct option


<input type="radio"/>	1	
<input checked="" type="radio"/>	3	<p>A hand-drawn logic circuit diagram in red ink. It shows three input lines labeled A, B, and C. Inputs A and B are connected to an OR gate, with the output labeled A+B. Input C is connected to an inverter gate, with the output labeled C'. The outputs of the OR gate (A+B) and the inverter gate (C') are connected to an AND gate. The output of the AND gate is labeled Z = ↑.</p>
<input type="radio"/>	4	
<input type="radio"/>	2	

Question # 4 of 10 (Start time: 10:02:47 AM, 23 May 2024)

According to De-Morgan's law, which of the following is TRUE?

Select the correct option

<input type="radio"/>	$A \cdot B = (A' \cdot B)'$
<input type="radio"/>	$(A + B)' = (A' + B)'$
<input type="radio"/>	$A + B = (A' \cdot B)'$
<input type="radio"/>	$A + B = (A + B)'$



Question # 2 of 10 (Start time: 09:59:41 AM, 23 May 2024)

According to the commutative law of Boolean algebra, which of the following expression is **TRUE**?

Select the correct option

<input type="radio"/>	$A.B = A+B$
<input checked="" type="radio"/>	$A.B = B.A$
<input type="radio"/>	$A.B' = A'.B$
<input type="radio"/>	$A'.B' = A.B$

Question # 2 of 5 (Start time: 10:35:27 AM, 05 July 2024)

An identify comparator is defined as a digital comparator which has -----

Select the correct option

<input type="radio"/>	Three output terminals
<input type="radio"/>	Only one output terminal
<input type="radio"/>	No output terminals
<input checked="" type="radio"/>	Two output terminals

Question # 4 of 5 (Start time: 10:36:54 AM, 05 July 2024)

Which of the following is an invalid BCD code?

Select the correct option

<input type="radio"/>	1001
<input checked="" type="radio"/>	1101 , 1010 , 1011 , 1100 , 1110 , 1111
<input type="radio"/>	0011
<input type="radio"/>	0101

The Gray Code

The Gray code does not have any weights assigned to its bit positions. The Gray Code is not a positional code. The Gray code is different from the unsigned binary code as successive values of Gray code differ by only one bit. Table 4.5 shows the Gray Code representation of Decimal numbers 0 to 9.

Decimal	Gray	Binary
0	0000	0000
1	000 1	0001
2	00 11	0010
3	00 10	0011
4	0 110	0100
5	0 111	0101
6	0 101	0110
7	0 100	0111
8	1100	1000
9	1101	1001

Table 4.5 Gray Code representation of Decimal values

The bits in **bold** change in successive values of Gray code representation

Question # 1 of 5 (Start time: 10:34:45 AM, 05 July 2024)

Convert the binary number 1100 to Gray code.

Select the correct option

<input type="radio"/>	1010
<input checked="" type="radio"/>	1000
<input type="radio"/>	0111
<input type="radio"/>	0101

Question # 3 of 5 (Start time: 11:24:02 AM, 28 June 2024)

A decimal counter has _____ states.

Select the correct option

7

10

2

9

Question # 2 of 5 (Start time: 11:22:30 AM, 28 June 2024)

Why do we use Gray Code?

Select the correct option



Error Detection



Error Correction



To count the number of bit changes



Invert the code

Question # 1 of 5 (Start time: 11:21:58 AM, 28 June 2024)

Comparators are used in -----

Select the correct option

<input type="radio"/>	Memory
<input checked="" type="radio"/>	CPU
<input type="radio"/>	Motherboard
<input type="radio"/>	Hard Drive

Question # 8 of 10 (Start time: 11:56:58 PM, 03 July 2024)

A full adder circuit takes _____ bit(s) as input and returns _____ bit(s) as output.

Select the correct option



2, 1



3, 2



2, 2



3, 1

Question # 7 of 10 (Start time: 11:56:39 PM, 03 July 2024)

Which of the following is the modified code of Excess-3 code?

Select the correct option

<input checked="" type="radio"/>	Gray Code
<input type="radio"/>	ASCII
<input type="radio"/>	EBDIC
<input type="radio"/>	BCD

Question # 7 of 10 (Start time: 11:56:39 PM, 03 July 2024)

Which of the following is the modified code of Excess-3 code?

Select the correct option

<input checked="" type="radio"/>	Gray Code
<input type="radio"/>	ASCII
<input type="radio"/>	EBDIC
<input type="radio"/>	BCD

Question # 6 of 10 (Start time: 11:55:51 PM, 03 July 2024)

To create a Johnson Counter by using D-flip flops, how flip flops should be connected together?

Select the correct option



Q output of previous flip flop should be connected to D input of second flip flop



Q output of previous flip flop should be connected to clock input of second flip flop



Q' output of previous flip flop should be connected to D input of second flip flop



Q' output of previous flip flop should be connected to clock input of second flip flop

Question # 5 of 10 (Start time: 11:55:32 PM, 03 July 2024)

How many flop flops are required to create a counter circuit which can count from 0 to 7?

Select the correct option



2



4



1



3

Question # 4 of 10 (Start time: 11:55:08 PM, 03 July 2024)

Which of the following symbols is used to represent XOR operation?

Select the correct option

<input type="radio"/>	\wedge
<input type="radio"/>	\times
<input type="radio"/>	$+$
<input checked="" type="radio"/>	\oplus

Question # 1 of 10 (Start time: 11:53:57 PM, 03 July 2024)

The parallel outputs of a counter circuit represent the -----

Select the correct option

<input type="radio"/>	Clock frequency
<input type="radio"/>	Parallel data word
<input checked="" type="radio"/>	Clock count
<input type="radio"/>	Counter modulus

Question # 2 of 10 (Start time: 11:54:12 PM, 03 July 2024)

Ripple counters are also called -----

Select the correct option

<input type="radio"/>	SSI counters
<input type="radio"/>	Synchronous counters
<input type="radio"/>	VLSI counters
<input checked="" type="radio"/>	Asynchronous counters

Question # 8 of 10 (Start time: 11:56:58 PM, 03 July 2024)

A full adder circuit takes _____ bit(s) as input and returns _____ bit(s) as output.

Select the correct option

<input type="radio"/>	2,1
<input checked="" type="radio"/>	3,2
<input type="radio"/>	2,2
<input type="radio"/>	3,1

Question # 1 of 10 (Start time: 10:11:50 AM, 26 June 2024)

The K-map based Boolean reduction is based on the following Unifying Theorem: $A + A' = 1$.

Select the correct option

<input checked="" type="radio"/>	Non Impact
<input type="radio"/>	Impact
<input type="radio"/>	Complementarity 
<input type="radio"/>	Force

Question # 5 of 10 (Start time: 10:14:27 AM, 26 June 2024)

In order to build an XOR gate using NAND gates only, ----- gate(s) are required.

Select the correct option



4



2



3



1

Question # 4 of 10 (Start time: 10:14:12 AM, 26 June 2024)

There are _____ cells in a 4-variable K-map.

Select the correct option



24



16



8



20

Question # 3 of 10 (Start time: 10:13:51 AM, 26 June 2024)

A Karnaugh map (K-map) is an abstract form of _____ diagram organized as a matrix of squares.

Select the correct option



Triangular Diagram



Venn Diagram



Block diagram



Cycle Diagram

Question # 2 of 10 (Start time: 10:13:05 AM, 26 June 2024)

In a full adder circuit having inputs $A = 1$, $B = 1$, $C_{in} = 0$, the outputs S and C_{out} will be _____.

Select the correct option



$S = 1$, $C_{out} = 1$



$S = 0$, $C_{out} = 0$



$S = 1$, $C_{out} = 0$



$S = 0$, $C_{out} = 1$

Question # 8 of 10 (Start time: 10:15:59 AM, 26 June 2024)

In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the multiplexer?

Select the correct option

<input type="radio"/>	Y
<input type="radio"/>	W
<input checked="" type="radio"/>	G'
<input type="radio"/>	Vcc

Half-Adder Sum & Carry Out Boolean Expressions

The Sum and Carry Out expressions of the Half-Adder can be determined from the function table. The Half-Adder Sum and Carry Out outputs are defined by the expressions

$$\text{Sum} = \overline{A}B + A\overline{B} = A \oplus B$$

$$\text{CarryOut} = AB$$

Half-Adder Logic Circuit

The Half-Adder Logic Circuit can be directly implemented from the Sum and Carry Out Boolean expressions. Figure 14.6

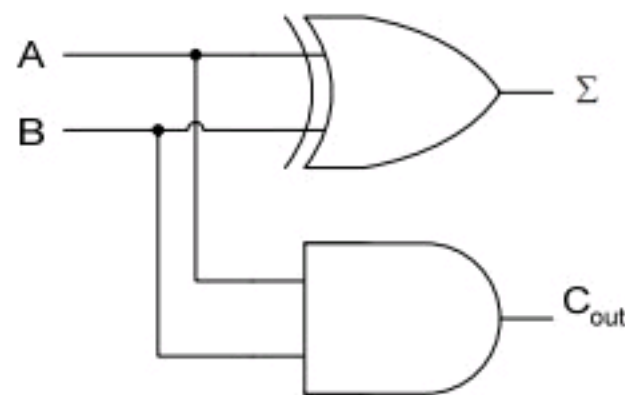


Figure 14.6 Half-Adder Logic Circuit

2. Full-Adder

A Full-Adder can be fully described in terms of its Function table, its Sum and Carry Out Boolean Expressions and the circuit Implementation.

Full-Adder Function Table

The Full-Adder has a 3-bit input and a 2-bit output. The function table of the Full-Adder

Question # 6 of 10 (Start time: 10:14:45 AM, 26 June 2024)

When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

Select the correct option

<input type="radio"/>	OR
<input checked="" type="radio"/>	XOR
<input type="radio"/>	NAND
<input type="radio"/>	AND

✓

Question # 9 of 10 (Start time: 10:16:58 AM, 26 June 2024)

When implementing a half adder by using gates, which of the following gates is used to give Sum (S) as an output?

Select the correct option

<input type="radio"/>	OR
<input type="radio"/>	AND
<input checked="" type="radio"/>	XOR
<input type="radio"/>	NOR

Question # 10 of 10 (Start time: 10:17:16 AM, 26 June 2024)

There are _____ cells in a 5-variable K-map.

Select the correct option

<input type="radio"/>	32	
<input type="radio"/>	24	
<input type="radio"/>	64	
<input type="radio"/>	16	

Question # 7 of 10 (Start time: 10:15:24 AM, 26 June 2024)

A half adder can be built by using the combination of _____ and _____ gates.

Select the correct option

<input type="radio"/>	AND, NOT
<input type="radio"/>	OR, XOR
<input checked="" type="radio"/>	AND, XOR
<input type="radio"/>	AND, OR

Question # 5 of 5 (Start time: 06:06:02 AM, 10 May 2024)

According to the distributive law of Boolean algebra, which of the following statements is **TRUE**?

Select the correct option



$$X + (Y Z) = X+Y+Z$$



$$X + (Y Z) = (X + Y) (X + Z)$$



$$X + (Y Z) = XYZ$$



$$X + (Y Z) = XY+XZ$$

Question # 1 of 5 (Start time: 06:01:57 AM, 10 May 2024)

According to De-Morgan's Law, the expression $(A+BC)'$ is equivalent to

Select the correct option

<input type="radio"/>	$A'B+BC$
<input checked="" type="radio"/>	$A'B'+A'C'$
<input type="radio"/>	$A'B+AC'$
<input type="radio"/>	$A' + B' + C'$

Question # 2 of 5 (Start time: 06:03:17 AM, 10 May 2024)

A commutative law of boolean algebra involves _____ boolean variable(s).

Select the correct option

<input type="radio"/>	4
<input type="radio"/>	1
<input type="radio"/>	3
<input checked="" type="radio"/>	2

Question # 5 of 5 (Start time: 09:26:08 AM, 17 May 2024)

A Karnaugh map (K-map) is an abstract form of _____ diagram organized as a matrix of squares.

Select the correct option



Triangular Diagram



Cycle Diagram



Block diagram



Venn Diagram

Question # 4 of 5 (Start time: 09:24:54 AM, 17 May 2024)

Which of the following is not a valid number for grouping of terms in K-Map?

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | 1 |
| <input checked="" type="radio"/> | 3 |
| <input type="radio"/> | 4 |
| <input type="radio"/> | 2 |

Question # 3 of 5 (Start time: 09:24:05 AM, 17 May 2024)

A K-Map of size 2x2 can be used to map a _____ input boolean expression.

Select the correct option

<input checked="" type="radio"/>	2
<input type="radio"/>	1
<input type="radio"/>	3
<input type="radio"/>	4

Question # 2 of 5 (Start time: 09:23:26 AM, 17 May 2024)

----- is known as a universal gate.

Select the correct option



OR



XNOR



NAND



AND

Question # 1 of 5 (Start time: 09:22:44 AM, 17 May 2024)

----- gates are economical and easier to fabricate and are the basic gates used in all IC digital logic families.

Select the correct option

<input type="radio"/>	Inverse
<input type="radio"/>	Boolean
<input checked="" type="radio"/>	Universal
<input type="radio"/>	Logic

Question # 5 of 5 (Start time: 03:41:35 PM, 14 June 2024)

When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

Select the correct option

<input type="radio"/>	OR
<input type="radio"/>	NAND
<input checked="" type="radio"/>	AND
<input type="radio"/>	XOR

Question # 4 of 5 (Start time: 03:40:45 PM, 14 June 2024)

Which of the following symbols is used to represent XOR operation?

Select the correct option

 \wedge  \oplus 

+



x

Question # 3 of 5 (Start time: 03:39:13 PM, 14 June 2024)

Which of the following gates is used for parity generation for a binary data string?

Select the correct option

<input type="radio"/>	NOR
<input type="radio"/>	AND
<input type="radio"/>	OR
<input checked="" type="radio"/>	XOR

Question # 2 of 5 (Start time: 03:38:08 PM, 14 June 2024)

In a full adder circuit having inputs $A = 1$, $B = 1$, $C_{in} = 0$, the outputs S and C_{out} will be

Select the correct option



$S = 1$, $C_{out} = 0$



$S = 1$, $C_{out} = 1$



$S = 0$, $C_{out} = 1$



$S = 0$, $C_{out} = 0$

Question # 1 of 5 (Start time: 03:37:18 PM, 14 June 2024)

How many select lines would be required for an 8x1 multiplexer?

Select the correct option



2



1



8



3



Question # 5 of 5 (Start time: 09:39:24 AM, 24 May 2024)

It should be kept in mind that don't care terms should be used along with the terms that are present in -----.



Select the correct option

<input type="radio"/>	K-Map
<input type="radio"/>	Latches
<input checked="" type="radio"/>	Minterms
<input type="radio"/>	Expressions

Question # 4 of 5 (Start time: 09:38:34 AM, 24 May 2024)

To build a full adder using gates, how many gates are required?

Select the correct option

- | | |
|----------------------------------|--------------------------------------|
| <input type="radio"/> | 2 AND gates, 3 OR gates, 1 XOR gates |
| <input type="radio"/> | 2 AND gates, 2 OR gates, 2 XOR gates |
| <input checked="" type="radio"/> | 2 AND gates, 2 XOR gates, 1 OR gate |
| <input type="radio"/> | 1 AND gate, 2 OR gates, 1 XOR gate |

Question # 3 of 5 (Start time: 09:38:14 AM, 24 May 2024)

Each product term of a group, wxy' and wy , represents the _____ in that group.

Select the correct option

<input type="radio"/>	Input
<input type="radio"/>	Sum of Maxterms
<input type="radio"/>	POS
<input checked="" type="radio"/>	Sum of Minterms

Question # 2 of 5 (Start time: 09:37:46 AM, 24 May 2024)

Which of the following gates is used for parity generation for a binary data string?

Select the correct option

<input checked="" type="radio"/>	XOR
<input type="radio"/>	AND
<input type="radio"/>	NOR
<input type="radio"/>	OR

Question # 1 of 5 (Start time: 09:37:11 AM, 24 May 2024)

A Karnaugh map (K-map) is an abstract form of _____ diagram organized as a matrix of squares.

Select the correct option

- | | |
|----------------------------------|--------------------|
| <input type="radio"/> | Cycle Diagram |
| <input checked="" type="radio"/> | Venn Diagram |
| <input type="radio"/> | Block diagram |
| <input type="radio"/> | Triangular Diagram |

Question # 1 of 10 (Start time: 10:03:12 AM, 07 May 2024)


We can change the number of inputs for a gate by using -----.

Select the correct option

<input type="radio"/>	Gate Structure
<input type="radio"/>	Truth Table
<input type="radio"/>	Gate Diagram
<input checked="" type="radio"/>	Gate Properties

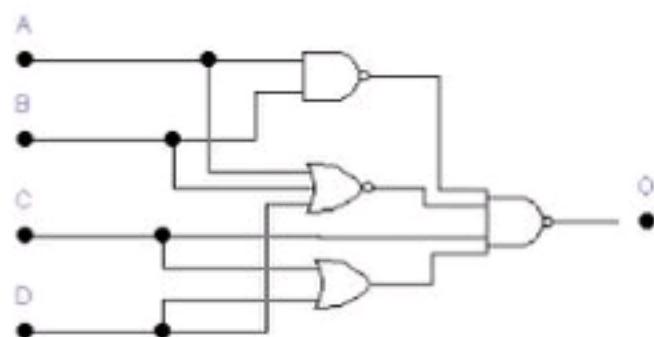Question # 10 of 10 (Start time: 10:12:16 AM, 07 May 2024)

What will be the simplified Boolean Expression of the stated Gate Level Diagram.



Select the correct option



$$A + B + C' + D$$



$$A + B' + C' + D$$




$$A' + B' + C' + D$$

Question # 4 of 10 (Start time: 10:05:35 AM, 07 May 2024)


Which version of Electronics Workbench is being used in this course for creating and simulating digital circuits?

Select the correct option

- | | |
|-----------------------|--|
| <input type="radio"/> | version 6 |
| <input type="radio"/> | version 10 |
| <input type="radio"/> | version 12.5 |
| <input type="radio"/> | version 5.12  |

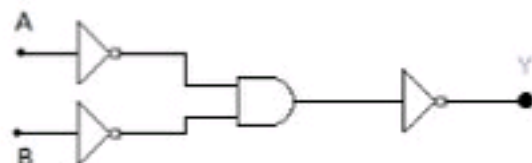Question # 1 of 5 (Start time: 08:13:57 PM, 26 April 2024)

What will be the Boolean Equation for (Y) for the given Gate Level Diagram.



Select the correct option

$A'B'$

$A'B$

$A + B$

$A' + B$



Question # 2 of 5 (Start time: 08:15:05 PM, 26 April 2024)

In Electronics Workbench, the default value for the frequency of the clock source is

Select the correct option


- | | |
|----------------------------------|-------|
| <input type="radio"/> | 2 Hz |
| <input type="radio"/> | 5 Hz |
| <input type="radio"/> | 2 KHz |
| <input checked="" type="radio"/> | 50 Hz |
- 

Question # 3 of 5 (Start time: 08:15:58 PM, 26 April 2024)

----- is used to generate a square wave/pulse.

Select the correct option

<input type="radio"/>	Time Interval
<input checked="" type="radio"/>	NAND Gate
<input type="radio"/>	Clock
<input type="radio"/>	Frequency



Question # 10 of 10 (Start time: 10:11:22 AM, 29 August 2022)

Total Marks: 1

How many select lines would be required for an 8:1 multiplexer?



Select the correct option

- | | | | |
|----------------------------------|---|--|--|
| <input checked="" type="radio"/> | 3 | | www.thundershare.net |
| <input type="radio"/> | 2 | | |
| <input type="radio"/> | 1 | | |
| <input type="radio"/> | 8 | | |

Question # 1 of 5 (Start time: 09:22:44 AM, 17 May 2024)

----- gates are economical and easier to fabricate and are the basic gates used in all IC digital logic families.

Select the correct option

<input type="radio"/>	Inverse
<input type="radio"/>	Boolean
<input checked="" type="radio"/>	Universal
<input type="radio"/>	Logic

Question # 2 of 5 (Start time: 09:23:26 AM, 17 May 2024)

----- is known as a universal gate.

Select the correct option

<input type="radio"/>	OR
<input type="radio"/>	XNOR
<input checked="" type="radio"/>	NAND
<input type="radio"/>	AND

Question # 4 of 5 (Start time: 09:24:54 AM, 17 May 2024)

Which of the following is not a valid number for grouping of terms in K-Map?

Select the correct option



1



3



4



2

Question # 5 of 5 (Start time: 09:26:08 AM, 17 May 2024)

A Karnaugh map (K-map) is an abstract form of _____ diagram organized as a matrix of squares.

Select the correct option

- | | |
|-----------------------|--------------------|
| <input type="radio"/> | Triangular Diagram |
| <input type="radio"/> | Cycle Diagram |
| <input type="radio"/> | Block diagram |
| <input type="radio"/> | Venn Diagram |

Question # 2 of 10 (**Start time: 07:28:06 AM, 05 June 2023**)

_____ is also known as a Universal gate.

Select the correct option



OR

www.thundershare.net



XNOR



NOR



AND

Question # 3 of 10 (Start time: 07:28:41 AM, 05 June 2023)

There are _____ cells in a 5-variable K-map.

Select the correct option



24

www.thundershare.net

32



16



64

Question # 4 of 10 (Start time: 07:29:17 AM, 05 June 2023)

The K-map based Boolean reduction is based on the following Unifying Theorem: $A + A' = 1$.

Select the correct option

Impact

www.thundershare.net

Force

Complementarity

Non Impact

Question # 5 of 10 (Start time: 07:31:14 AM, 05 June 2023)

----- is known as a universal gate.

Select the correct option



NAND

www.thundershare.net



XNOR



OR



AND

Question # 6 of 10 (Start time: 07:31:44 AM, 05 June 2023)

It should be kept in mind that don't care terms should be used along with the terms that are present in _____.

Select the correct option

<input checked="" type="radio"/>	Minterms	www.thundershare.net
<input type="radio"/>	K-Map	
<input type="radio"/>	Latches	
<input type="radio"/>	Expressions	

Question # 7 of 10 (Start time: 07:32:45 AM, 05 June 2023)

Consider a 3-variable Karnaugh Map. How many groups of 1's can be made from the below given Karnaugh Map?

A/BC	00	01	11	10
0	0	1	1	0
1	1	1	1	1

www.thundershare.net

& Cell = $(2)^3 = 8$

Select the correct option



1

Question # 8 of 10 (Start time: 07:33:52 AM, 05 June 2023)

Don't care conditions can be used for simplifying Boolean expressions in _____.

Select the correct option

<input type="radio"/>	Registers	www.thundershare.net
<input checked="" type="radio"/>	K-maps	
<input type="radio"/>	Terms	
<input type="radio"/>	Latches	

Question # 9 of 10 (Start time: 07:34:59 AM, 05 June 2023)

There are _____ cells in a 4-variable K-map.

Select the correct option



20

www.thundershare.net



8



16

$(2)^4$



24

Question # 10 of 10 (**Start time: 07:35:31 AM, 05 June 2023**)

----- gate with a bubble at the output is know as NAND gate.

Select the correct option

www.thundershare.net



NOR



OR



NOT



AND

Question # 5 of 5 (Start time: 03:51:53 PM, 03 May 2024)

A commutative law of boolean algebra involves _____ boolean variable(s).

Select the correct option

- | | |
|----------------------------------|---|
| <input type="radio"/> | 3 |
| <input checked="" type="radio"/> | 2 |
| <input type="radio"/> | 1 |
| <input type="radio"/> | 4 |

Cin is part of _____ Adder.

Select the correct option


Full



Single

Half

Double

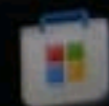

Question # 1 of 5 (Start time: 06:01:57 AM, 10 May 2024)

According to De-Morgan's Law, the expression $(A+BC)'$ is equivalent to _____.

Select the correct option

<input type="radio"/>	$A'B+BC$
<input type="radio"/>	$A'B'+A'C'$
<input checked="" type="radio"/>	$A'B+AC'$
<input type="radio"/>	$A' + B' + C'$

Figure 14.5 Block diagrams of Half-Adder and Full-Adder

Half-Adder Function Table

The Half-Adder has a 2-bit input and a 2-bit output. The function table of the Half-Adder has two input columns representing the two single bit numbers A and B. The function table also has two output columns representing the Sum bit and Carry Out bit. Table 14.3

Input		Output	
A	B	Sum	Carry Out
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Table 14.3 Half-Adder Function Table

Question # 2 of 15 (Start time: 02:56:23 PM, 30 January 2023)

Total Marks: 1

Total number of inputs in a half adder is _____

Select the correct option

 Reload Math Equations

3



2



1



4

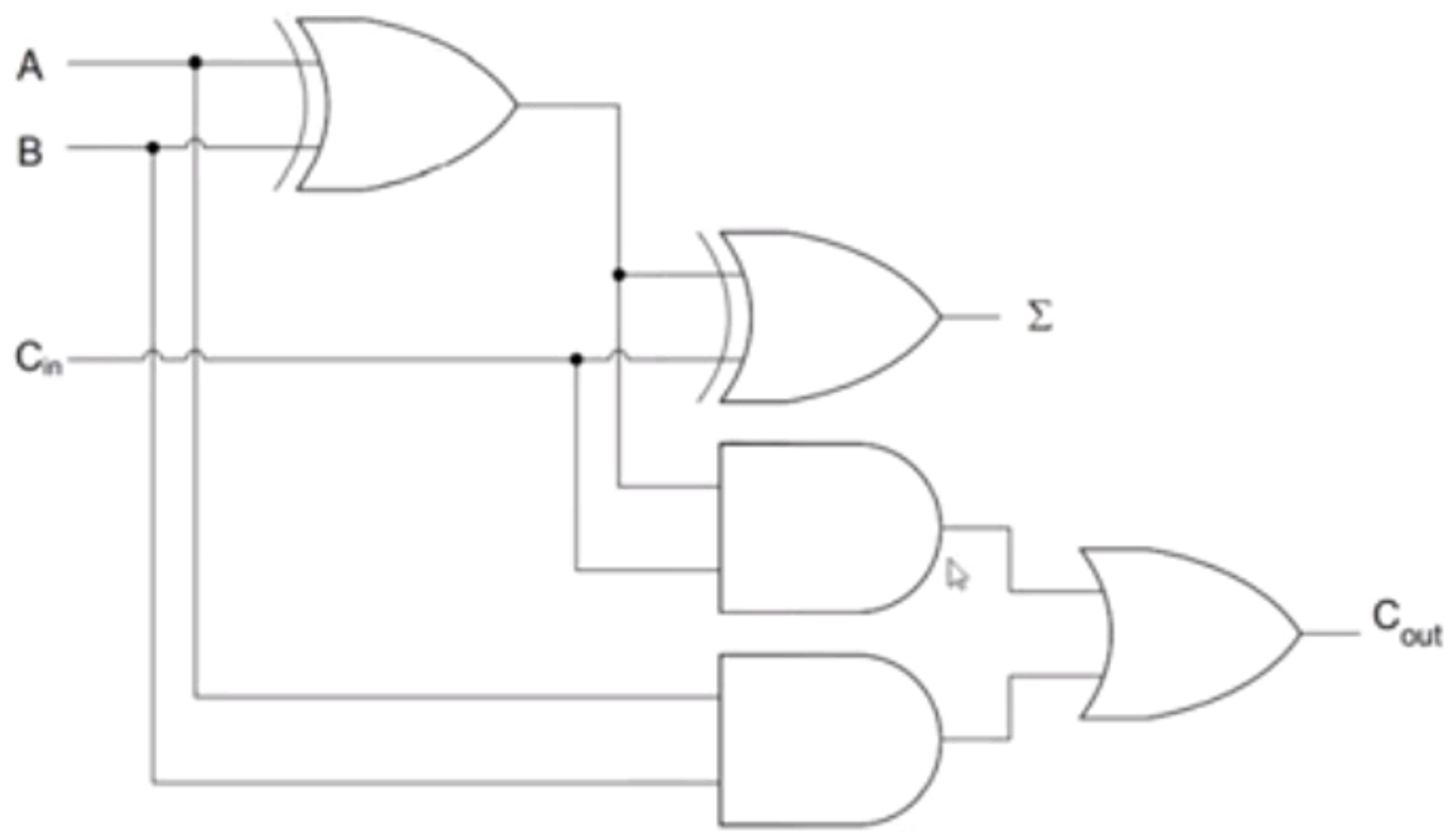


Figure 14.7 Full-Adder Logic Circuit

Question # 3 of 15 (Start time: 02:57:02 PM, 30 January 2023)

Total Marks: 1

To build a full adder using gates, how many gates are required?

Select the correct option

[Reload Math Equations](#)

1 AND gate, 2 OR gates, 1 XOR gate



2 AND gates, 3 OR gates, 1 XOR gates



2 AND gates, 2 OR gates, 2 XOR gates



2 AND gates, 2 XOR gates, 1 OR gate



Question # 4 of 15 (Start time: 02:57:58 PM, 30 January 2023)

Total Marks: 1

Which of the following symbols is used to represent XOR operation?

Select the correct option

[Reload Math Equations](#)

+

 \oplus 

^



x

10 states

اردو میں

In English

Explanation: Decimal counter is also known as 10 stage counter. So, it has **10 states**. It is also known as Decade Counter counting from 0 to 9.

<https://www.sanfoundry.com> › digital-circuits-questions-a... ⋮

Digital Circuits Questions and Answers – Counters - Sanfoundry



About featured snippets



Feedback

People also ask ⋮

Question # 6 of 15 (Start time: 03:00:16 PM, 30 January 2023)

Total Marks: 1

A decimal counter has _____ states.

Select the correct option

[Reload Math Equations](#)

7



9



10

4



2

[Click to Save Answer & Move to Next Question](#)

rotate right operations. When data is rotated through a register counter a specific sequence of states is repeated. Two commonly used register counters in digital logic are the Johnson Counter and the Ring Counter.

1. Johnson Counter

In a Johnson counter, the \bar{Q} output of the last flip-flop of the shift register is connected to the data input of the first flip-flop. The circuit of a 4-bit, D flip-flop based Johnson Counter is shown in figure 34.16. The sequence of states that are implemented by a n-bit Johnson counter are $2n$. Thus a 4-bit Johnson counter sequences through 8 states and a 5-bit Johnson counter sequences through 10 states. Table 34.1

Question # 7 of 15 (Start time: 03:01:23 PM, 30 January 2023)

Total Marks: 1

To create a Johnson Counter by using D-flip flops, how flip flops should be connected together?

Select the correct option

[Reload Math Equations](#)

- Q output of previous flip flop should be connected to D input of second flip flop
- Q output of previous flip flop should be connected to clock input of second flip flop
- Q' output of previous flip flop should be connected to clock input of second flip flop
- Q' output of previous flip flop should be connected to D input of second flip flop

[Click to Save Answer & Move to Next Question](#)

اردو میں

In English

Explanation: The maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops is **0 to 2^n-1** . For say, there is a 2-bit counter, then it will count till $2^2-1 = 3$. Thus, it will count from 0 to 3.

<https://www.sanfoundry.com> › [digital-circuits-questions-a...](#) ⋮

Digital Circuits Questions and Answers – Counters - Sanfoundry



About featured snippets



Feedback

Question # 9 of 15 (Start time: 03:02:57 PM, 30 January 2023)

Total Marks: 1

What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

Select the correct option

[Reload Math Equations](#)0 to 2^{n+1} 0 to $2^n - 1$ 0 to 2^n 0 to $2^n + 1$

Question # 8 of 15 (Start time: 03:01:50 PM, 30 January 2023)

Total Marks: 1

Which of the following gates is used for parity generation for a binary data string?

Select the correct option

[Reload Math Equations](#)

OR



XOR



AND



NOR

[Click to Save Answer & Move to Next Question](#)

the clock count

اردو میں

In English

Explanation: The parallel outputs of a counter circuit represent **the clock count**. A counter counts number of times an event takes place in accordance to the clock pulse.

<https://www.sanfoundry.com> › [digital-circuits-questions-a...](#)

Digital Circuits Questions and Answers – Counters - Sanfoundry

[?](#) About featured snippets • [!](#)

Question # 10 of 15 (Start time: 03:07:26 PM, 30 January 2023)

Total Marks: 1

The parallel outputs of a counter circuit represent the

Select the correct option

[Reload Math Equations](#)

Parallel data word



Counter modulus



Clock frequency



Clock count



How many flip-flops are required to design a mod 7 counter?

3 flip flops are required to design a mod-7 counter.

[https://www.quora.com/How-many-flip-flops-will-be-re...](https://www.quora.com/How-many-flip-flops-will-be-required-to-design-a-MOD-7-counter)

How many flip flops will be required to design a MOD

Quora

Search for: How many flip-flops are required to design a mod 7 co

Question # 11 of 15 (Start time: 03:09:09 PM, 30 January 2023)

Total Marks: |

How many flop flops are required to create a counter circuit which can count from 0 to 7?

Select the correct option

[Reload Math Equations](#) 4 3 1 2

Inputs			Outputs	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Question # 12 of 15 (Start time: 03:13:42 PM, 30 January 2023)

Total Marks: 1

In a full adder circuit having inputs $A = 1$, $B = 1$, $C_{in} = 0$, the outputs S and C_{out} will be

Select the correct option

[Reload Math Equations](#) $S = 0, C_{out} = 1$  $S = 1, C_{out} = 0$  $S = 0, C_{out} = 0$  $S = 1, C_{out} = 1$ [Click to Save Answer & Move to Next Question](#)

About 1,010,000 results (0.55 seconds)

اردو میں

In English

The half adder can be built from an **XOR gate and an AND gate**. In a multi-bit adder, C_{out} is added or carried in to the next most significant bit.

<https://www.sciencedirect.com> › topics › computer-science

Half Adder - an overview | ScienceDirect Topics



About featured snippets



Feedb

Question # 13 of 15 (Start time: 03:15:42 PM, 30 January 2023)

Total Marks: |

A half adder can be built by using the combination of and gates.

Select the correct option

[Reload Math Equations](#) AND, XOR OR, XOR AND, NOT AND, OR

Question # 14 of 15 (Start time: 03:17:13 PM, 30 January 2023)

Total Marks: 1

A counter circuit is usually constructed of -----

Select the correct option

[Reload Math Equations](#) A number of NOR gates connected in cascade form A number of NAND gates connected in cascade form A number of latches connected in cascade form A number of flip-flops connected in cascade[Click to Save Answer & Move to Next Question](#)

اردو میں

In English

A full adder can be viewed as a **3:2** lossy compressor: **it sums three one-bit inputs and returns the result as a single two-bit number**; that is, it maps 8 input values to 4 output values. Thus, for example, a binary input of 101 results in an output of $1 + 0 + 1 = 10$ (decimal number 2).

<https://encyclopedia.pub> › entry

Binary Adder - Scholarly Community Encyclopedia



About featured snippets



Feedback

Question # 5 of 15 (Start time: 02:58:42 PM, 30 January 2023)

Total Marks: 1

A full adder circuit takes _____ bit(s) as input and returns _____ bit(s) as output.

Select the correct option

[Reload Math Equations](#)

2, 1



3, 2



2, 2



3, 1

A decimal counter has _____ states.

Select the correct option



7



2



10



9

TTL 74LS85 is a _____

Select the correct option



8-bit magnitude comparator



4-bit magnitude comparator




8-bit word comparator



1-bit digital comparator

2. A counter circuit is usually constructed of _____

- a) A number of latches connected in cascade form
- b) A number of NAND gates connected in cascade form
- c) A number of flip-flops connected in cascade
- d) A number of NOR gates connected in cascade form

 View Answer

Answer: c

About 163,000,000 results (0.48 seconds)

اردو میں

In English

Explanation: Three decade counter has **30 states** and a BCD counter has 10 states. So would require **3 BCD counters**. Thus, a three decade counter will count from 0 to 29.


<https://www.sanfoundry.com> > digital-circuits-questions-a... ⋮

Digital Circuits Questions and Answers – Counters - Sanfoundry

ⓘ About featured snippets • 🗨️ Feedback

Three decade counter would have _____

Select the correct option

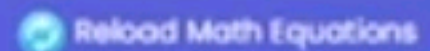 Reload Math Equations



5 BCD counters



4 BCD counters



3 BCD counters



2 BCD counters

4



Click to Save Answer & Move to Next Question

Question # 5 of 10 (Start time: 02:06:38 PM, 18 July 2023)


Which of the following gates is used for parity generation for a binary data string?

Select the correct option

<input checked="" type="radio"/>	XOR
<input type="radio"/>	AND
<input type="radio"/>	NOR
<input type="radio"/>	OR

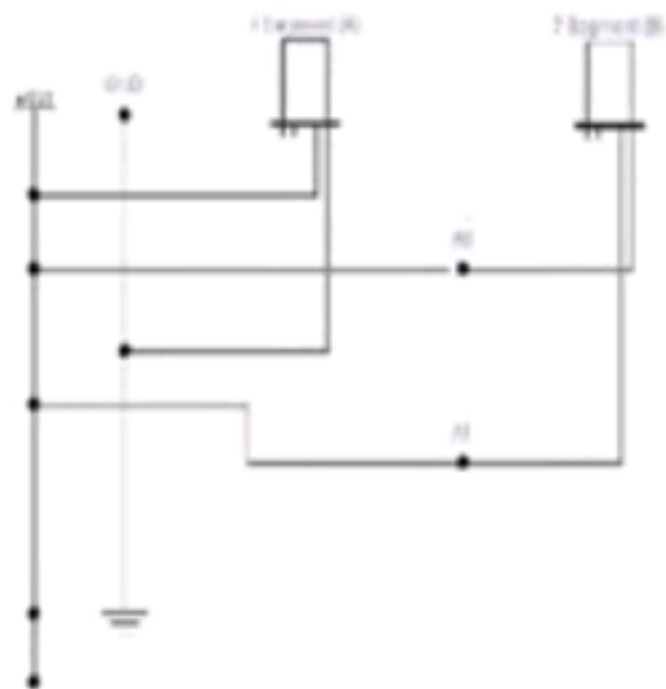Question # 7 of 10 (Start time: 02:08:10 PM, 18 July 2023)

Consider the below given EWB circuit, what values will be displayed on 7-segment displays A and B when the circuit simulation is activated in EWB?



213

Select the correct option

Question # 5 of 10 (Start time: 10:02:25 AM, 29 August 2022)

Total Marks: 1

In order to build an XOR gate using NAND gates only, gate(s) are required.

Select the correct option



- | | | |
|----------------------------------|---|--|
| <input type="radio"/> | 2 | www.thundershare.net |
| <input type="radio"/> | 1 | |
| <input checked="" type="radio"/> | 4 | |
| <input type="radio"/> | 3 | |



APPLICATIONS OF SHIFT REGISTERS

The major application of a shift register is to convert between parallel and serial data. Shift registers are also used as keyboard encoders. The two applications of the shift registers are discussed.

1. Serial-to-Parallel Converter

Earlier, Multiplexer and Demultiplexer based Parallel to Serial and Serial to Parallel converters were discussed. The Multiplexer and Demultiplexer require registers to store the parallel data that is converted into serial data and parallel data which is obtained after converting the incoming serial data. A Parallel In/Serial Out shift register offers a better solution instead of using a Multiplexer-Register combination to convert parallel data into serial data. Similarly, a Serial In/Parallel Out shift register replaces a Demultiplexer-Register combination.

In Asynchronous S...
bits (which can includ...
to indicate when d...
is being transmit...
character. A cha...
high when a ch...

ter which is constitute... of 8-...
acter from anot... and...
n line is idle (data...
ends of the 8-bit...
le it is set logic...
to logic lo... the

imp topic

Integrated Circuit Up/Down Decade Counter Quiz

Implementing a 4-bit Up/Down counter by connecting flip-flops and logic gate increases the circuit size and requires many connections. The 74HC190 is a 4-bit Up/Down Synchronous Counter available in an Integrated Circuit form. Figure 29.3. (The counter has the following pins. Quiz + Short

1. Parallel data inputs D_0, D_1, D_2 and D_3
2. Data outputs Q_0, Q_1, Q_2 and Q_3
3. Positive edge-triggered CLOCK signal
4. Active-low LOAD input which loads the 4-bit data applied at the counter inputs
5. Active-low CTEN counter enable input
6. D/\bar{U} the count down/up input. When the input is set to logic 1, the counter counts down and when the input is set to logic 0, the counter counts up
7. The MAX/MIN output that is set to high when the terminal count 1001 is reached when counting up or when the terminal count 0000 is reached when counting down. The MAX/MIN output is logic high for one complete cycle when a terminal count is reached.
8. The Ripple Clock Output RCO goes low when the Counter reaches the terminal count 1001 or 0000 when counting up or down respectively. (The RCO output remains low during the negative half of the clock cycle. The RCO, the MAX/MIN output along with CTEN input are used to cascade multiple counter ICs for implementing larger counters.)

Inputs D_0 D_1 D_2 D_3