

# Cs302

## Final Term Diagrams and Important Points

Presented by  Moon-Knight 

### Circuit Diagram of OLMC


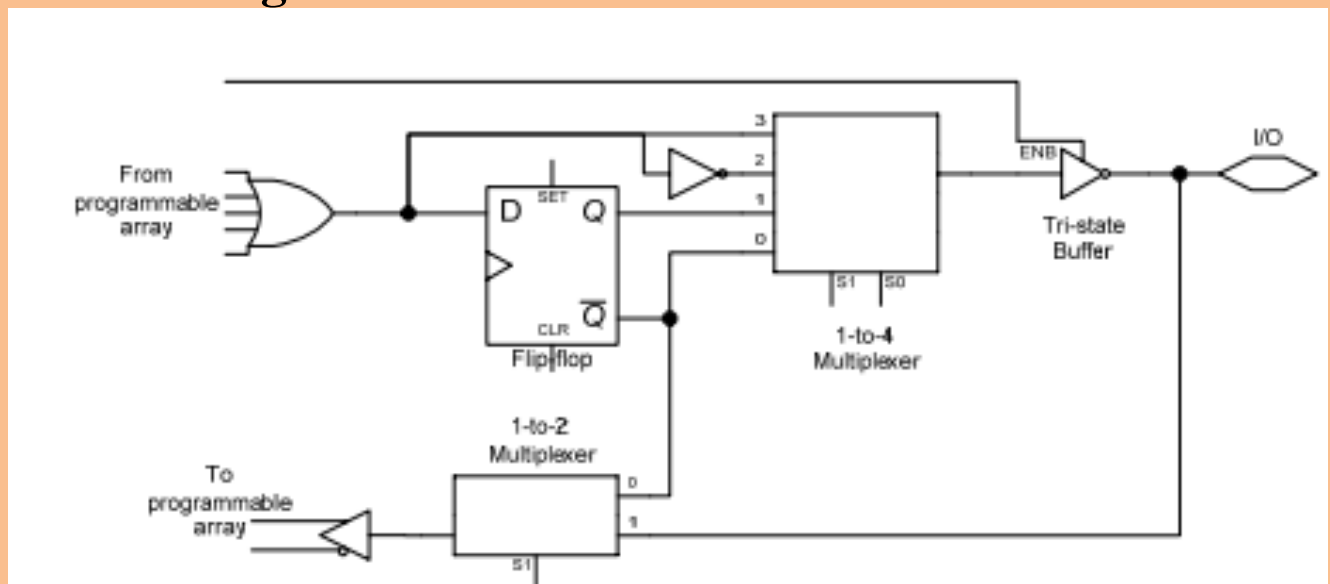


Figure 20.8 Circuit Diagram of OLMC

The four OLMC configurations are

- Combination Mode with active-low output
- Combinational Mode with active-high output
- Registered Mode with active-low output
- Registered Mode with active-high output
 
### Tri-State Buffer in High-Impedance State




## **Tri-state Buffer and OLMC output pin**

The tri-state buffer connecting the output of the OLMC circuit to the output pin is controlled through four different sources. The tri-state buffer control input can be connected in four different ways.

1. Connected to Vcc. The output is always enabled.
2. Connected to GND. The output is disabled and the output pin is configured as an input pin.
3. Connected to the external pin (11) which can be connected to Vcc or GND. The tri-state buffer is therefore controlled externally by applying an appropriate signal at the pin.
4. Connected to the output of one of the eight AND gates connected to the OLMC. Thus the tri-state buffer is controlled by a logical expression.
 
## **The tri-state buffer Combinational Input/Output**



## **ABEL**

ABEL provides three different text-based methods for describing and entering a logic design. The three methods are

- Boolean Equations
- Truth Tables
- State Diagrams


### **ABEL Symbols for logic operations**

Logic Operation	ABEL Symbol
NOT	!
AND	&
OR	#
XOR	\$

### **Boolean and equivalent ABEL Notations**

Boolean Notation	ABEL Notation
A	!A
.BA	A&B
+ BA	A#B
$\oplus$ BA	A\$B

 
### **The NAND gate based S-R (Set-Reset) Latch**



### Truth-Table of NAND based S-R Latch

Input		Output
S	R	$Q_{t+1}$
0	0	invalid
0	1	1
1	0	0
1	1	$Q_t$

 
### The NOR gate based S-R (Set-Reset) Latch




### Truth-Table of NOR based S-R Latch

Input output		
S	R	$Q_{t+1}$
0	0	$Q_t$
0	1	0
1	0	1
1	1	invalid

 
## NOR based Active-High and NAND based Active-Low S-R Latches



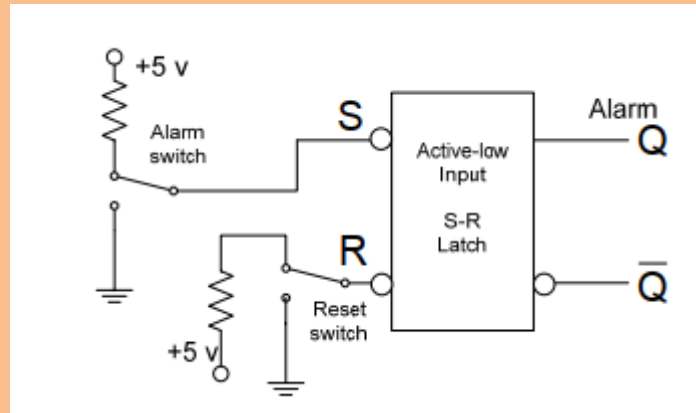
The switch connected through an S-R latch



 **The circuit diagram of the gated S-R latch**



**Logic Symbol of a Gated S-R Latch**

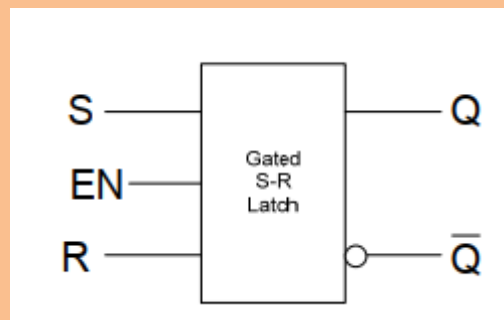


**Truth-Table of a gated S-R Latch**

input		output	
EN	S	R	$Q_{t+1}$

0	x	x	$Q_t$
1	0	0	$Q_t$
1	0	1	0
1	1	0	1
1	1	1	invalid


## The Gated D Latch

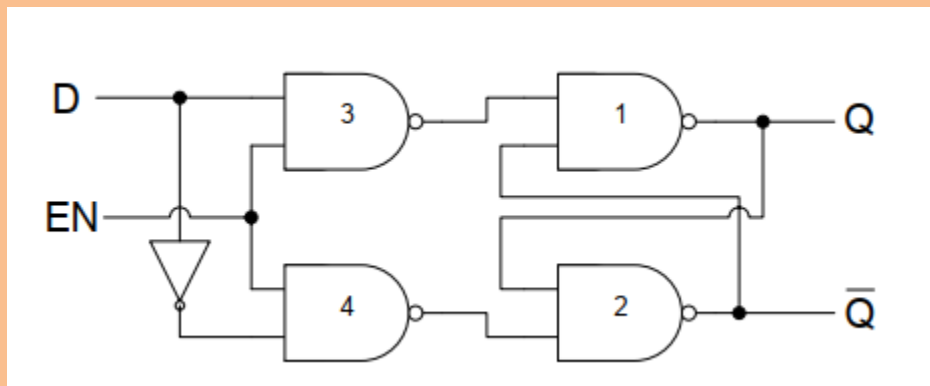


## Truth-Table of a gated D Latch

Input		Output
EN	D	$Q_{t+1}$
0	x	$Q_t$
1	0	0
1	1	1

## Logic Symbol of a Gated D Latch

 

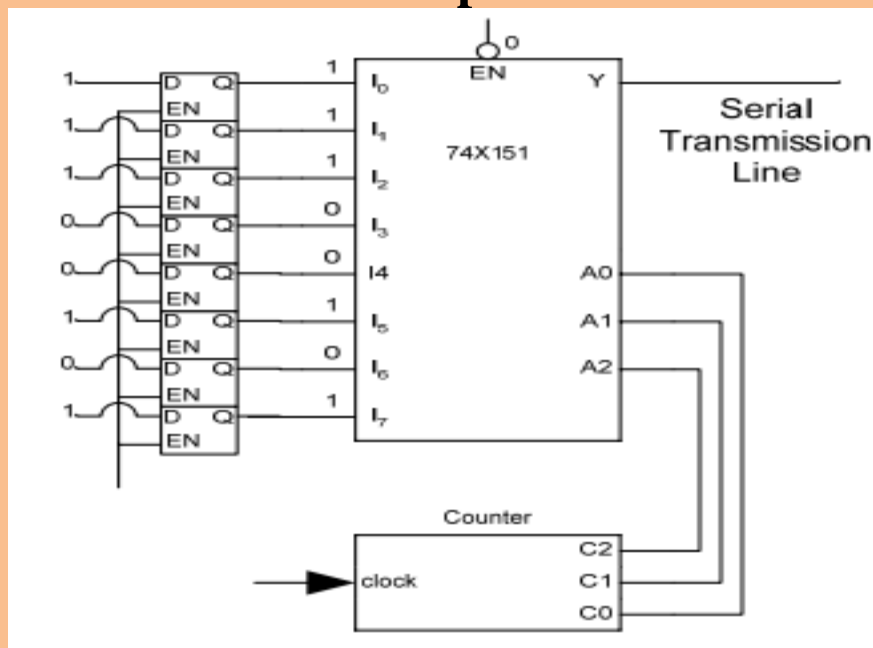
## Gated D-latch used to store parallel data



Three different types of edge-triggered flip-flops are generally used in digital logic circuits.

- S-R edge-triggered flip-flop
- D edge-triggered flip-flop
- J-K edge-triggered flip-flop
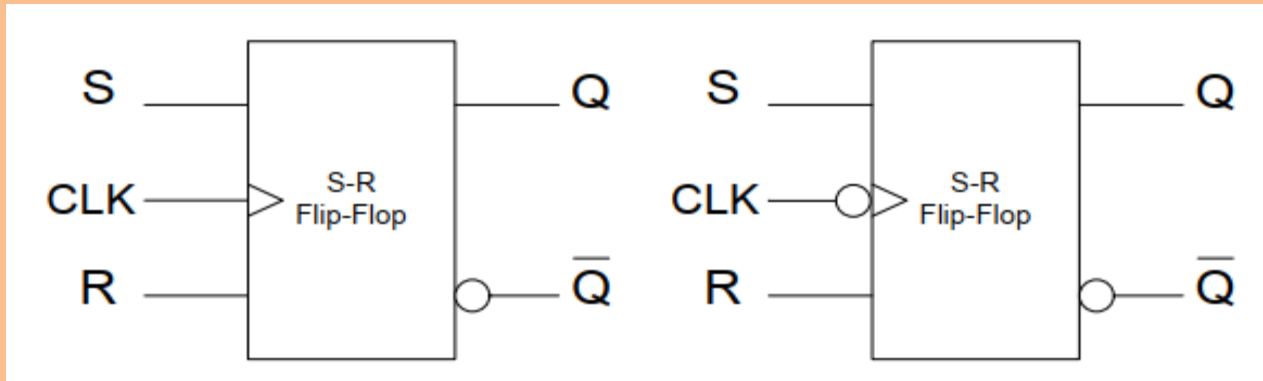
## Logic Symbol of Positive and Negative edge triggered S-R flip-flops




## Truth-Table of Positive and Negative Edge triggered S-R flip-flops

Input			Output
CLK	S	R	$Q_{t+1}$
0	X	X	$Q_t$
1	X	X	$Q_t$
$\uparrow$	0	0	$Q_t$
$\uparrow$	0	1	0
$\uparrow$	1	0	1
$\uparrow$	1	1	invalid

Input			Output
CLK	S	R	$Q_{t+1}$
0	x	x	$Q_t$
1	x	x	$Q_t$
$\downarrow$	0	0	$Q_t$
$\downarrow$	0	1	0
$\downarrow$	1	0	1
$\downarrow$	1	1	invalid
 
## Logic Symbol of Positive and Negative edge triggered D flip-flops




## Truth-Table of Positive and Negative Edge triggered D flip-flops

Input		Output
CLK	D	$Q_{t+1}$
0	X	$Q_t$
1	X	$Q_t$
↑	0	0
↑	1	1

Input		Output
CLK	D	$Q_{t+1}$
0	X	$Q_t$
1	X	$Q_t$
↓	0	0
↓	1	1

## Edge-Triggered J-K Flip-flop

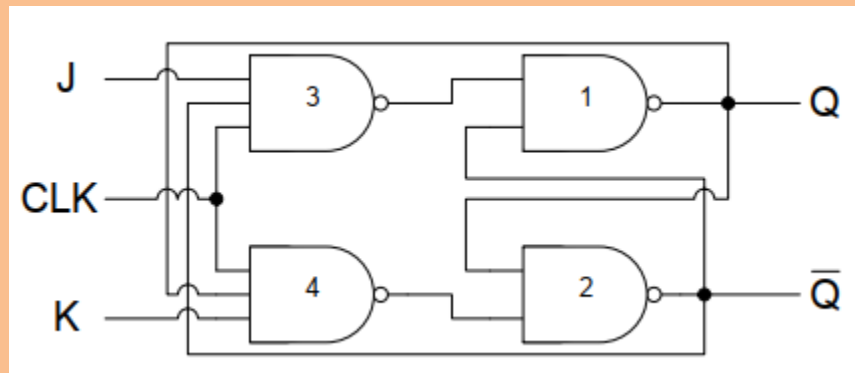


## Truth-Table of Positive and Negative Edge triggered J-K flip-flops


Input			Output
CLK	J	K	$Q_{t+1}$
0	x	X	$Q_t$
1	x	X	$Q_t$
↑	0	0	$Q_t$
↑	0	1	0
↑	1	0	1
↑	1	1	$\bar{Q}_t$

Input			Output
CLK	J	K	$Q_{t+1}$
0	x	x	$Q_t$
1	x	x	$Q_t$
↓	0	0	$Q_t$
↓	0	1	0
↓	1	0	1
↓	1	1	$\bar{Q}_t$

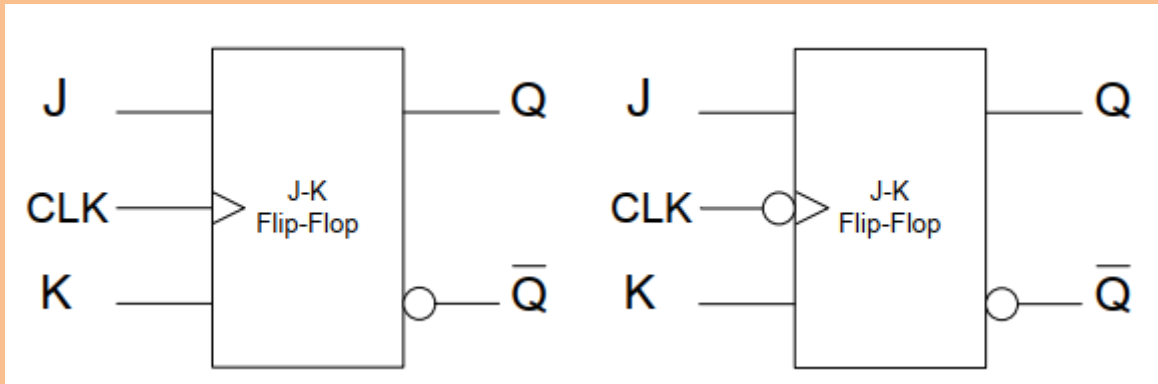
## Logic Symbol of Positive and Negative edge triggered J-K flip-flops



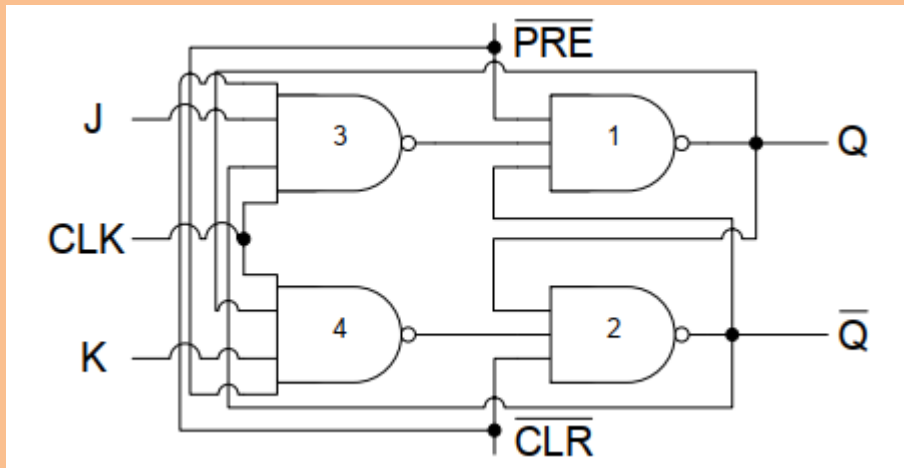**J-K flip-flop with Asynchronous Preset and Clear inputs**



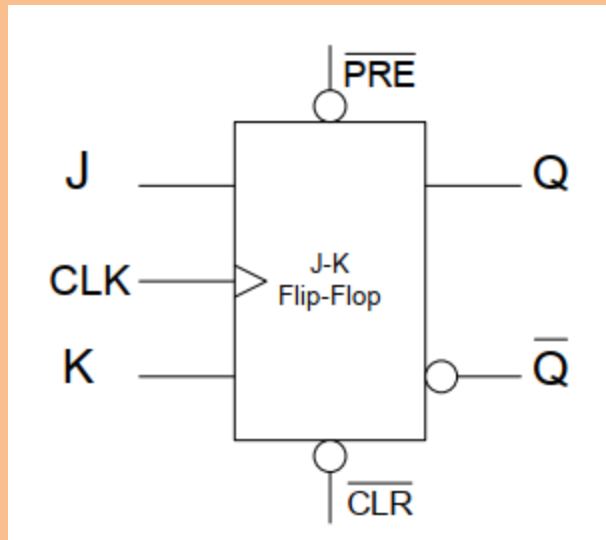
**Logic Symbol of a J-K flip-flop with Asynchronous inputs**



### Truth table of J-K flip-flop with Asynchronous inputs

Input		Output
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	$Q_{t+1}$
0	0	Invalid
0	1	1
1	0	0
1	1	Clocked operation

### Master-Slave flip-flop

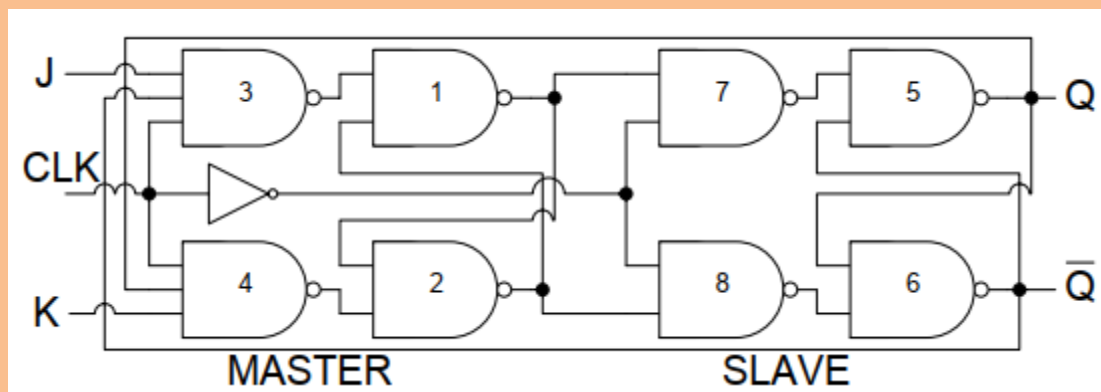


### Truth table of the Master-Slave J-K flip-flop

Input			Output
CLK	J	K	$Q_{t+1}$
Pulse	0	0	$Q_t$
Pulse	0	1	0
Pulse	1	0	1
Pulse	1	1	$\overline{Q}_t$


## Flip-Flop Operating Characteristics

- Propagation Delay
- Set-up Time
- Hold Time
- Maximum Clock frequency
- Pulse width
- Power Dissipation

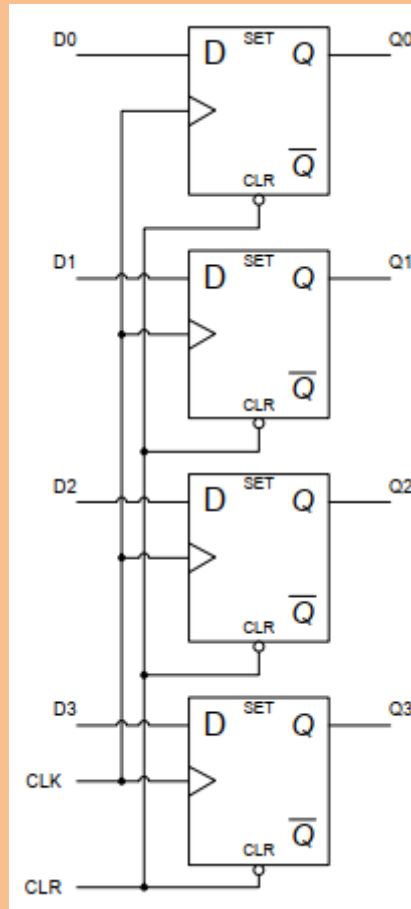
**D-flip-flops used for Parallel Data Storage**



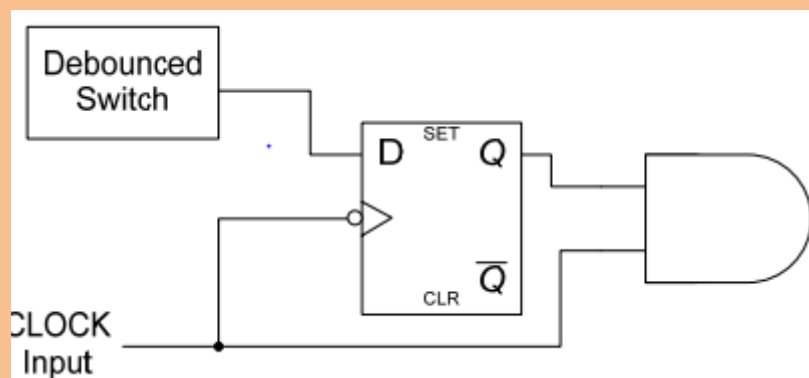
## D flip-flop used to synchronize the AND Gate output



## Edge-triggered J-K flip-flop

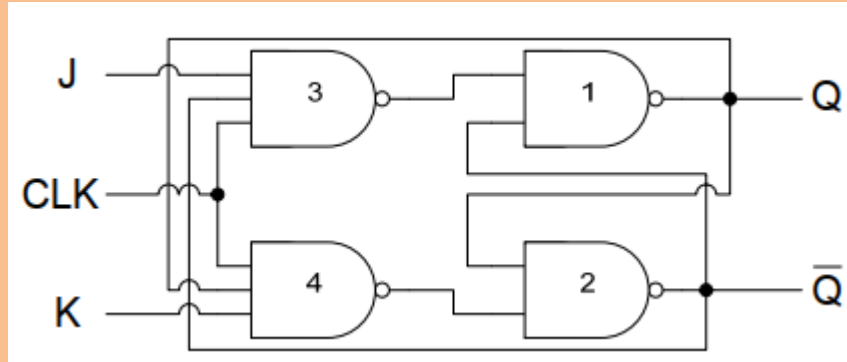
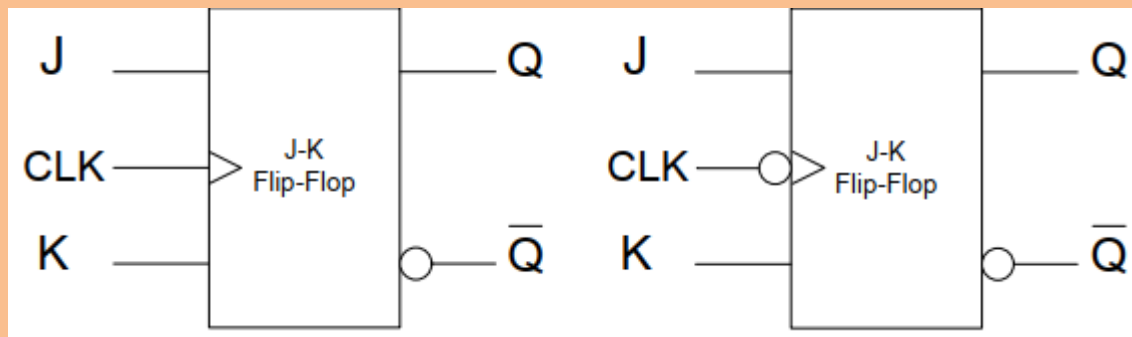
## Logic Symbol of Positive and Negative edge triggered J-K flip-flops




## Truth-Table of Positive and Negative Edge triggered J-K flip-flop


Input			Output
CLK	J	K	$Q_{t+1}$
0	x	X	$Q_t$
1	x	X	$Q_t$
↑	0	0	$Q_t$
↑	0	1	0
↑	1	0	1
↑	1	1	$\bar{Q}_t$

Input			Output
CLK	J	K	$Q_{t+1}$
0	x	x	$Q_t$
1	x	x	$Q_t$
↓	0	0	$Q_t$
↓	0	1	0
↓	1	0	1
↓	1	1	$\bar{Q}_t$

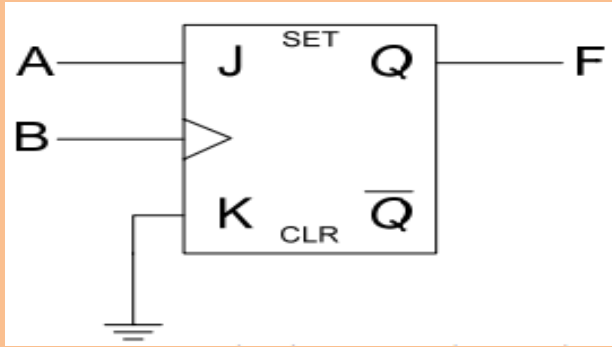
## J-K flip-flop used as sequence detector



 
### J-K flip-flop used as frequency divider



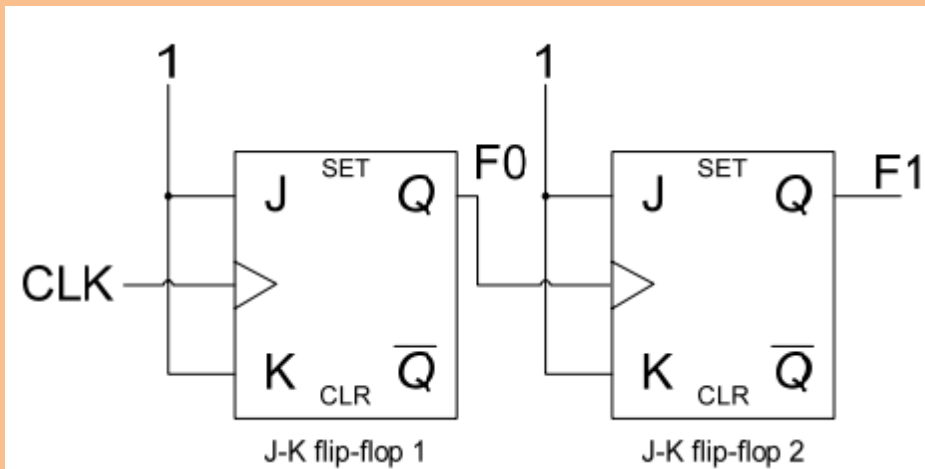
### J-K flip-flop connected as divide-by-4 frequency divider



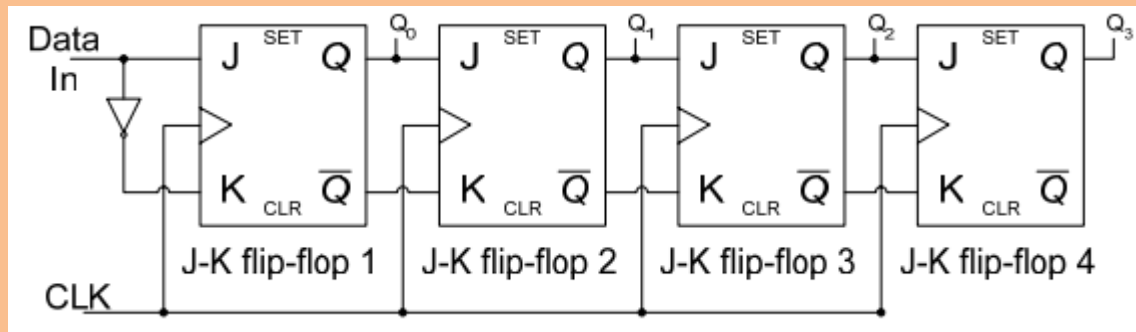
### J-K flip-flop used as a shift register




## J-K flip-flop used as a up counter

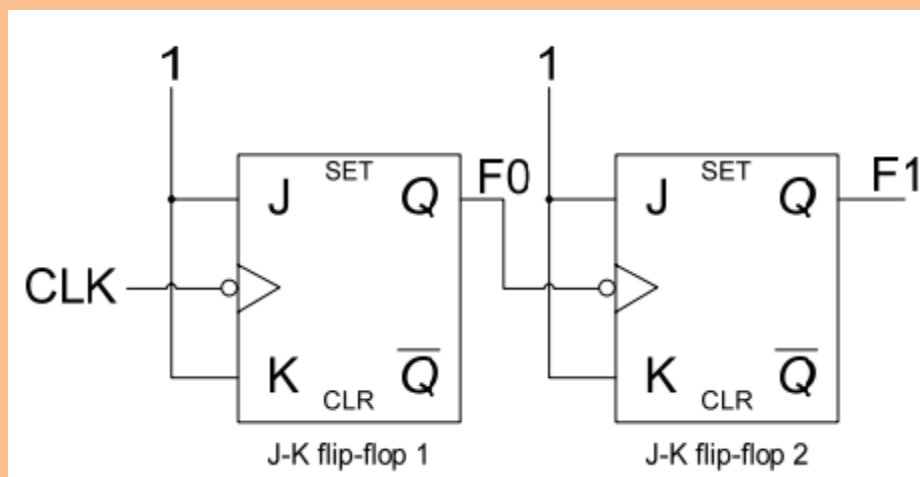

## ASYNCHRONOUS PRESET AND CLEAR INPUTS

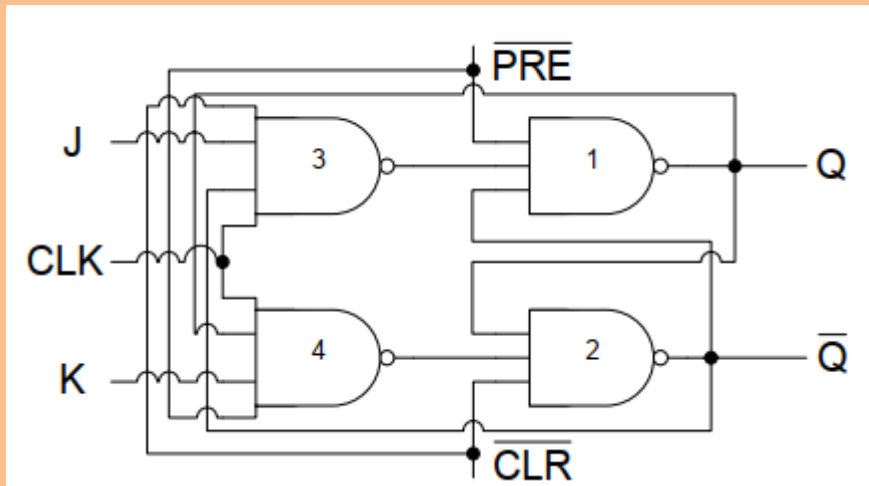

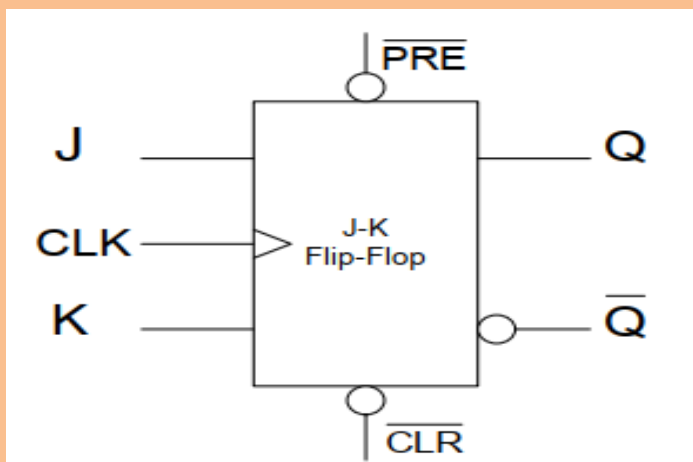
## Logic Symbol of a J-K flip-flop with Asynchronous inputs




## Truth table of J-K flip-flop with Asynchronous inputs

Input		Output
$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	$Q_{t+1}$
0	0	Invalid
0	1	1
1	0	0
1	1	Clocked operation

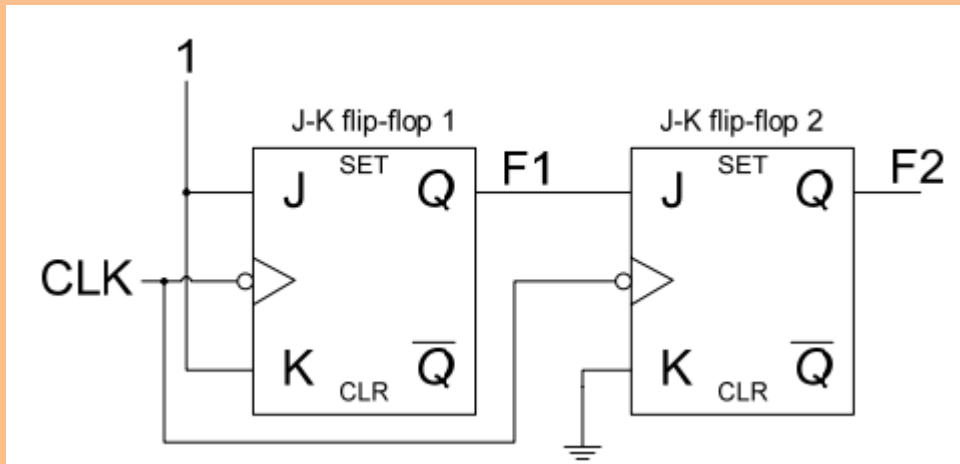
## J-K flip-flop circuit with potential timing problem


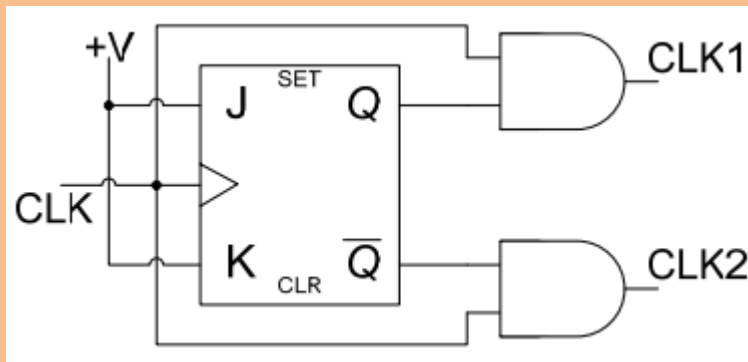
## J-K flip-flop circuit with potential race condition




## 3-bit Asynchronous Up-Counter

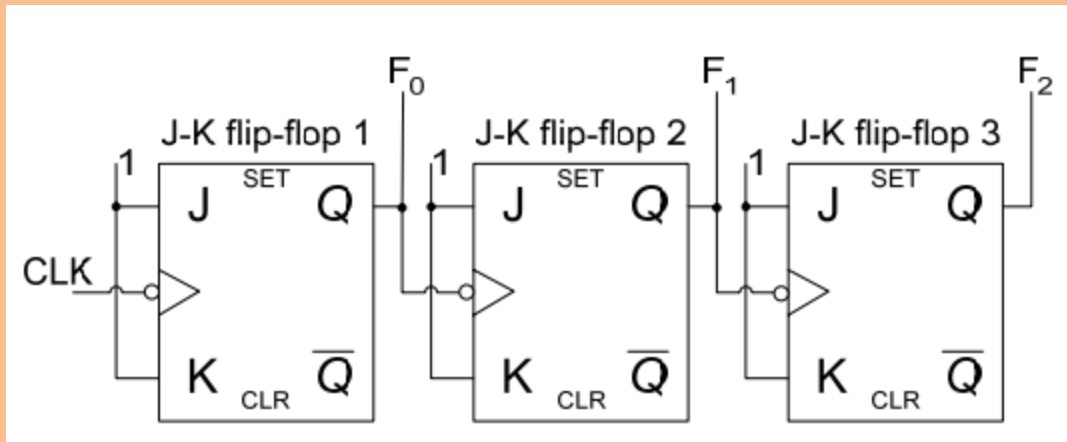


## Output State of a 3-bit Asynchronous Up-Counter

Input Clock Pulses	Output		
	F <sub>2</sub>	F <sub>1</sub>	F <sub>0</sub>
1	0	0	0
2	0	0	1
3	0	1	0
4	0	1	1
5	1	0	0
6	1	0	1
7	1	1	0
8	1	1	1


## Mod-n Counters\ Mod-6 Counter

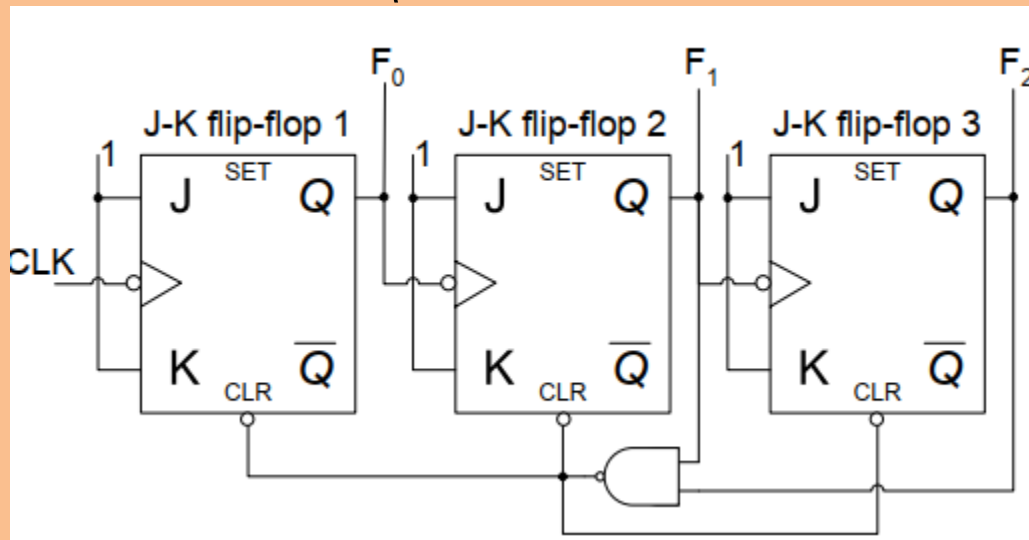

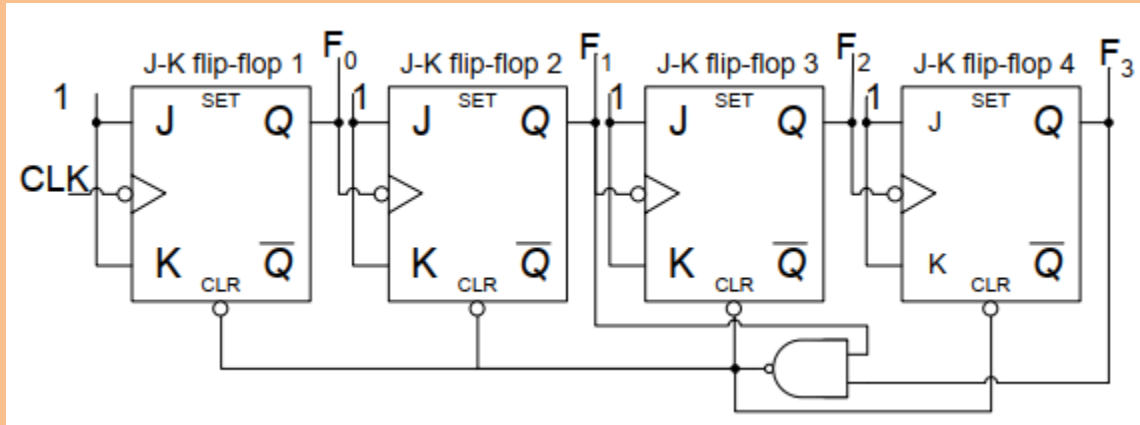
## Mod-10 Counter (Decade Counter)\ Asynchronous Decade Counter



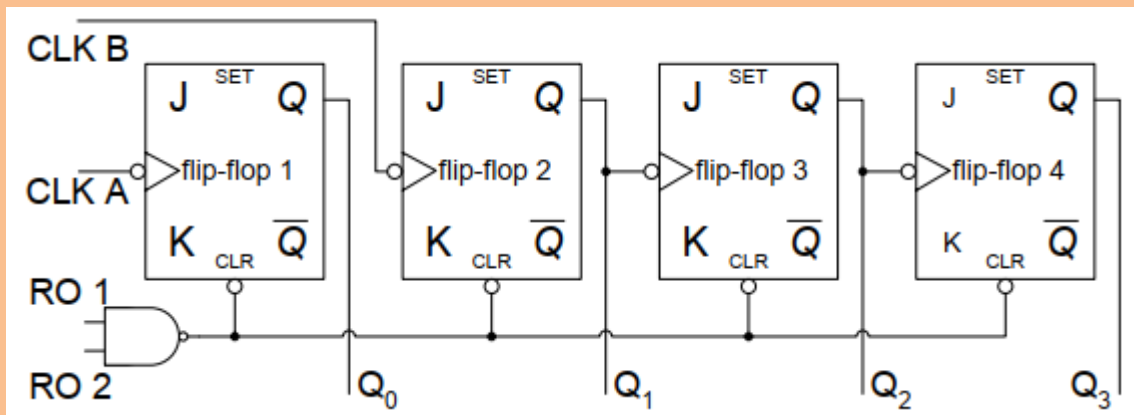
Internal circuit diagram of the 74LS93A Counter




74LS93A connected as MOD-16 Counter

 


**74LS93A connected as Decade Counter**

 

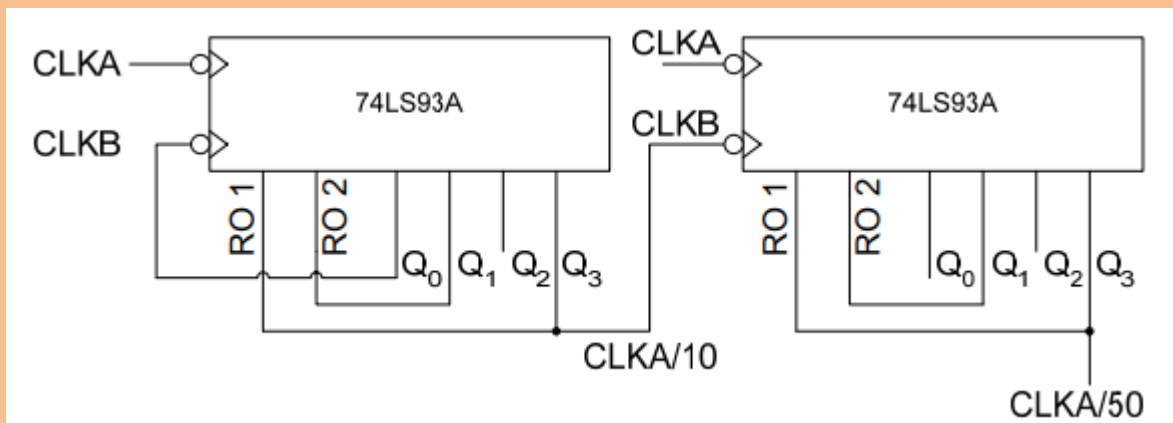
**74LS93A Connected as a frequency divider (divide by 50)**




**3-bit Asynchronous Down-Counter**

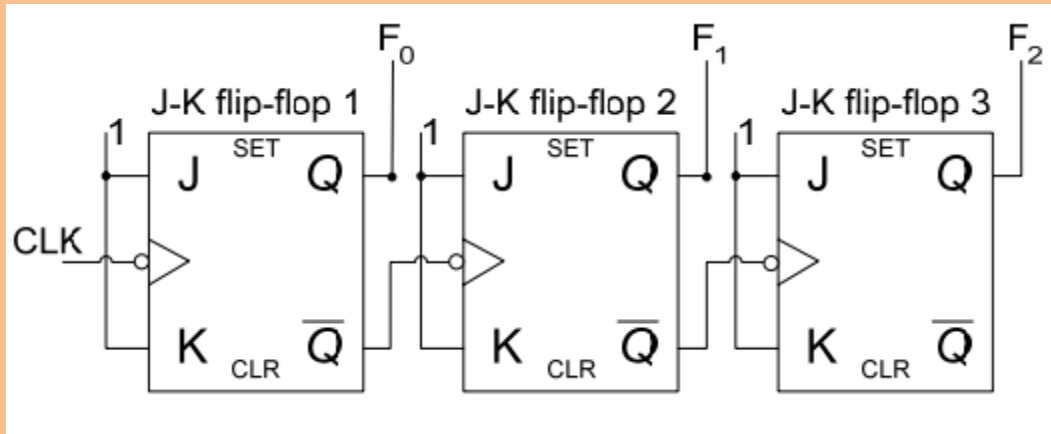

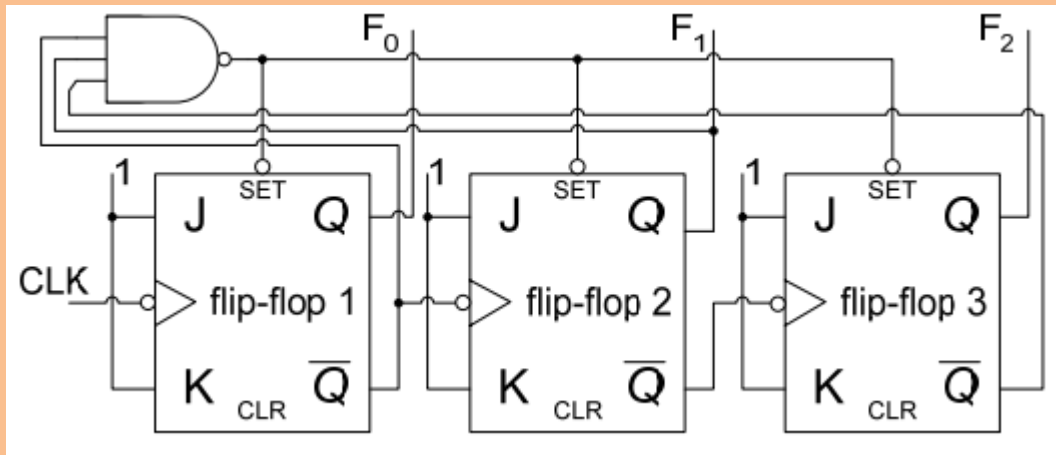
**Down Counter with truncated sequence** \ Down-counter configured to count a truncated sequence




**2-bit Synchronous Counter**

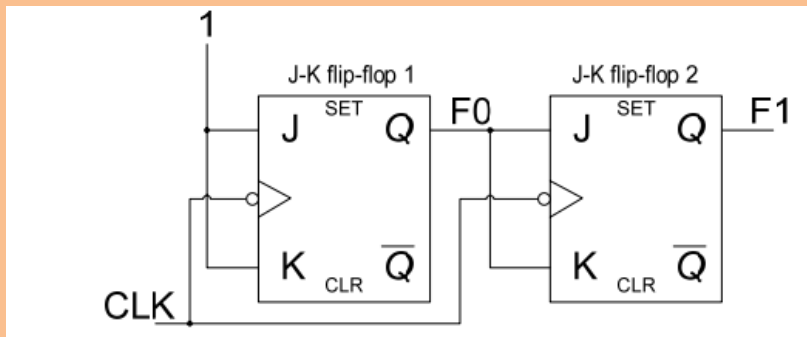

## A 3-bit Synchronous Counter

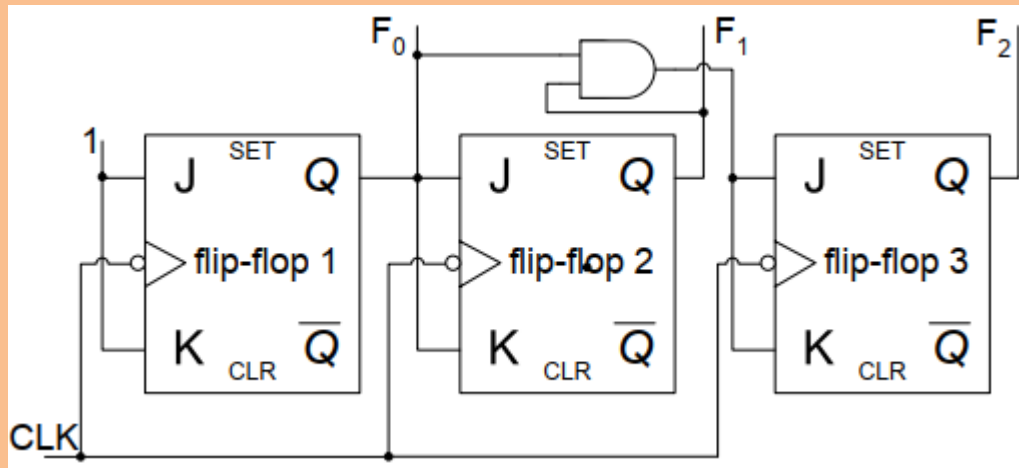


## 4-bit Synchronous Binary Counter

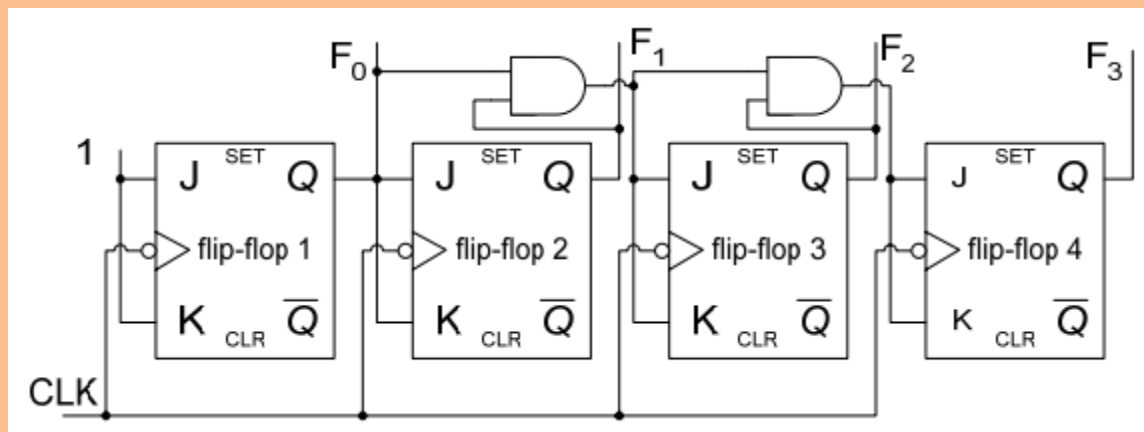

## Output of a Synchronous Decade Counter

Input Clock Pulses	Output			
	F <sub>3</sub>	F <sub>2</sub>	F <sub>1</sub>	F <sub>0</sub>
1	0	0	0	0
2	0	0	0	1
3	0	0	1	0
4	0	0	1	1
5	0	1	0	0
6	0	1	0	1
7	0	1	1	0
8	0	1	1	1
9	1	0	0	0
10	1	0	0	1

## Synchronous Decade Counter

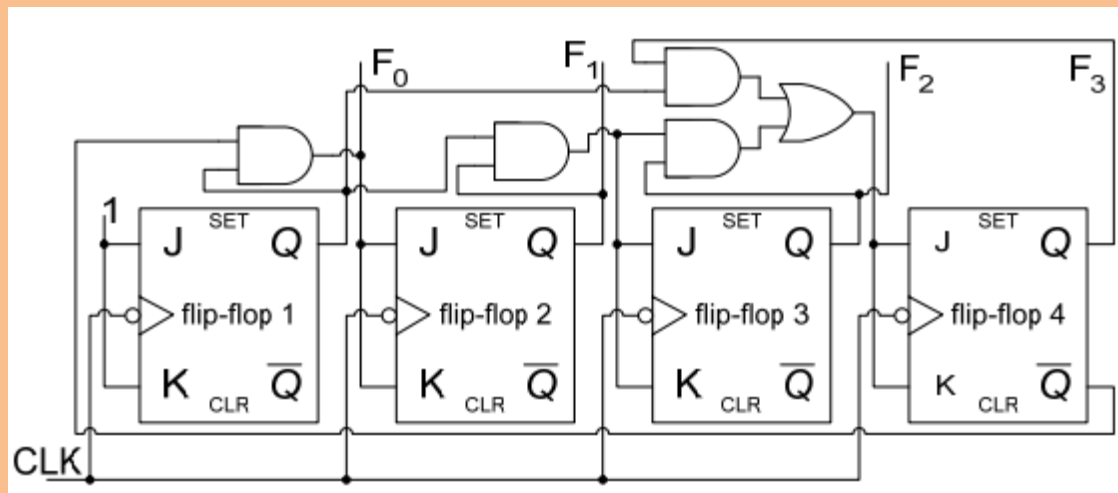


**The 74HC163 is a 4-bit Synchronous Counter. Figure 28.2. The counter has the following pins.**


1. Parallel data inputs D0, D1, D2 and D3
2. Data outputs Q0, Q1, Q2 and Q3
3. Positive edge-triggered CLOCK signal
4. Active-low CLR input which resets the Counter output to 0000

5. Active-low LOAD input which loads the 4-bit data applied at the counter inputs
6. Active-high ENT and ENP enable inputs. For the counter to operate both the enable inputs have to be high
7. The Ripple Clock Output RCO goes high when the Counter reaches the terminal count 1111. The RCO output along with ENT and ENP enable input pins are used to cascade multiple counter ICs for implementing larger counters

 
### **74HC163 4-bit Synchronous Counter**




### **Cascaded Decade Counters**

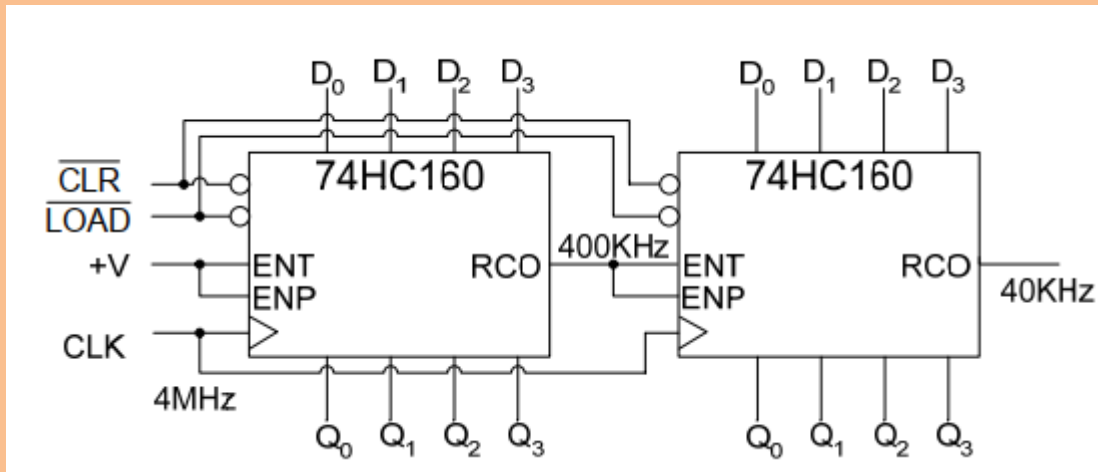

 
## Integrated Circuit Counters with Truncated Sequences\ 74HC163 configured as Mod-7 counter



## 74HC161 configured as Mod-9 counter

 

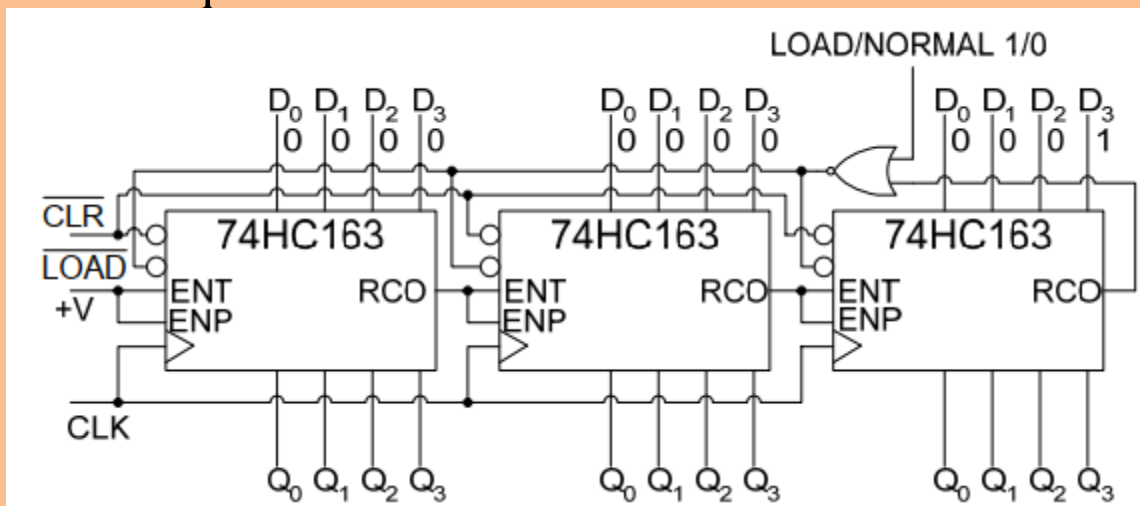
## 74HC163 counters connected for cascaded truncated count sequence




## Up-counting sequence of a 3-bit Synchronous Counter

Clock Pulse	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1




 

 
## 74HC190 4-bit Synchronous Up/Down Counter



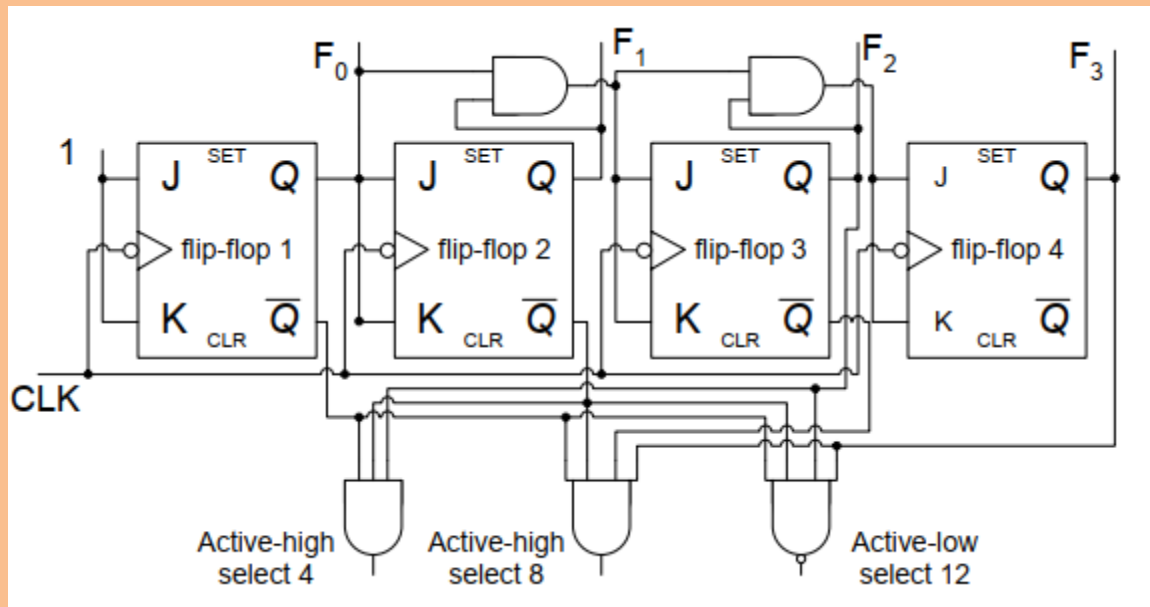
Decoder circuit decoding counter outputs 4, 8 and 12



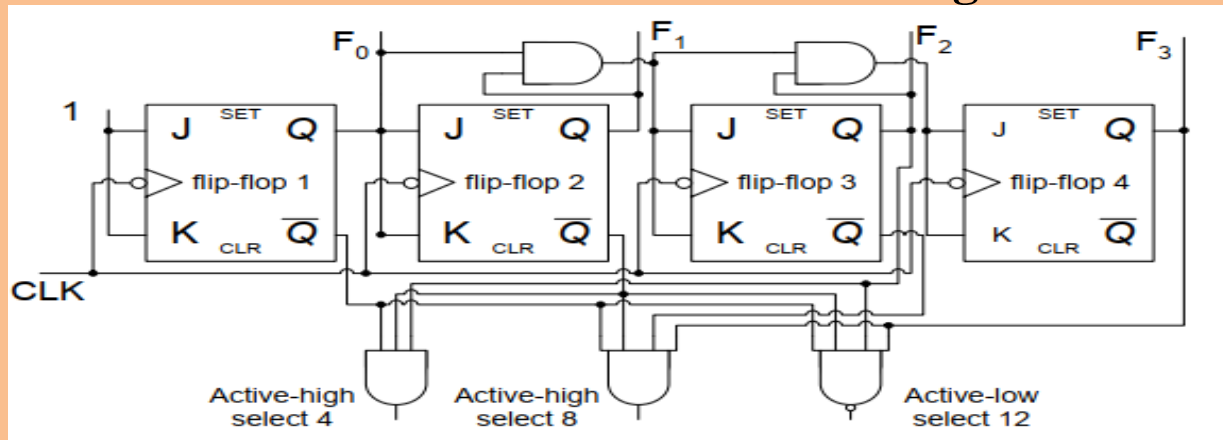
**The Decoder circuit connected to remove glitches**



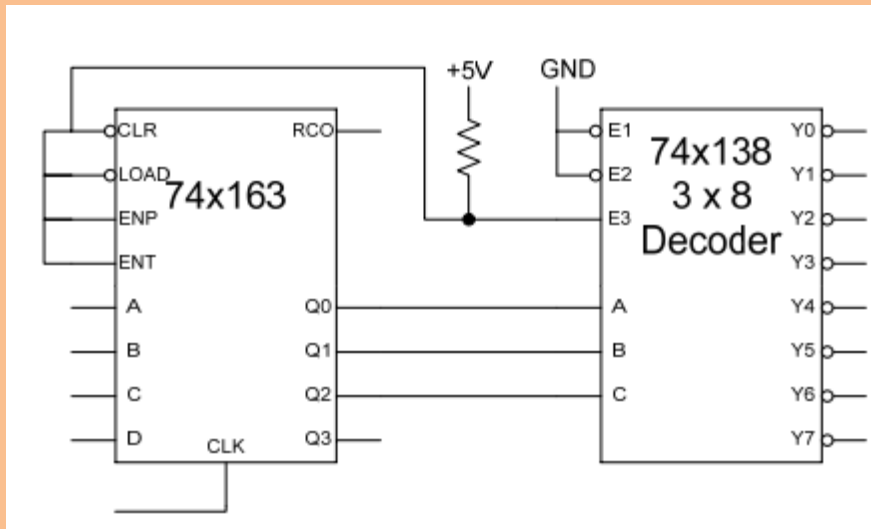
**74x163 Counter output Decoded using a 3 x 8, 74x138 Decoder**



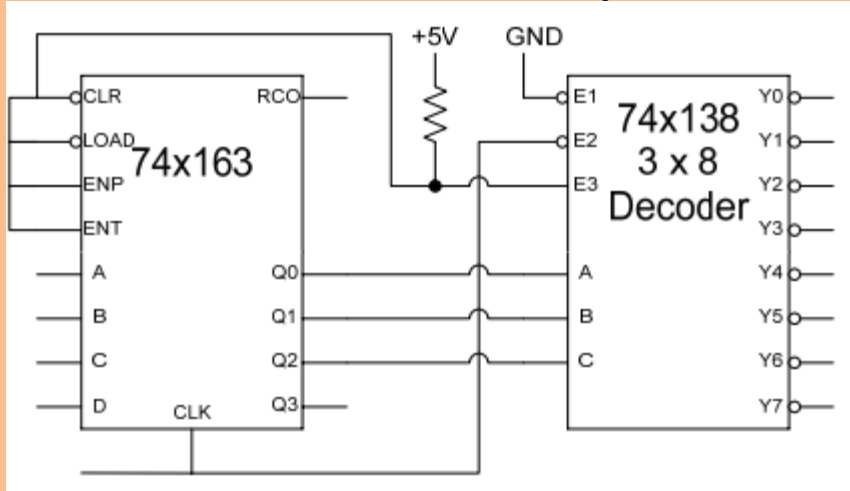
**74x138 Decoder enabled by a clock signal**




**Frequency Counter Circuit**

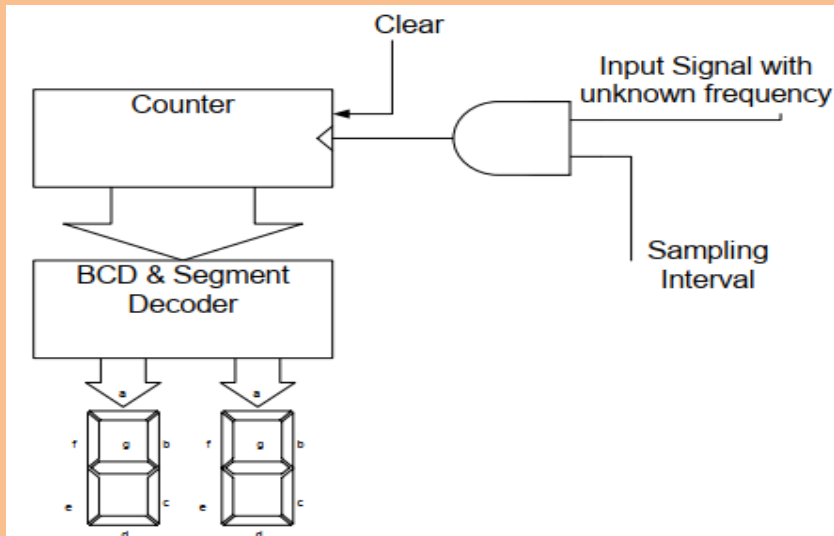

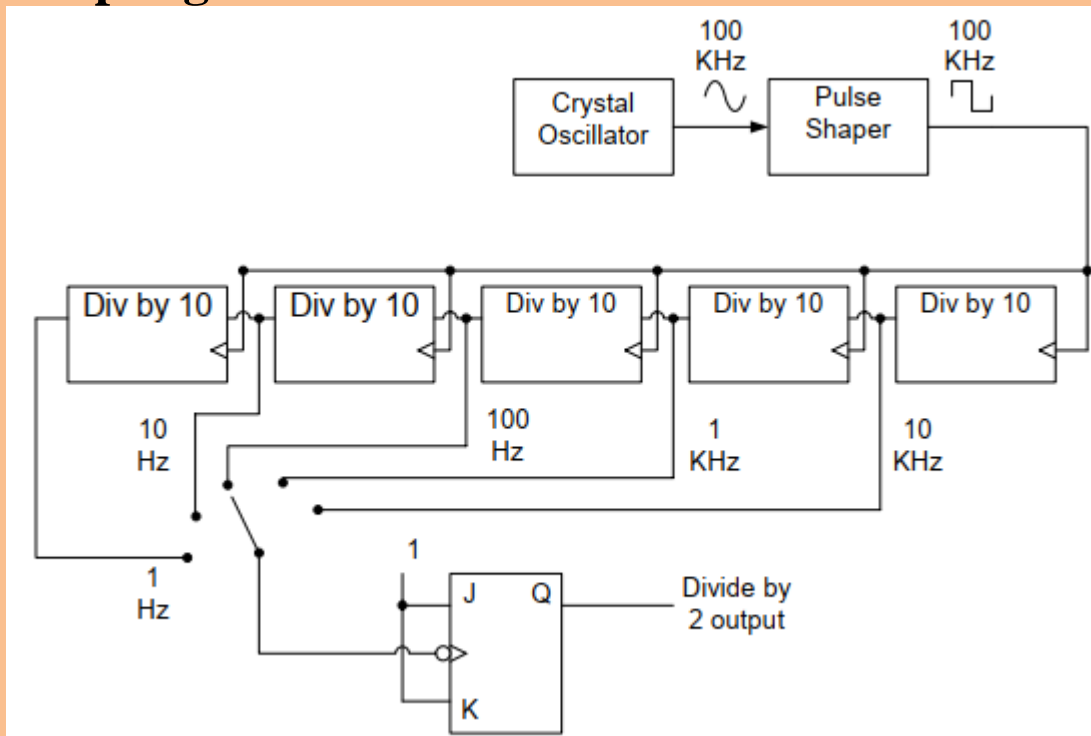
## Cascaded Counter circuit for obtaining accurate sampling intervals



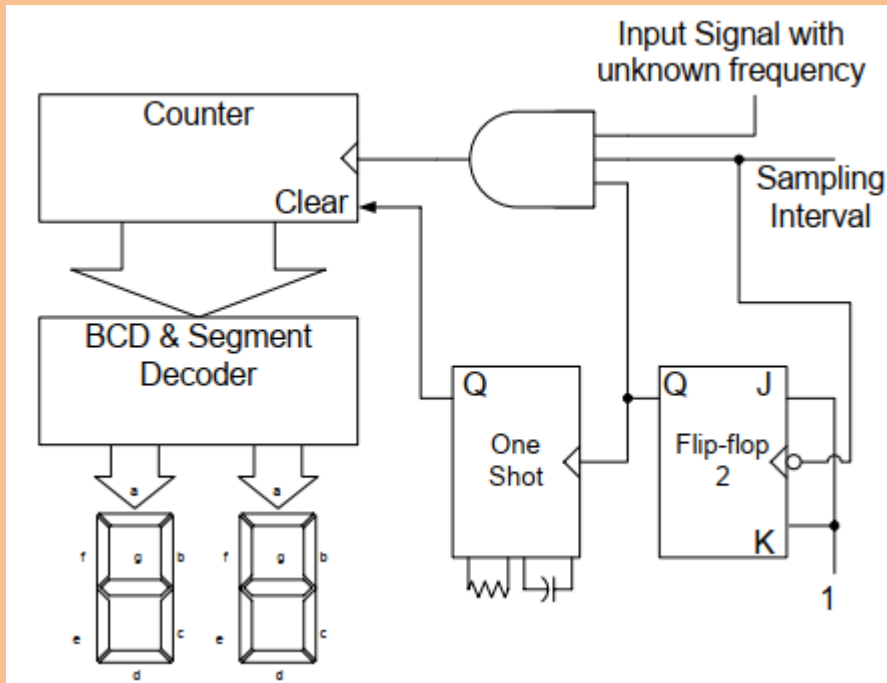
## Detailed circuit diagram of a frequency counter


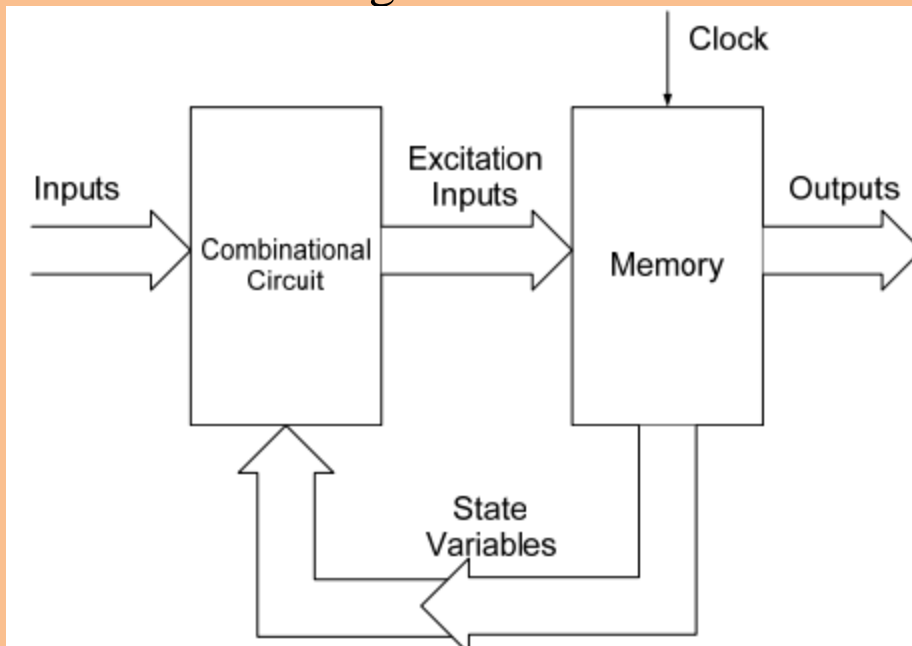
## Sequential Circuit (State Machine) Clocked Sequential Circuit Block diagram




## State diagram of a 3-bit Up-Counter

 

### Next-State Table for a 3-bit Up-Counter

Present State			Next State		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

### State diagram of a 3-bit Up-Counter

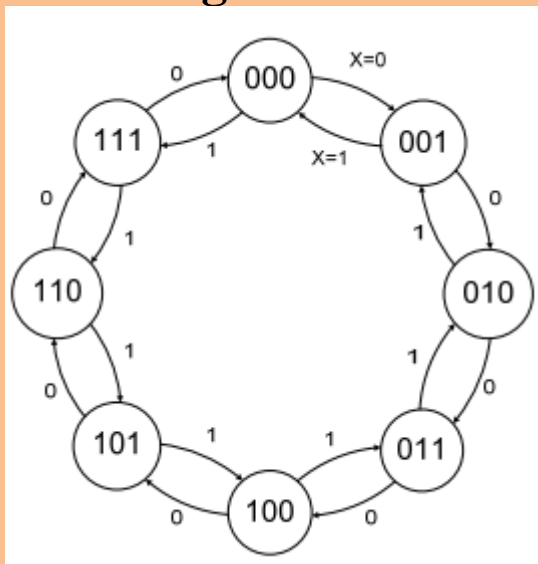

### Next-State Table for a 3-bit Up-Counter

Present State			Next State X=0			Next State X=1		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0


### J-K flip-flop input table for X=0

Present State			Next State X=0			J-K flip-flop inputs					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
0	0	0	0	0	1	0	x	0	x	1	x
0	0	1	0	1	0	0	x	1	x	x	1
0	1	0	0	1	1	0	x	x	0	1	x
0	1	1	1	0	0	1	x	x	1	x	1
1	0	0	1	0	1	x	0	0	x	1	x
1	0	1	1	1	0	x	0	1	x	x	1
1	1	0	1	1	1	x	0	x	0	1	x
1	1	1	0	0	0	x	1	x	1	x	1


### J-K flip-flop input table for X=1

Present State			Next State X=1			J-K flip-flop inputs					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>
0	0	0	1	1	1	1	x	1	x	1	x
0	0	1	0	0	0	0	x	0	x	x	1
0	1	0	0	0	1	0	x	x	1	1	x
0	1	1	0	1	0	0	x	x	0	x	1
1	0	0	0	1	1	x	1	1	x	1	x
1	0	1	1	0	0	x	0	0	x	x	1
1	1	0	1	0	1	x	0	x	1	1	x
1	1	1	1	1	0	x	0	x	0	x	1

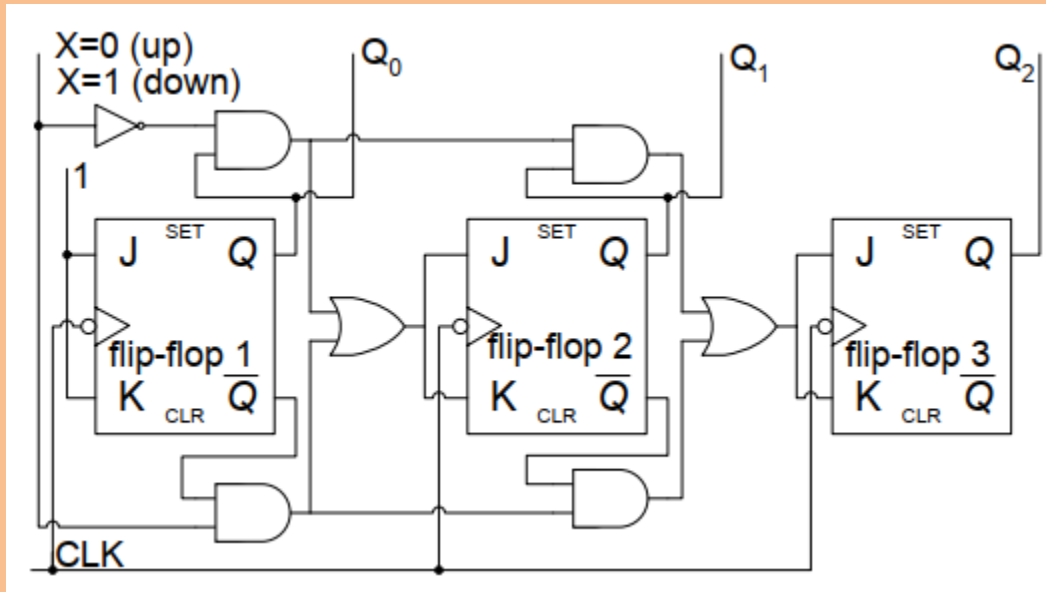
### Implementation of the Sequential Circuit



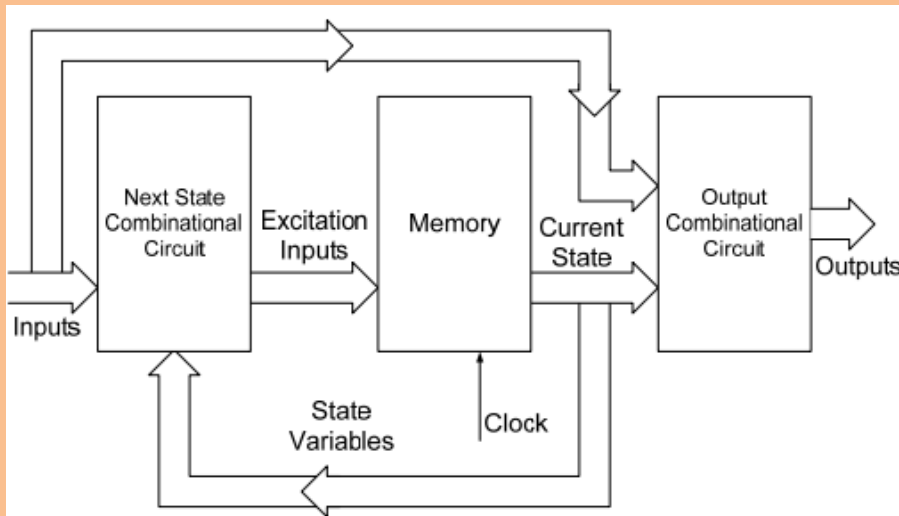
**Clocked Sequential State Machine (Mealy Machine)**



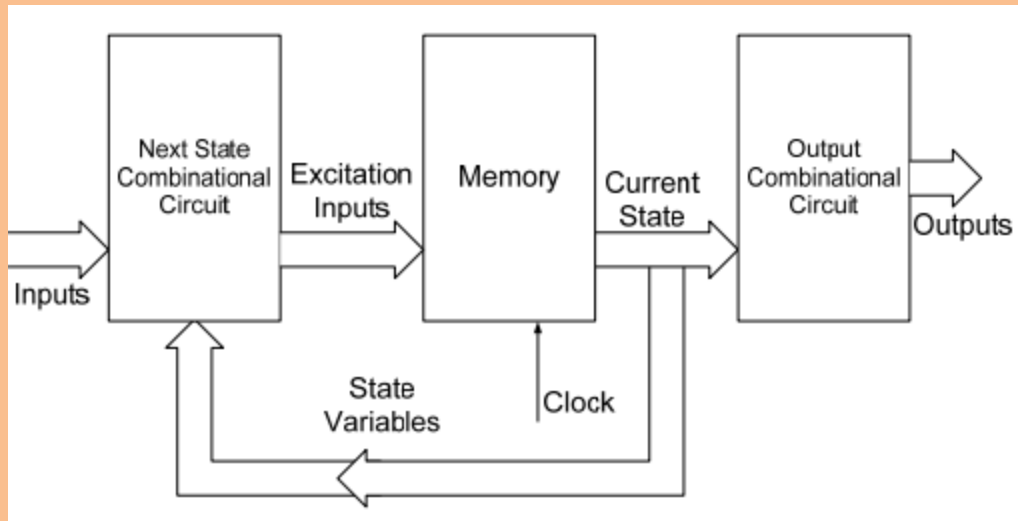
**Clocked Sequential State Machine (Moore Machine)**


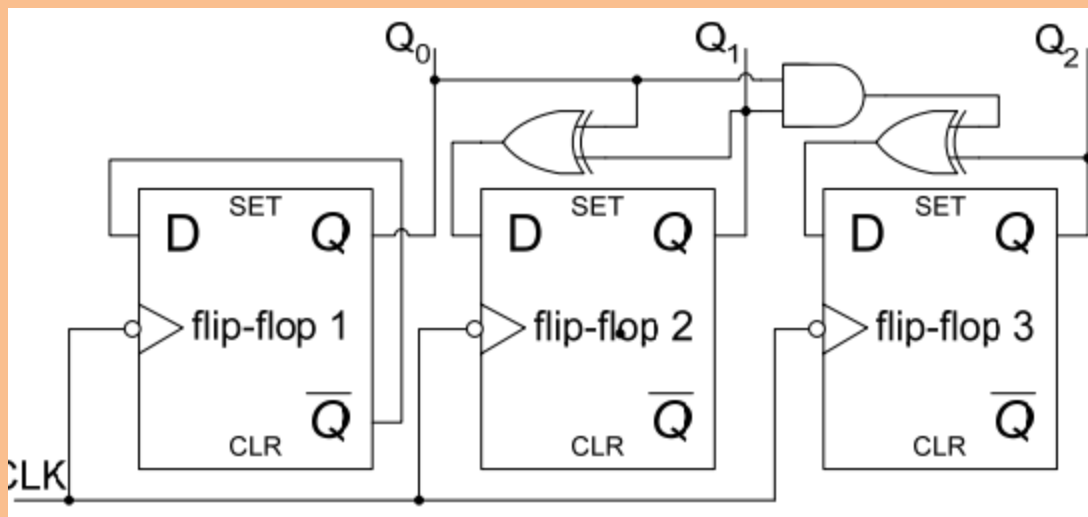
## D flip-flop based implementation of 3-bit Synchronous Counter




## State diagram of a 3-bit Up-Counter

 


## Next-State Table for a 3-bit Up-Counter

Present State			Next State X=0			Next State X=1		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	0	0	1	1	1	1
0	0	1	0	1	0	0	0	0
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	0	1	0
1	0	0	1	0	1	0	1	1
1	0	1	1	1	0	1	0	0
1	1	0	1	1	1	1	0	1
1	1	1	0	0	0	1	1	0
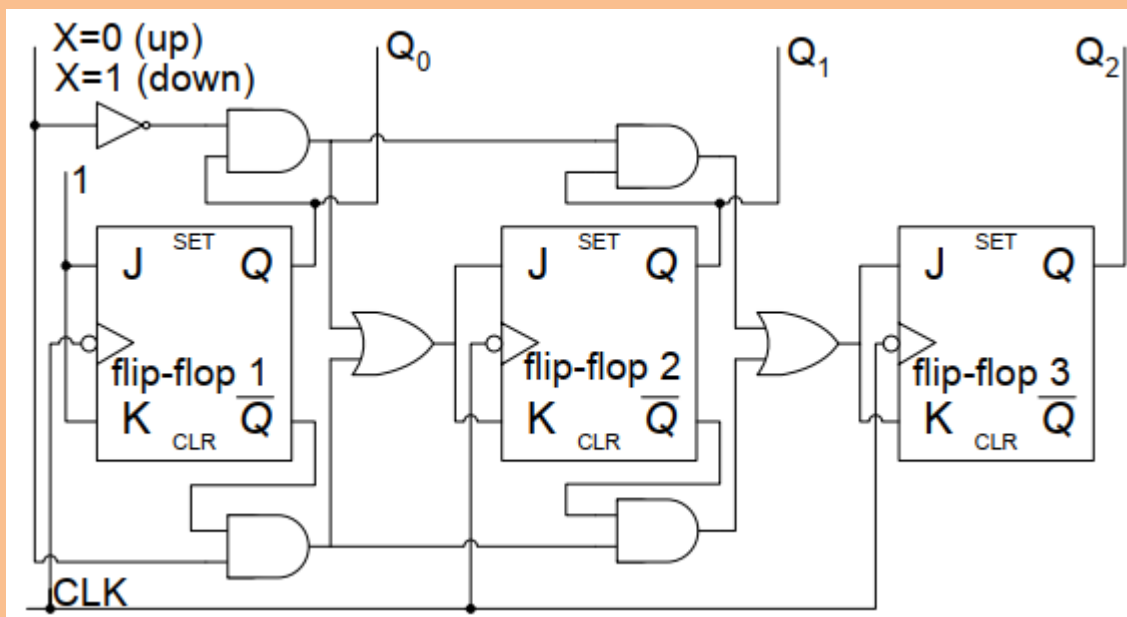
## Implementation of the Sequential Circuit




## State Reduction \ State diagram

 

The input and output table of **State Reduction** sequence

state	a	b	c	f	d	d	e	g	d	e	a	f	d	e	a
Input	1	1	1	0	1	0	1	0	0	0	0	0	0	0	
Output	0	1	1	0	0	1	1	0	1	0	0	0	1	0	


## Simplified State diagram

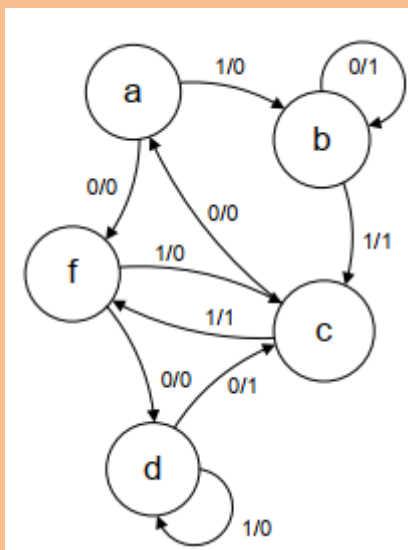

The input and output sequence obtained from the simplified state diagram

state	a	b	c	f	d	d	c	f	d	c	a	f	d	c	a
Input	1	1	1	0	1	0	1	0	0	0	0	0	0	0	
Output	0	1	1	0	0	1	1	0	1	0	0	0	1	0	


## State diagram of a Moore Machine

 


## Next-State table of the Moore Machine

Present State			Next State		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	1	1	1	1	1
1	1	1	0	0	1
0	0	1	0	1	0
0	1	0	1	0	0
1	0	0	1	1	0
1	1	0	0	1	1

## Implementation of the Moore Machine

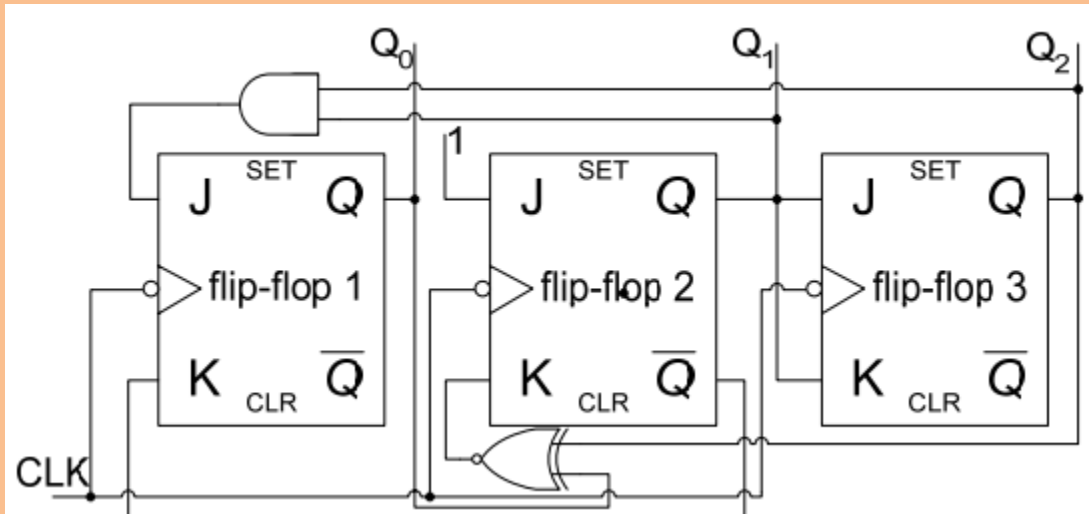


**State diagram of a Mealy Machine**

 


**Next-State table of a Mealy Machine**

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
a	a	b	011	111
b	b	c	111	001
c	c	d	001	010
d	d	e	010	100
e	e	f	100	110
f	f	a	110	011

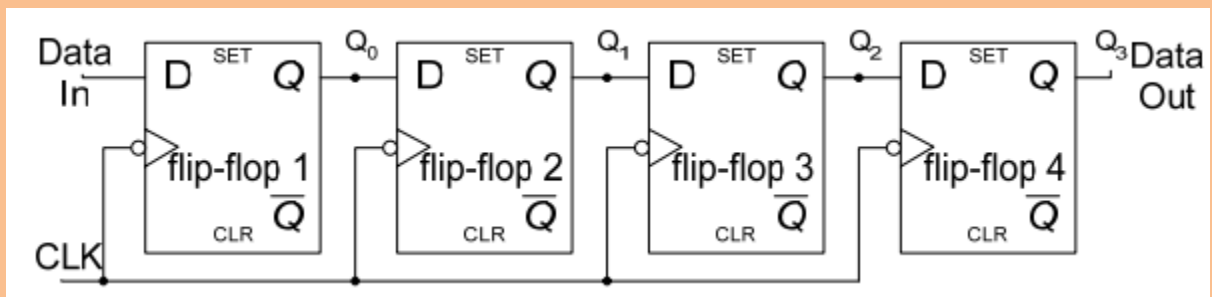
## Serial In/Shift Right/Serial Out Register




## Bi-directional, 4-bit Shift register

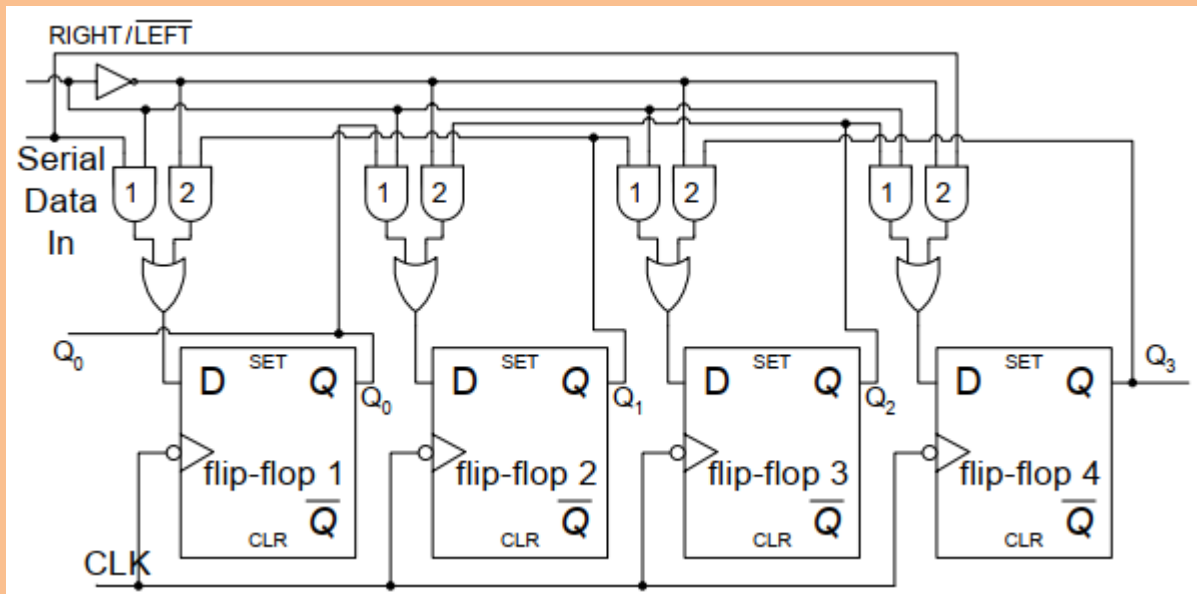

 
## 74HC164, 8-bit Serial In/Parallel Out Shift Register



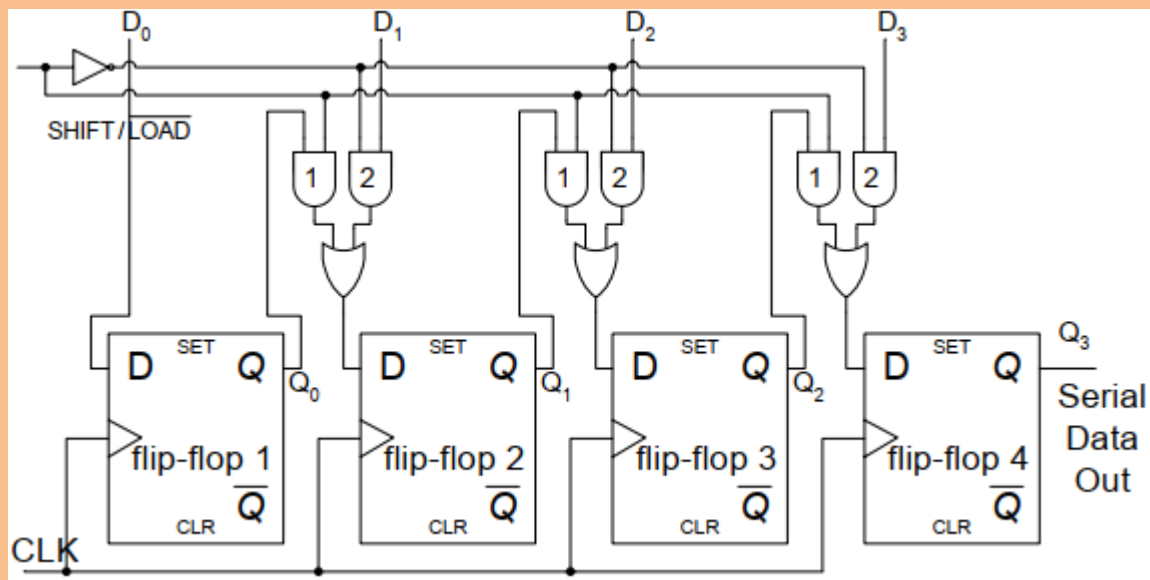
## 4-bit Parallel In/Serial Out Shift register



 
## 74HC165, 8-bit Parallel In/Serial Out Shift Register




## Parallel In/Parallel Out Operation

 

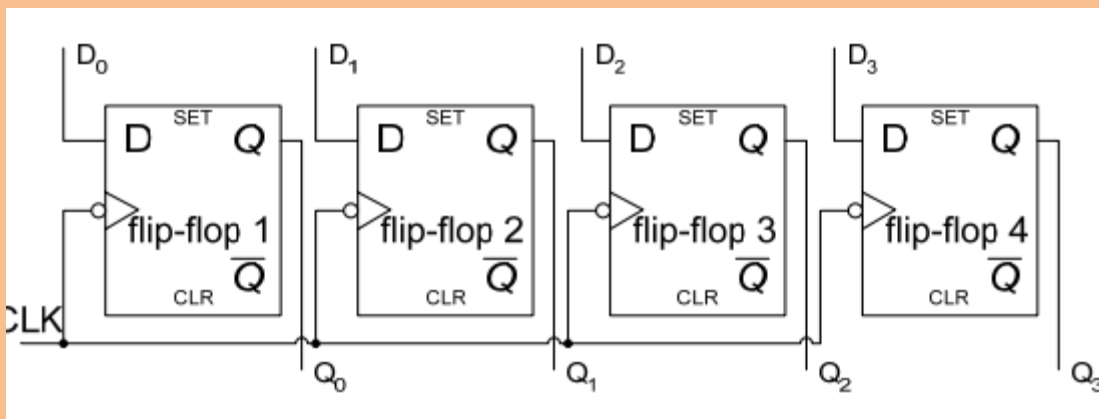
## A D-flip-flop based 4-bit Parallel In/Parallel Out Register



 
## 74HC195, 4-bit Parallel In/Parallel Out Shift Register


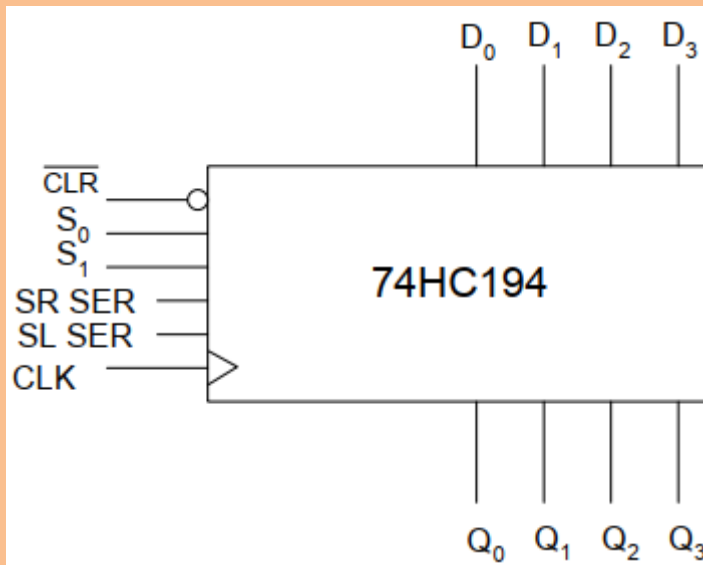
## Bi-directional 4-bit Universal Shift Register




## 4-bit Johnson Counter

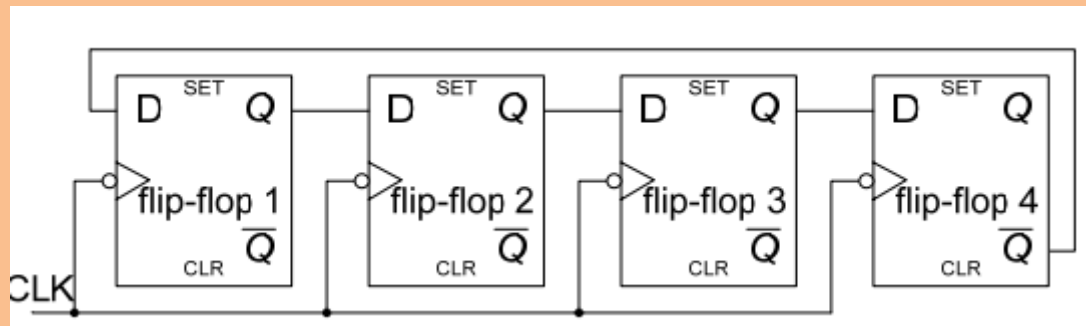

## Sequence of states of a 4-bit Johnson Counter

Clock Pulse	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1


## 4-bit Ring Counter

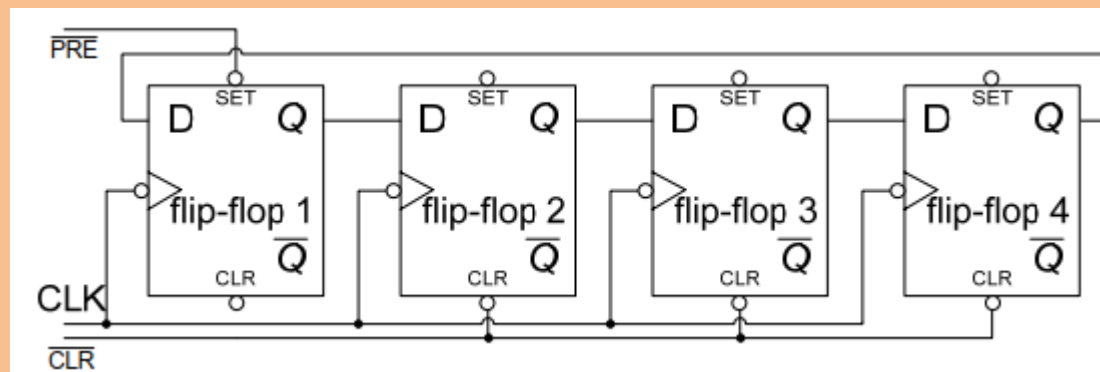

## Sequence of states of a 4-bit Ring Counter


Clock Pulse	Q <sub>0</sub>	Q <sub>1</sub>	Q <sub>2</sub>	Q <sub>3</sub>
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1

## Series-to-Parallel Converter

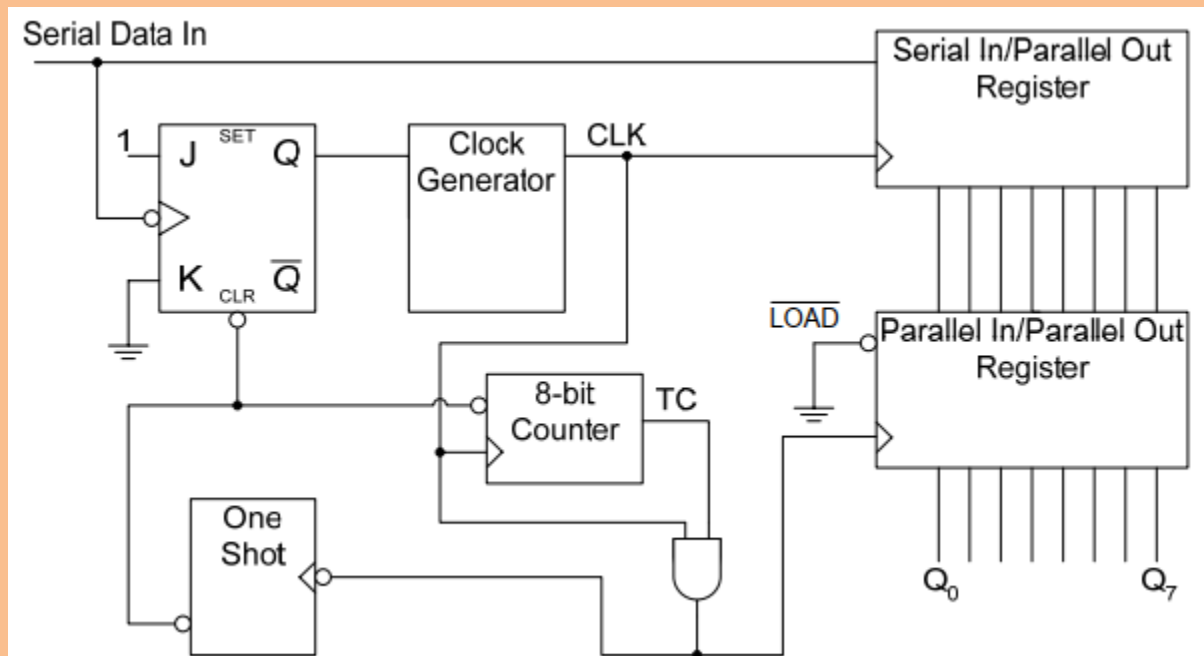


## OLMC of the GAL22V10 device




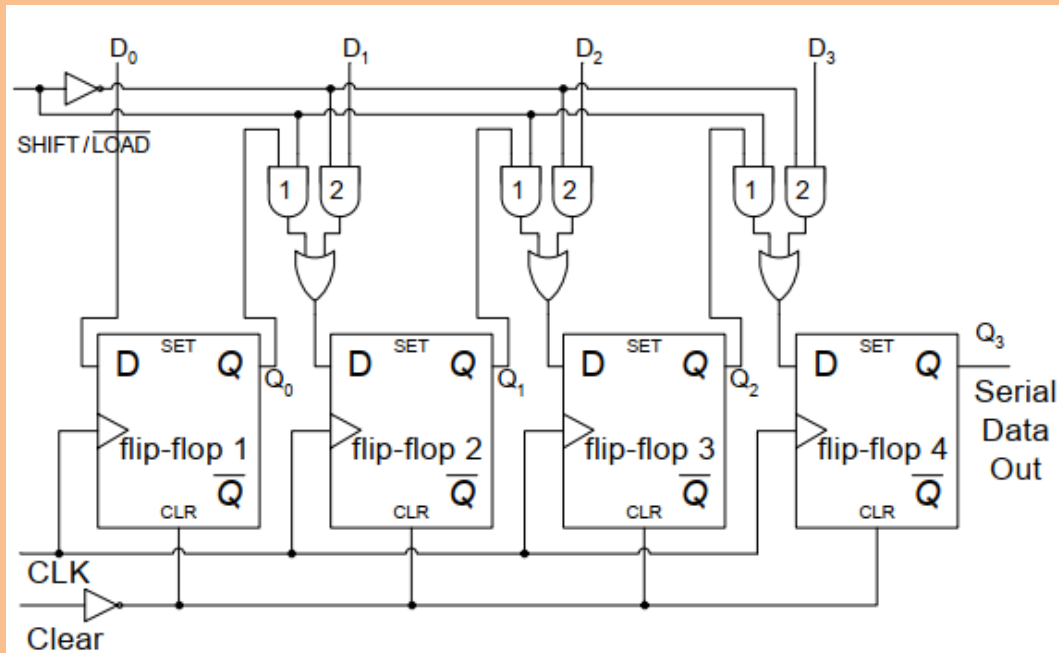


### 3-bit Up/Down Counter

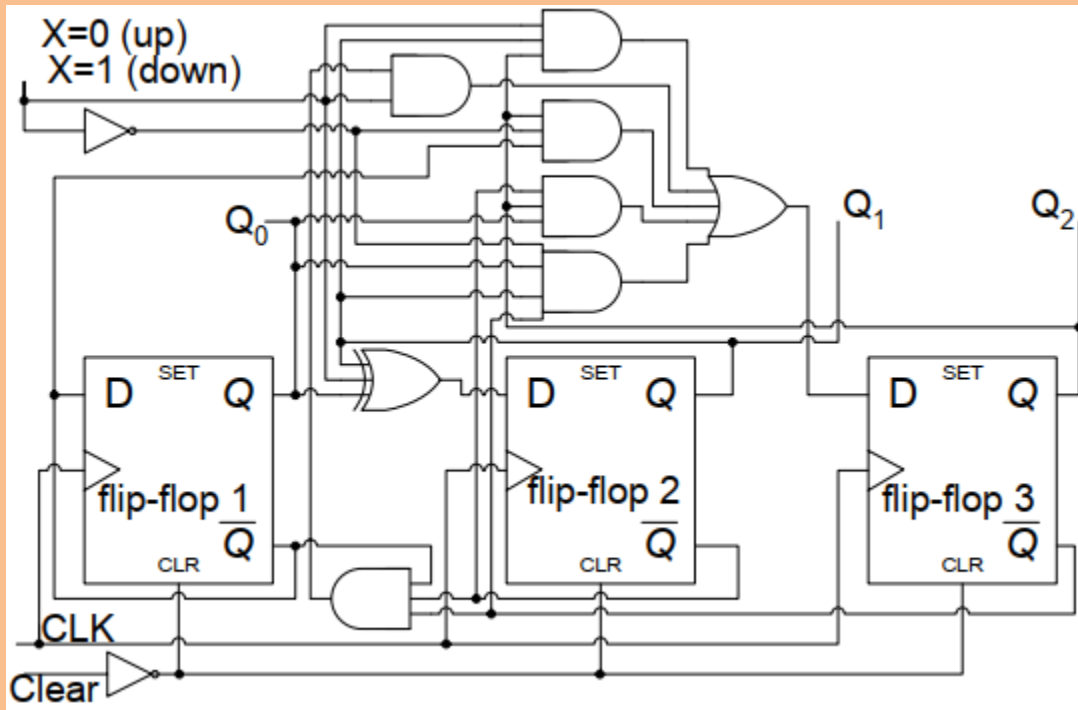


### State Diagram of Elevator

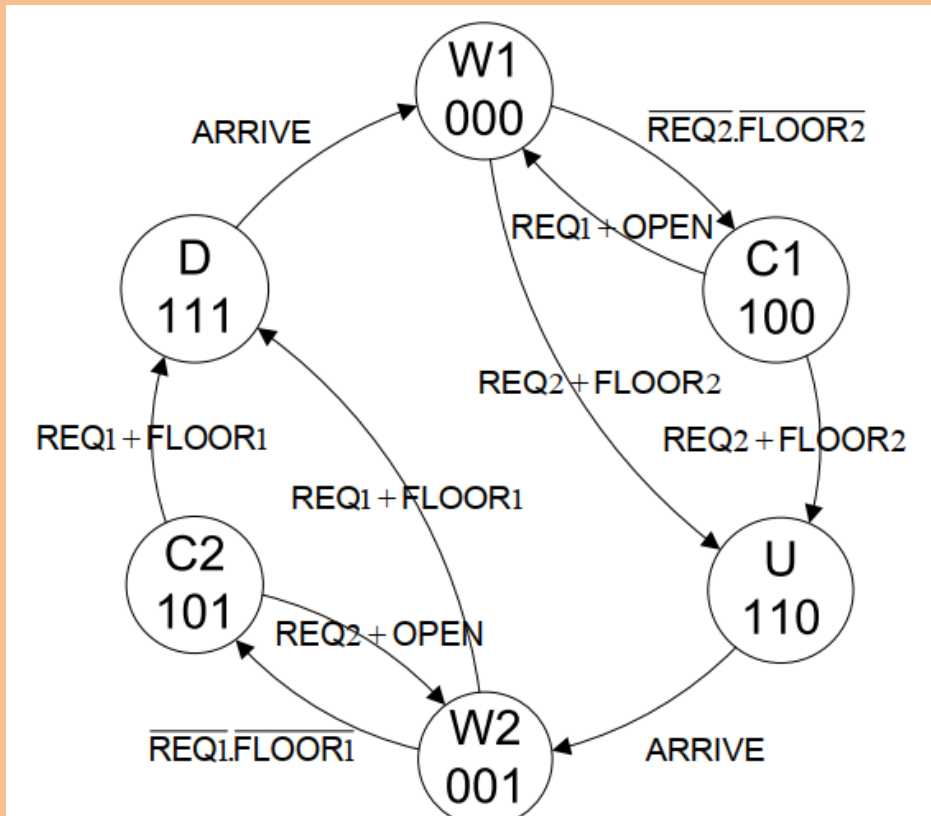
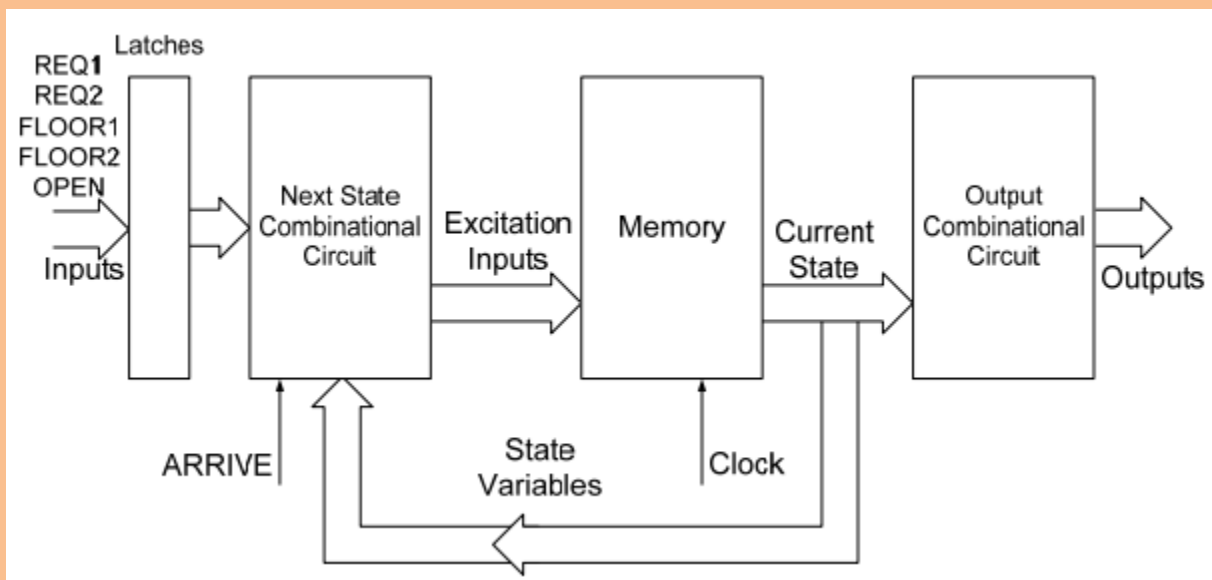
## Block diagram of the Elevator State Machine



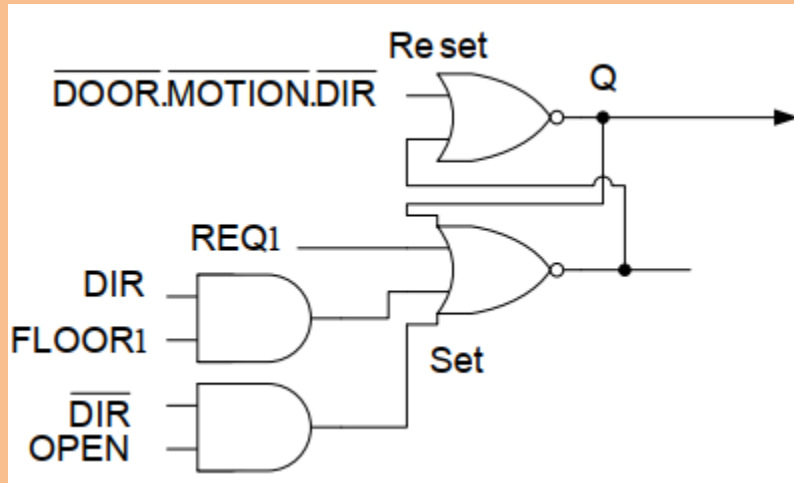
**The circuit diagram of the SR1 latch \ SR1 latch which stores the status of the REQ1, FLOOR1 and OPEN buttons**



**Simplified State table for Elevator Control for REQ1, FLOOR1 and OPEN inputs**

Present State	Next State	Next State
	SR1=0	SR1=1
W1(000)	x	x
C1(100)	C1	W1
UP(110)	x	x
W2(001)	C2	DO
C2(101)	C2	DO
DO(111)	x	x

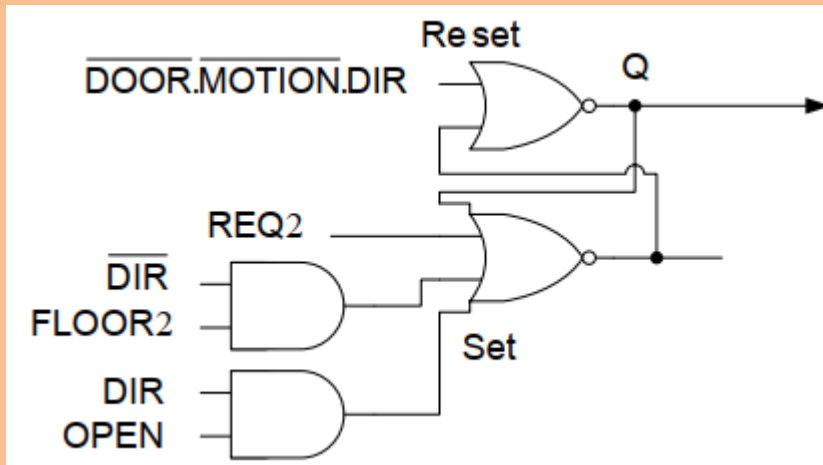
**The circuit diagram and the Boolean expression can similarly be represented \ SR2 latch which stores the status of the REQ2, FLOOR2 and OPEN buttons**



**Simplified State table for Elevator Control for REQ2, FLOOR2 and OPEN inputs**

Present State	Next State	Next State
	SR2=0	SR2=1
W1(000)	C1	UP
C1(100)	C1	UP
UP(110)	x	x
W2(001)	x	x
C2(101)	C2	W2
DO(111)	x	x

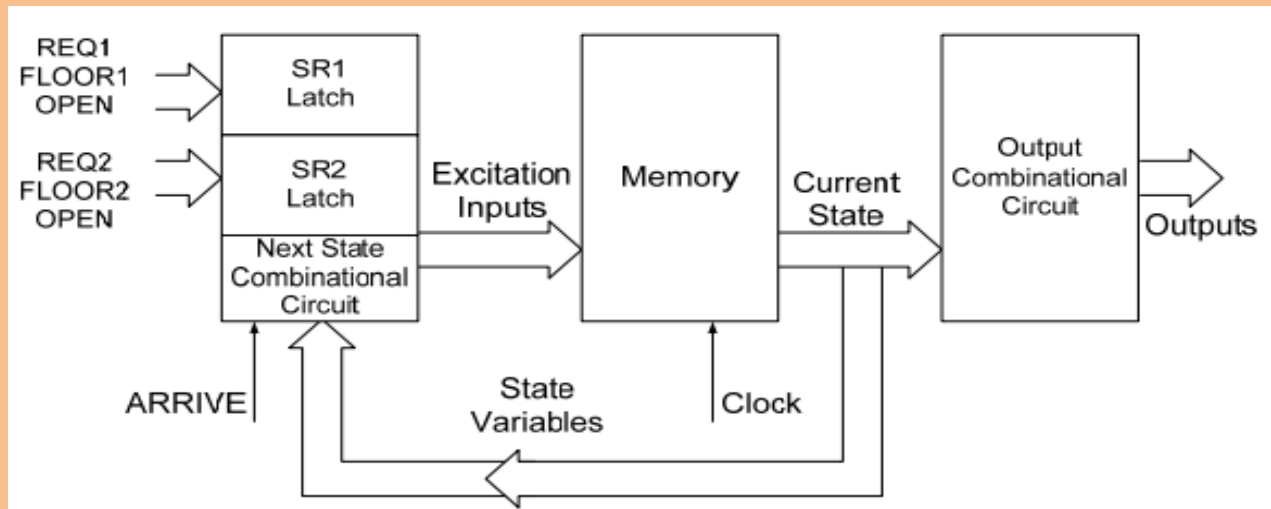**Modified Block diagram of the Elevator State Machine \ The Next State Table for the Elevator State Machine based on the inputs SR1, SR2 and ARRIVAL**



## Traffic Signal Controller Inputs and Outputs

The State Machine which controls the Traffic Signal has several inputs and outputs.

The inputs are the

- **NSSR:** The NSSR is activated when a car is over either of the four sensors on the NorthSouth section of the road
- **EWSR:** The EWSR is activated when a car is over either of the four sensors on the EastWest section of the road

A Timer is used to count the 5 minute and 1 minute traffic signal cycle during the day and night. Two signals **LTIME** and **STIME** provide the timing inputs to the State Machine.

- **LTIME:** The LTIME signal is activated if 5 minutes have elapsed; the signal remains active unless the timer is reset.
- **STIME:** The STIME signal is activated if 1 minute has

elapsed; the signal remains active unless the timer is reset.


The outputs of the State Machine are

- NSGrn: The Green signal controlling the traffic on the North-South section
- NSYel: The Yellow signal controlling the traffic on the North-South section


NSRed: The Red signal controlling the traffic on the North-South section

- EWGrn: The Green signal controlling the traffic on the East-West section
- EWYel: The Yellow signal controlling the traffic on the East-West section
- EWRed: The Red signal controlling the traffic on the East-West section
- TMRST: The Reset signal which resets the timer after the LTIME or the STIME signals are activated to indicate a time interval of 5 and 1 minutes respectively.

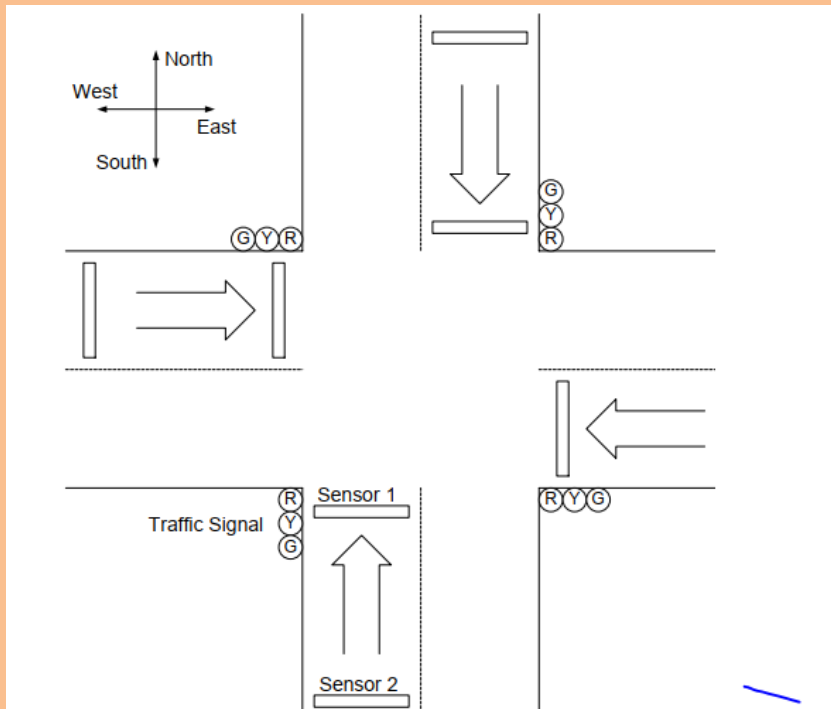
## **The Traffic signals and sensors at a Traffic Intersection**



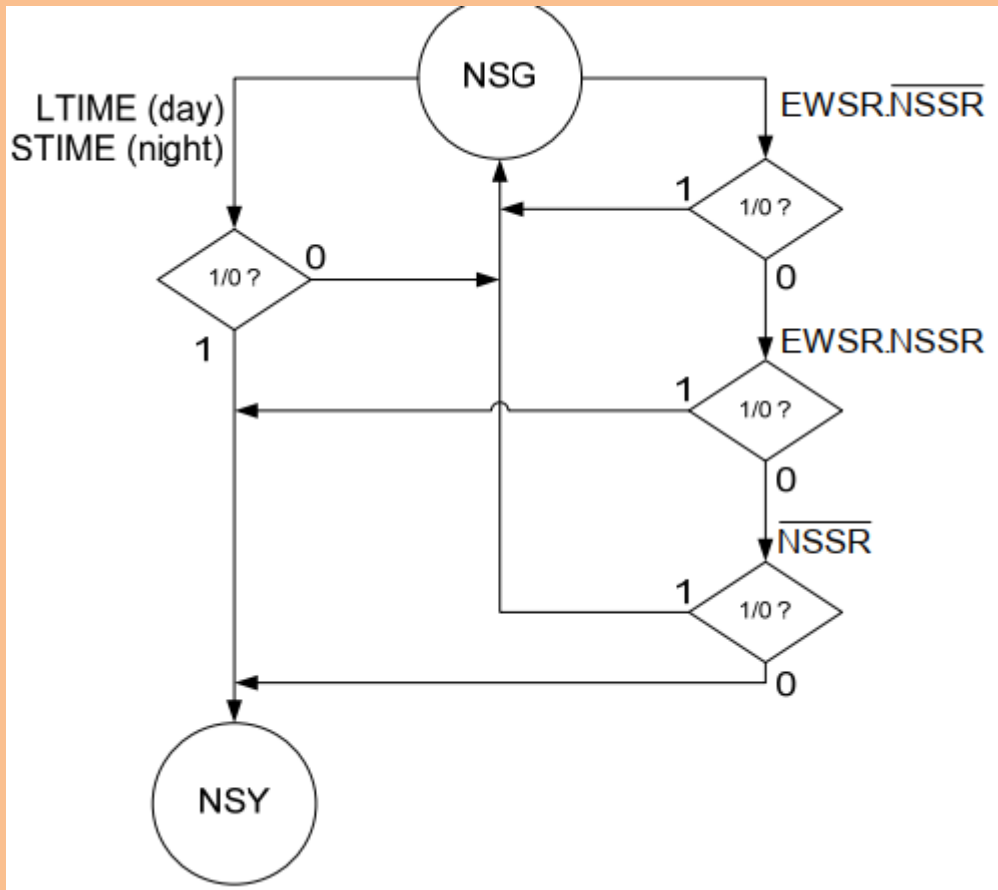
**The State Machine can be implemented using a GAL16V8 device. \ Flow chart of conditions which switch the state from NSG to NSY**



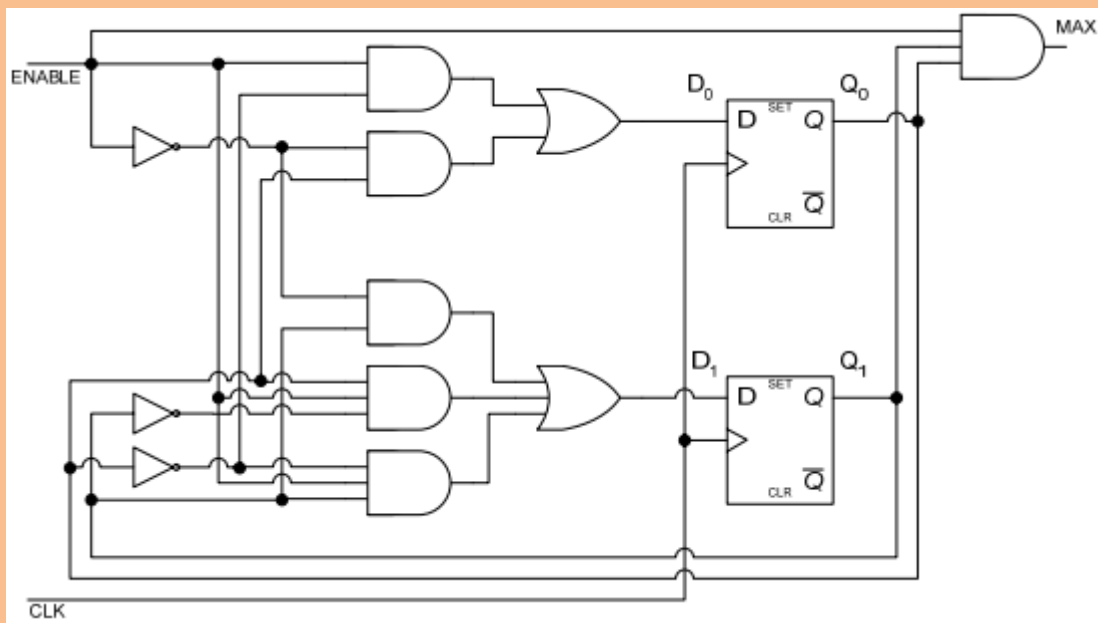
## A State Machine with two positive-edge triggered D flip-flops



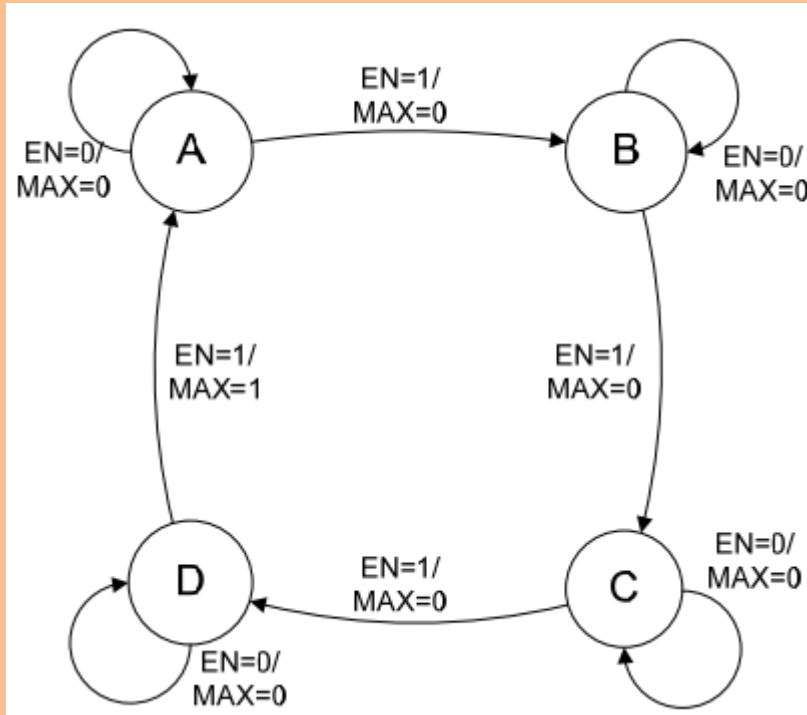
## The State Diagrams for the Mealy State machine derived from the State



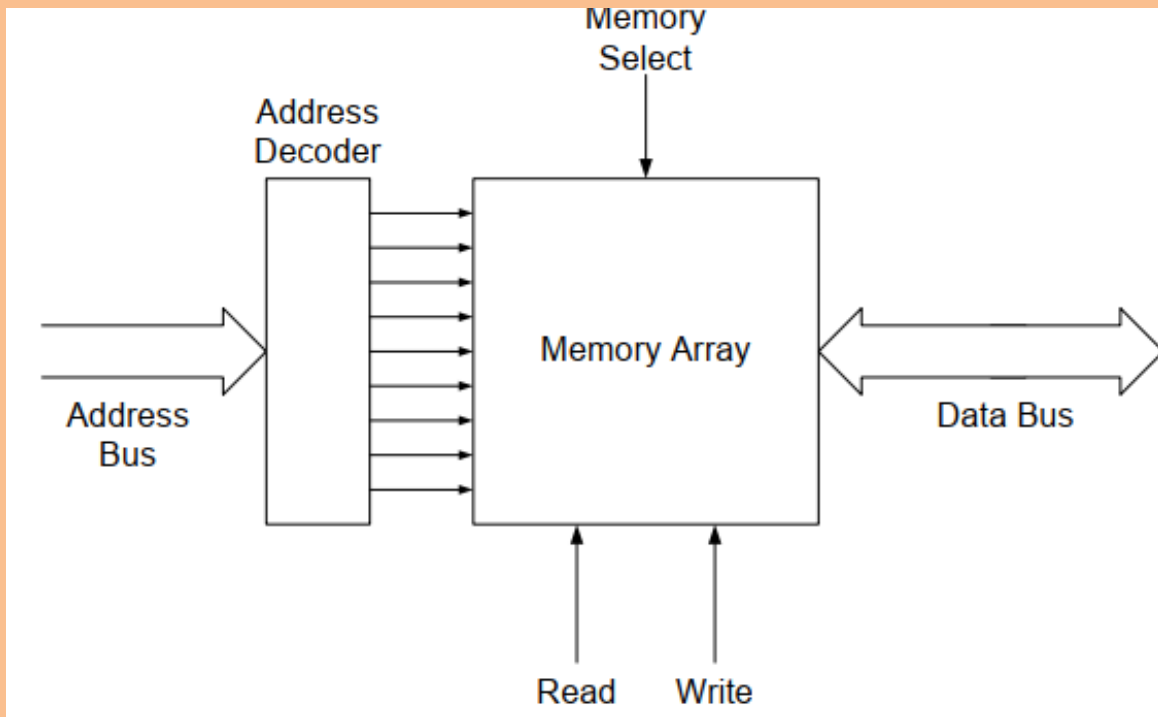
To support the two read and write operations memories provide several signals\ **Block Diagram of a Read-write Memory**




**Memory Read Operation diagram**

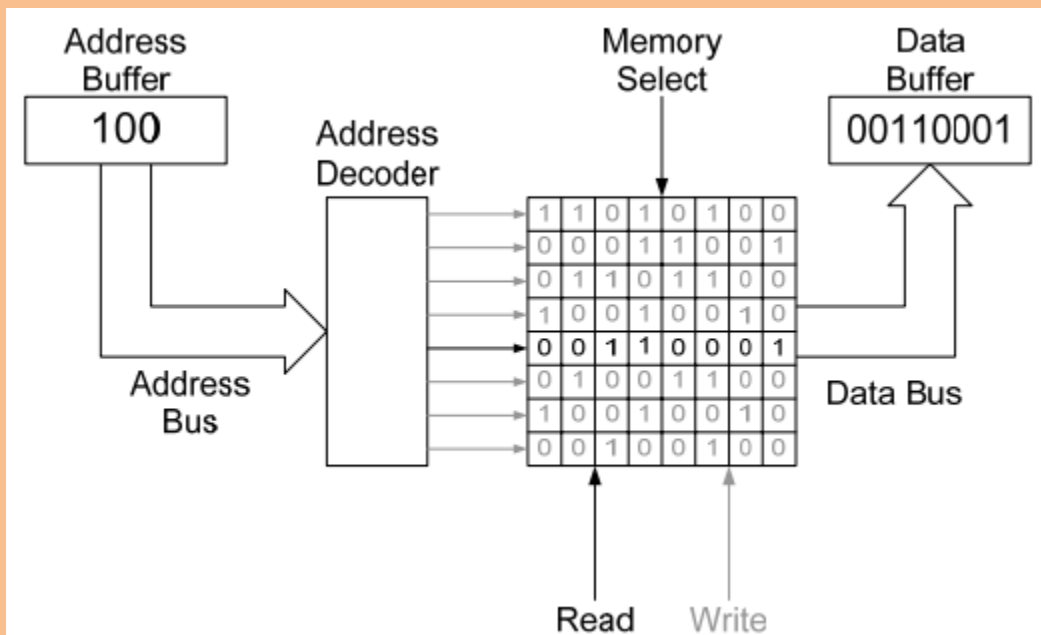


**Memory write Operation diagram**

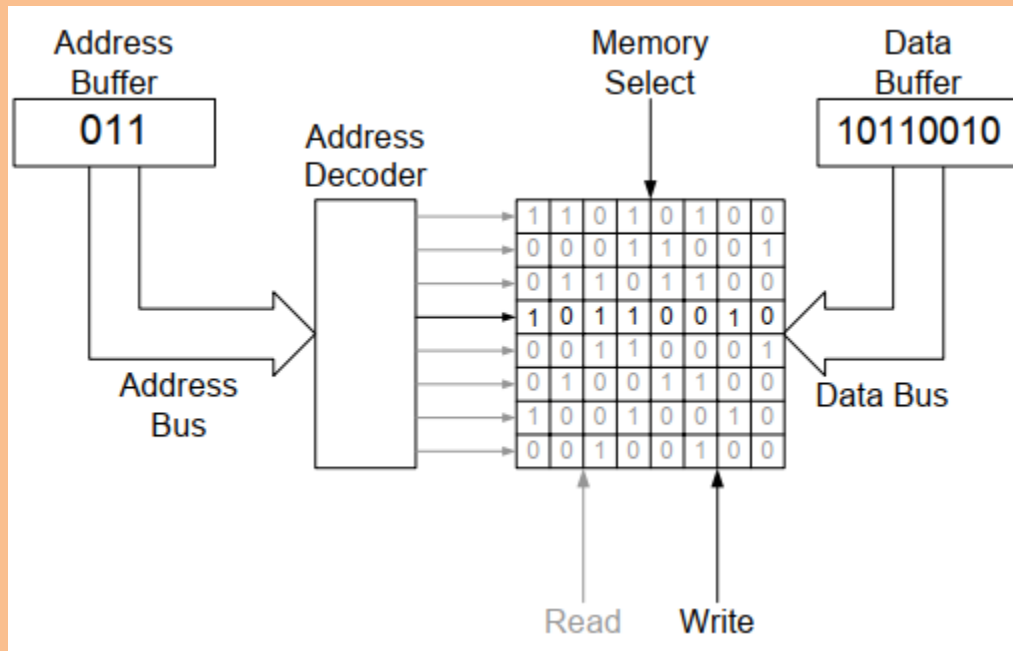

 
**The circuit of a single flipflop based cell which can store a binary 0 or 1**



**16K x 8 Static RAM**

 

## Burst Logic Circuit

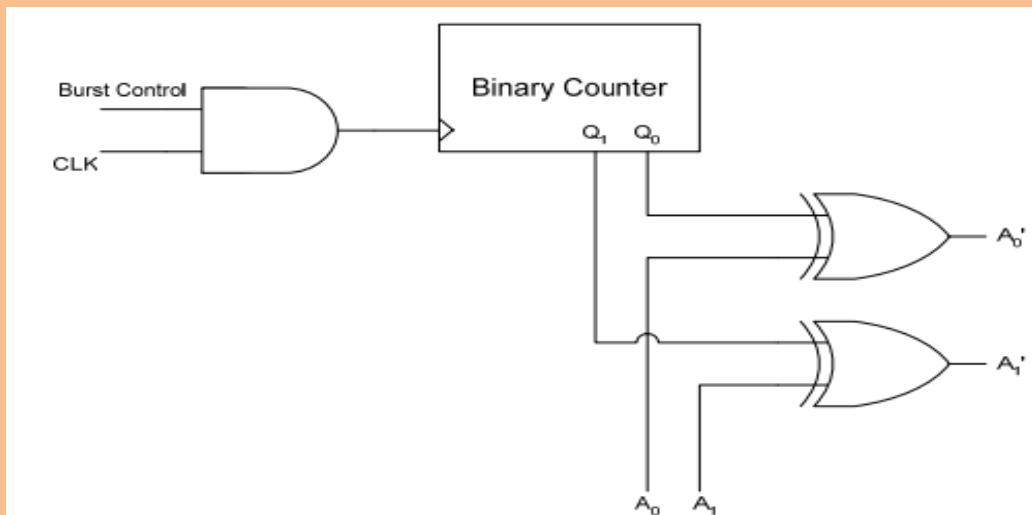


## ROM Read-Only Memory


- Mask ROM: Data is permanently stored during the manufacturing process.

- PROM: Programmable ROM allows storage of data by the user using a PROM programmer. The PROM once programmed stores the data permanently.
- EPROM: Erasable PROM allows erasing of stored data and reprogramming.
- UV EPROM: Is a programmable ROM. Data is erased by exposing the PROM to Ultraviolet light.
- EEPROM: Electrically Erasable PROM is erased electrically. EEPROM allows in-circuit programming and doesn't need to be removed from the circuit for erasure or programming.

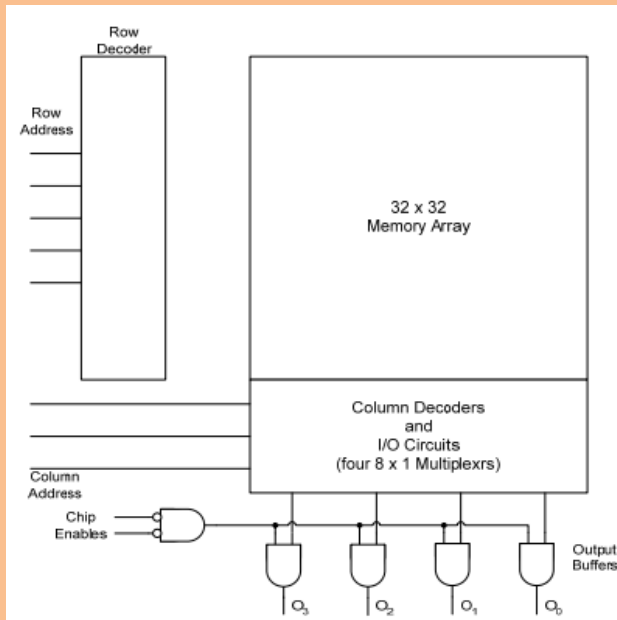
**1 out of 8 column lines by four 8 x 1 Multiplexers\  
Internal structure of a 264 x 4 ROM**


 
## A typical UV EPROM memory chip\ A 2 KB EPROM



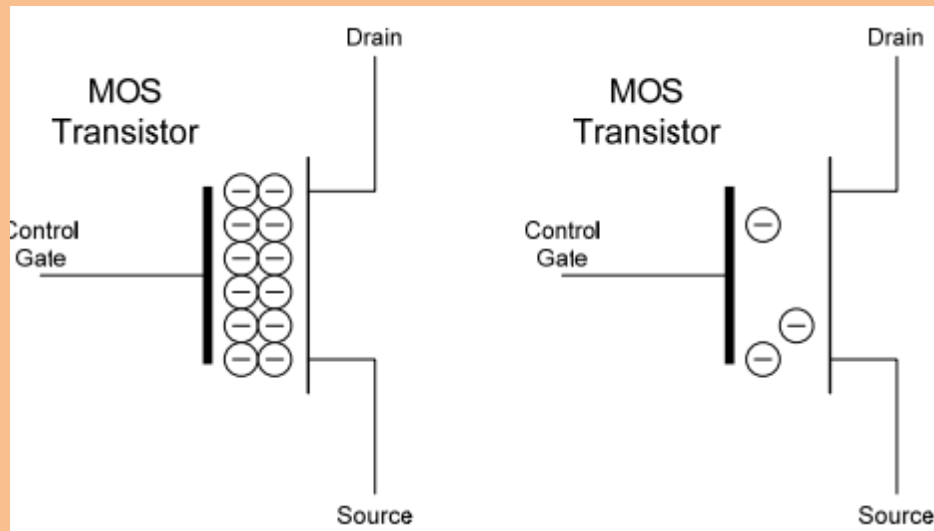**MOS transistor with charge (logic 0) and no charge (logic 1)**




## **FLASH Memory Operations**


FLASH Memory operations are classified into

- Programming Operation
- Read Operation
- Erase Operation

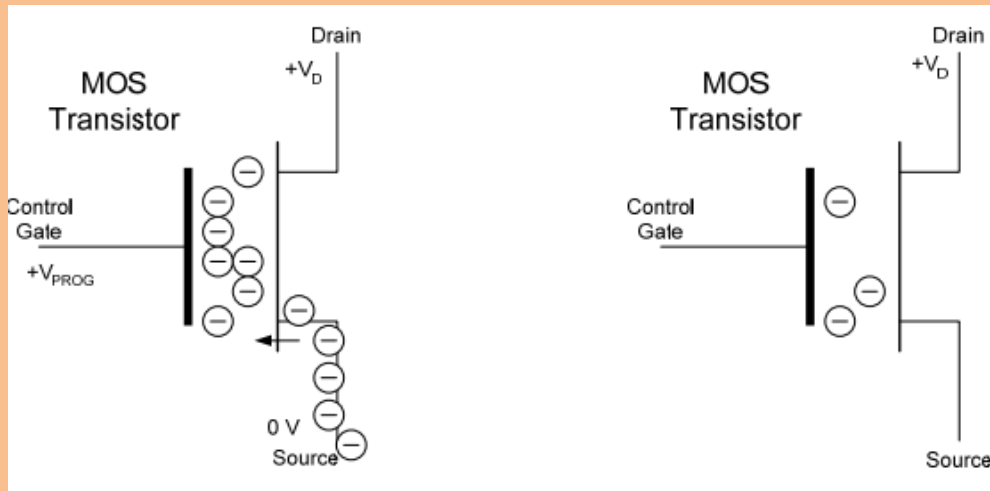
**FLASH Memory Cell programmed with logic 0 and logic 1**



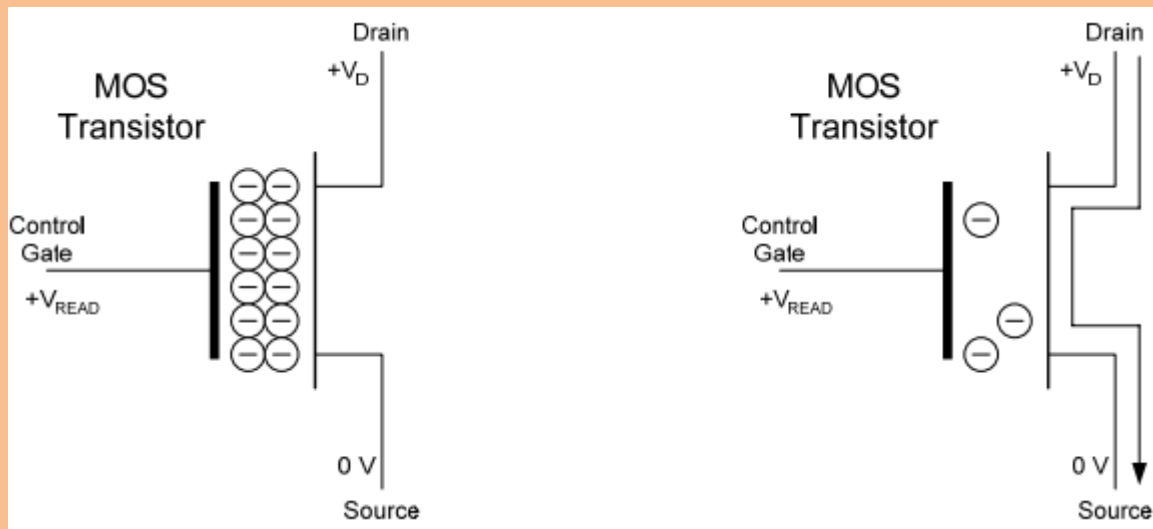
**Read operation to read a logic 0 and a logic 1**



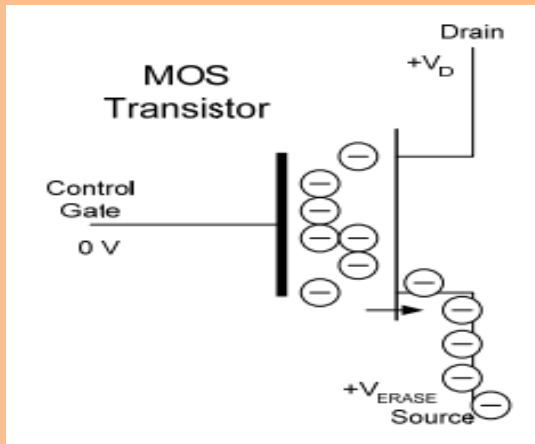**The Erase Operation of the FLASH Memory Cell**



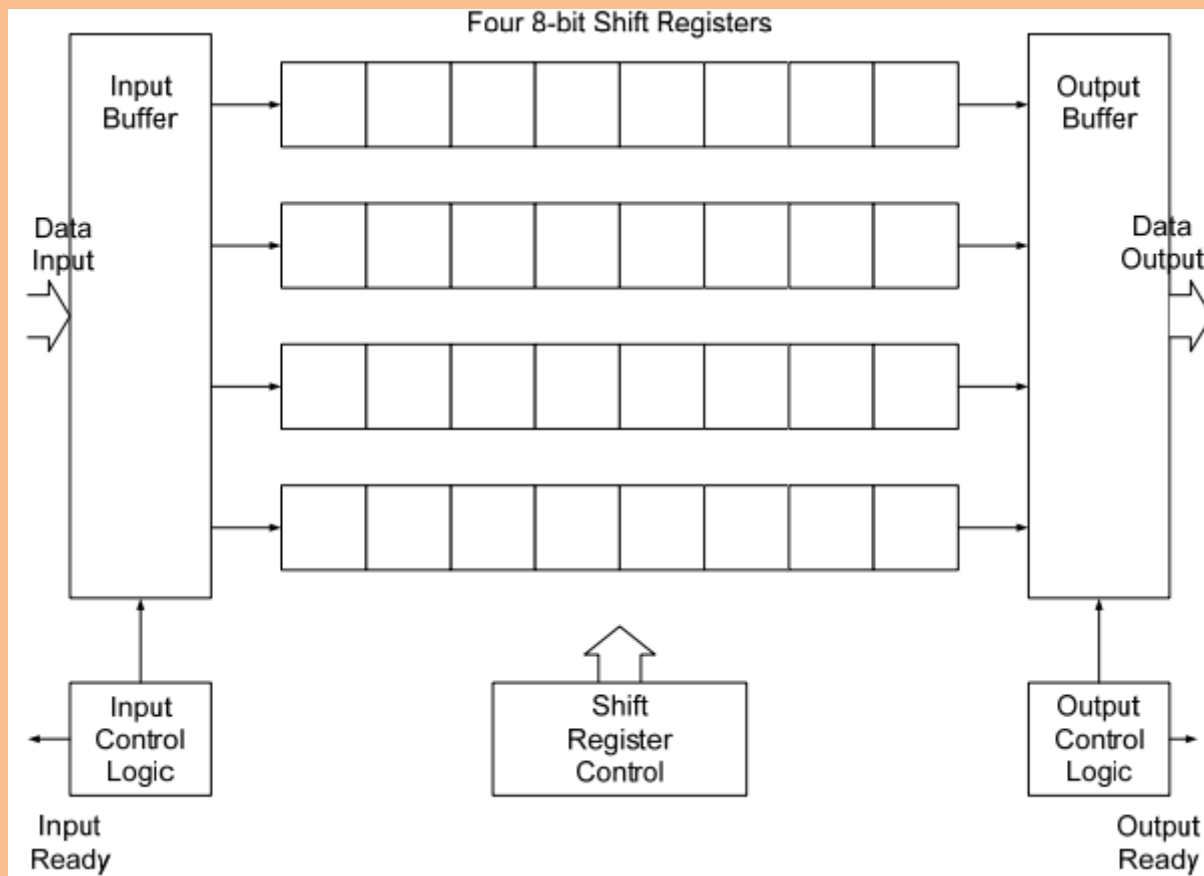
## FIFO Implementation using four 8-bit Shift Registers




## 1 MByte Memory Map

1 Mbyte Memory Space	Base Address
ROM	00000H
Data RAM	10000H
Program RAM	20000H
Vacant	30000H
Vacant	40000H
Vacant	50000H
Vacant	60000H
Vacant	70000H
Vacant	80000H
Vacant	90000H
Vacant	A0000H
Vacant	B0000H
Vacant	C0000H
Vacant	D0000H
Vacant	E0000H
Vacant	F0000H
Stack RAM	

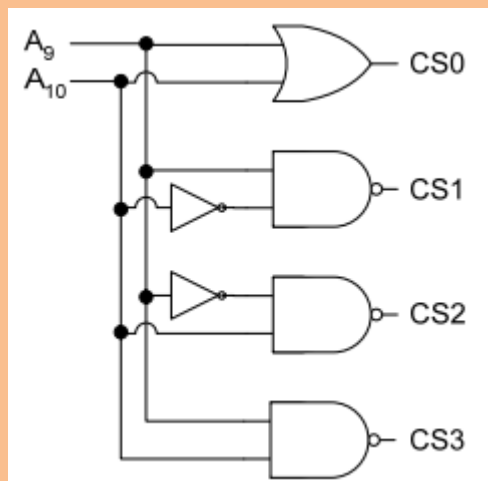**Memory Decoders can be implemented using Logic Gate based Address Decoder**



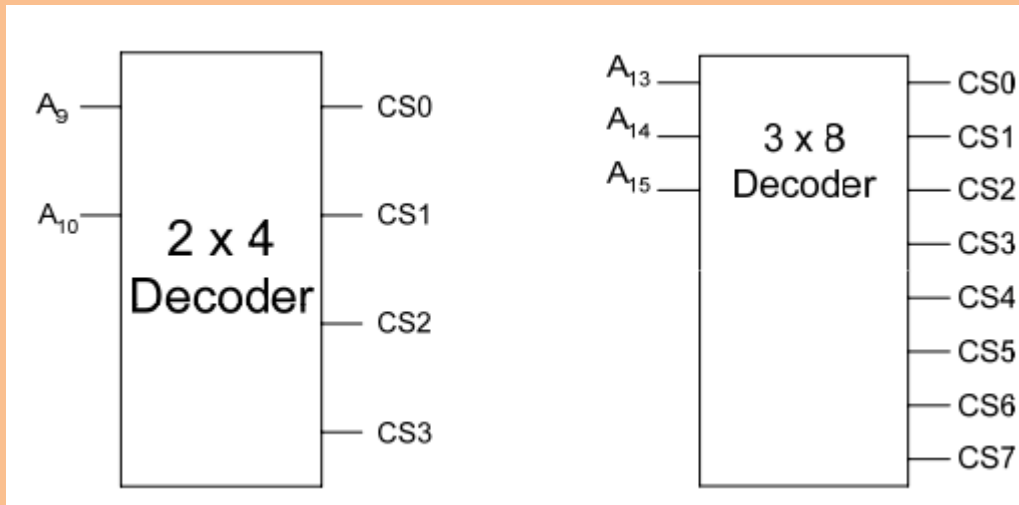**2 x 4 and 3 x 8 Decoder based Address Decoders**



## A 4-bit Binary-Weighted-Input D/A Converter

